

ULTRA-LOW-VOLTAGE (ULV) IC DESIGN: DESIGNING FOR VDD BELOW kT/q

Outline


- 1 The MOSFET : DC and small signal models**
- 2 ULV CMOS logic circuits**
- 3 ULV rectifiers**
- 4 ULV oscillators**

Self-powered applications


Low data rate, low duty cycle, ultra-low power




Solar Keyboard

 


Electronic Shelf Labels

 

Self-powered switches

 

Occupancy Sensor

 

Implantables



Pipelines



Oil Rig

Environmental Awareness




Smoke Detector




Structural sensors

Hard to Reach


TPMS

 

 
Ambient DC power supply voltages are ultra low



$$V_o \cong 50 \text{ mV}$$

 

 
$$V_o \text{ (interiors)} \cong 100 \text{ mV}$$



$$V_o \cong 20-200 \text{ mV}$$

The trend toward low supply voltages

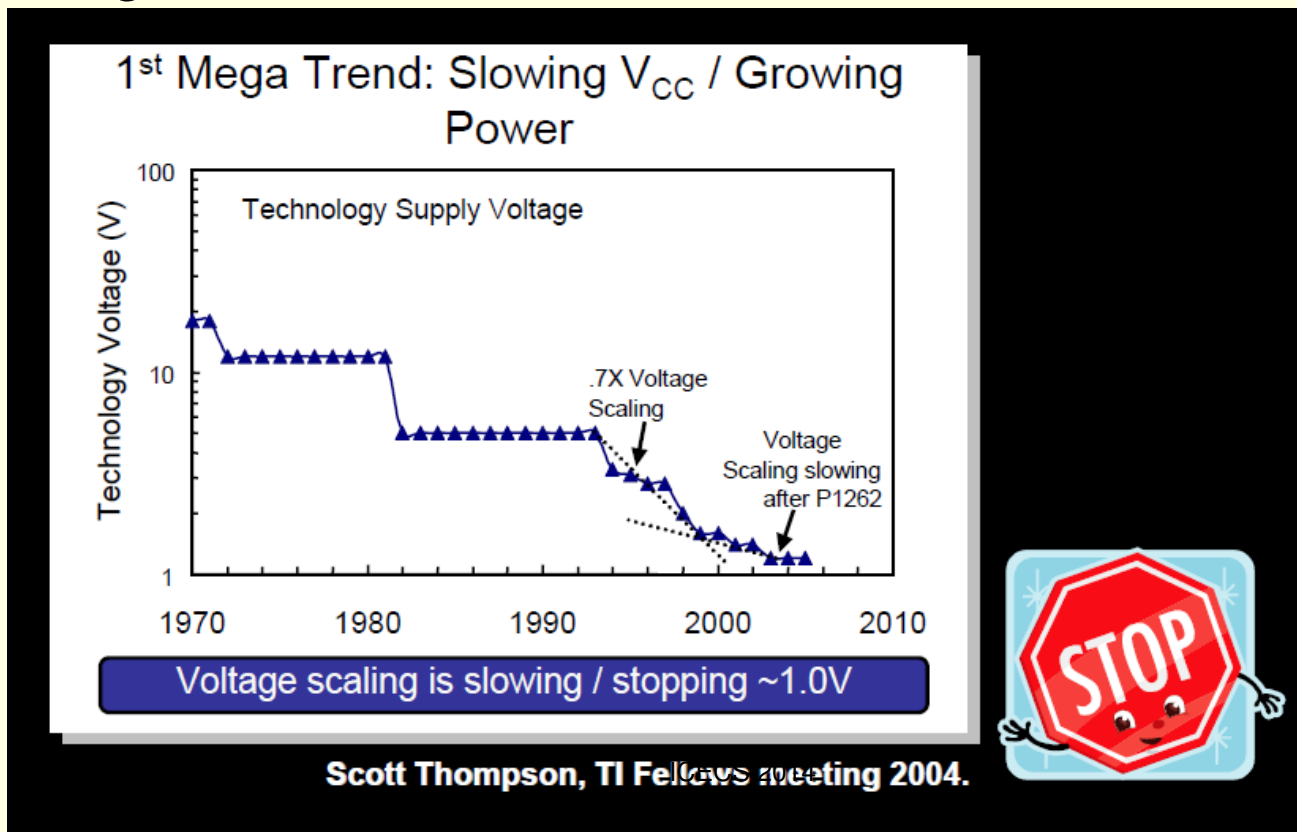
- Q1-Are there lower bounds on the supply voltages to power electronic circuits?
- Q2-What are the best technologies for ultra low voltage circuits?



ULTRA-LOW-VOLTAGE (ULV) IC DESIGN: DESIGNING FOR VDD BELOW kT/q

Chapter 1 The MOSFET : DC and small signal models

MOSFET capacitive model in inversion

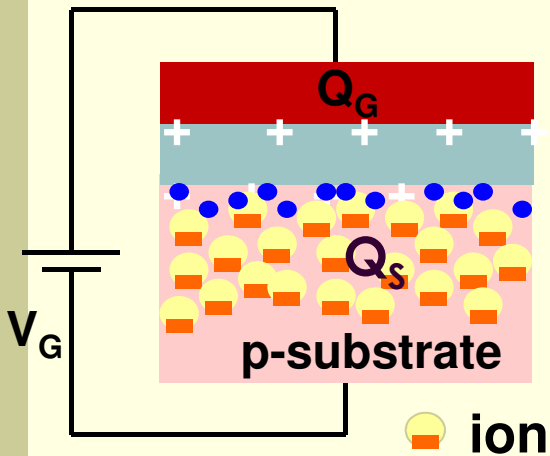

Many electrons ● approach the surface!


ϕ_s - surface potential

C'_{ox} - oxide capacitance/unit area

Q'_G (Q'_s) - gate (semiconductor) charge/ unit area

Q'_i (Q'_B) - inversion (depletion) charge/unit area

 C'_i (C'_b) - inversion (depletion) capacitance /unit area



$$C'_{gb} = \frac{dQ'_G}{dV_G}$$

$$C'_{gb} = \frac{1}{\frac{1}{C'_s} + \frac{1}{C'_{ox}}}$$

$$C'_s = -\frac{dQ'_s}{d\phi_s} = -\frac{d(Q'_B + Q'_I)}{d\phi_s} = C'_b + C'_i$$

Main approximation for compact MOS modeling: the charge-sheet model

Minority carriers occupy a *zero-thickness* layer at the Si-SiO₂

$\phi = \phi_s$ interface, where

$$Q'_I \propto e^{\phi_s / \phi_t} \quad \longrightarrow \quad C'_i = -\frac{dQ'_I}{d\phi_s} = -\frac{Q'_I}{\phi_t}$$

Charge-sheet + depletion approximation for the bulk charge gives


$$Q'_B \cong -qN_A x_d = -\sqrt{2q\epsilon_s N_A \phi_s}$$

$$C'_b \cong \frac{\sqrt{2q\epsilon_s N_A}}{2\sqrt{\phi_s}} = \frac{\gamma C'_{ox}}{2\sqrt{\phi_s}}$$

$$\gamma = \sqrt{2q\epsilon_s N_A} / C'_{ox}$$

is the body-effect coefficient

 
Surface potential for negligible inversion charge : ϕ_{sa}



Threshold voltage $V_G = V_{T0} \leftrightarrow \phi_s \cong 2\phi_F$ $\frac{\Delta\phi_{sa}}{\Delta V_G} \cong \frac{C'_{ox}}{C'_{ox} + C'_b} = \frac{1}{n}$

$\phi_{sa} \cong 2\phi_F + \frac{V_G - V_{T0}}{n} = 2\phi_F + V_P$ V_P is the pinch-off voltage

Unified Charge Control Model-1

 


$$C'_{ox} + C'_b = nC'_{ox}$$

$$n = n(V_G)$$


$$dQ'_I = nC'_{ox} d\phi_s$$

$$C'_i = -\frac{Q'_I}{\phi_t}$$

 

$$dV_C = dQ'_I \left(\frac{1}{nC'_{ox}} - \frac{\phi_t}{Q'_I} \right)$$

$$V_S \leq V_C \leq V_D$$

 

Unified Charge Control Model (UCCM) -2

$$dQ'_I \left(\frac{1}{nC'_{ox}} - \frac{\phi_t}{Q'_I} \right) = dV_C$$

Integrating from an arbitrary channel potential V_C to a reference potential V_P yields UCCM

$$n = 1 + \frac{C'_b}{C'_{ox}} = n(V_G)$$

$$Q'_{IP} = Q'_I \Big|_{V_C=V_P}$$

$$V_P - V_C = \phi_t \left[\frac{Q'_{IP} - Q'_I}{nC'_{ox}\phi_t} + \ln \left(\frac{Q'_I}{Q'_{IP}} \right) \right]$$

Choosing the thermal charge as the pinch-off charge

$$Q'_{IP} = -nC'_{ox}\phi_t$$


The normalized inversion (areal) charge density is

$$\frac{Q'_I}{Q'_{IP}} = q'_I$$

Normalized UCCM

$$V_P - V_C = \phi_t (q'_I - 1 + \ln q'_I)$$

Charge control current model

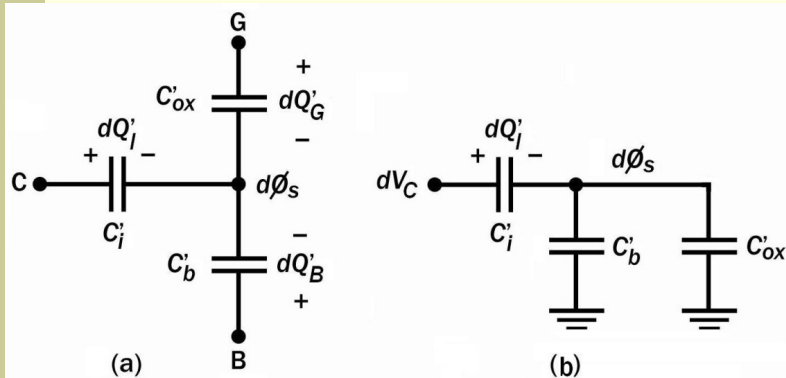

$$I_D = -\mu_n W Q'_I \frac{d\phi_s}{dy} + \mu_n W \phi_t \frac{dQ'_I}{dy}$$

$$dQ'_I = (C'_{ox} + C'_b) d\phi_s = n C'_{ox} d\phi_s$$

$n = n(V_G)$ is constant
along the channel

$$I_D = -\frac{\mu_n W}{n C'_{ox}} (Q'_I - \phi_t n C'_{ox}) \frac{dQ'_I}{dy}$$

Integrating along the channel yields


$$I_D = \frac{\mu_n W}{L} \left[\frac{Q'_{IS}{}^2 - Q'_{ID}{}^2}{2n C'_{ox}} - \phi_t (Q'_{IS} - Q'_{ID}) \right]$$

Forward and reverse currents

symmetry of the rectangular MOSFET

$$I_D = I_F - I_R = I(V_G, V_S) - I(V_G, V_D)$$
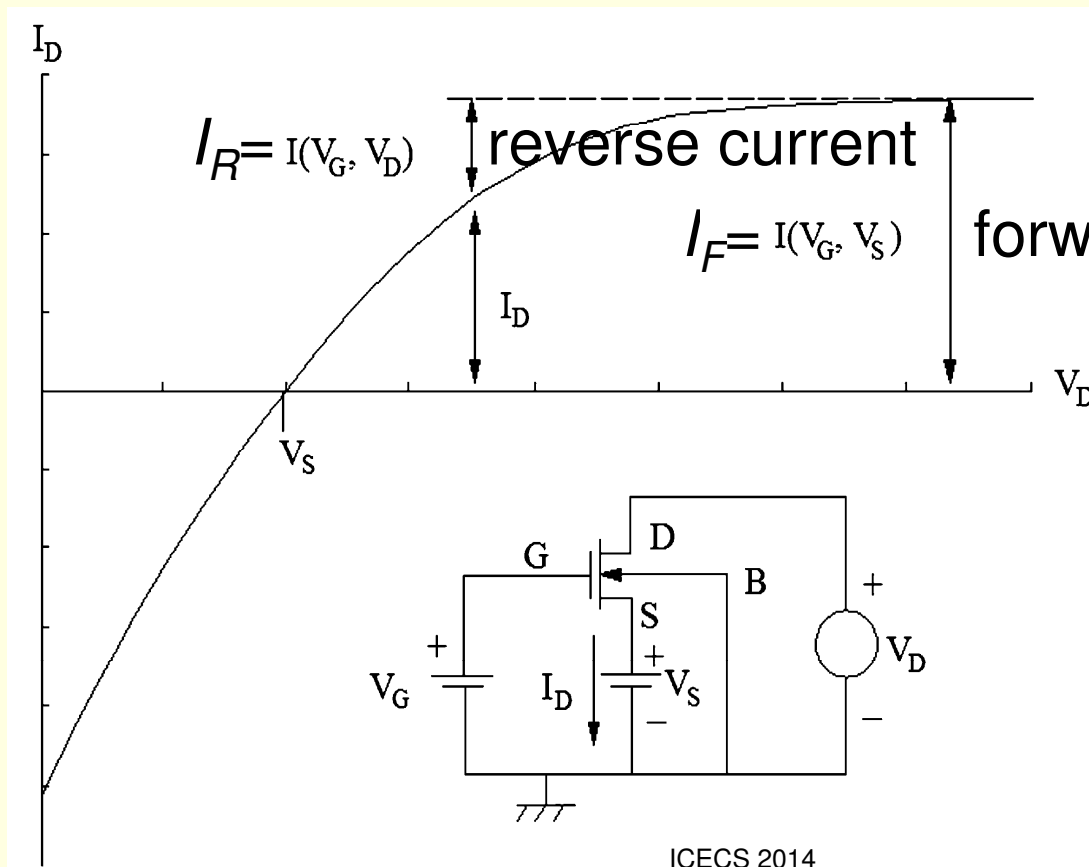
$$I_{F(R)} = \frac{W}{L} \mu_n \left[\frac{Q'_{IS(D)}{}^2}{2nC'_{ox}} - \phi_t Q'_{IS(D)} \right]$$



Normalization (areal) charge

$$I_D = -\frac{\mu_n W}{n C'_{ox}} (Q'_I - \phi_t n C'_{ox}) \frac{dQ'_I}{dy}$$

↑
↑

Drift
Diffusion

Normalization charge

Drift = Diffusion

$$Q'_I = -n C'_{ox} \phi_t \rightarrow$$

$$q'_{IS(D)} = Q'_{IS(D)} / (-n C'_{ox} \phi_t)$$

$$I_D = I_F - I_R = I_S [i_f - i_r]$$

Normalized unified charge control model

$$V_P - V_C = \phi_t (q'_I - 1 + \ln q'_I)$$

$$i_{f(r)} = I_{F(R)} / I_S = (1 + q'_{IS(D)})^2 - 1$$


$$I_S = \mu C'_{ox} n \frac{\phi_t^2}{2} \frac{W}{L} = I_{SQ} \frac{W}{L}$$

I_S and I_{SQ} are the normalization (specific) current and the “sheet” normalization current

Normalized charge-based MOSFET model



$$u_P - u_{S(D)} = \frac{V_P - V_{S(D)}}{\phi_t} = \sqrt{1 + i_{f(r)}} - 2 + \ln(\sqrt{1 + i_{f(r)}} - 1)$$

Inversion charge per unit area q'_I

 

The I-V relationship
  
$$V_P - V_S = \phi_t \left[\sqrt{1 + i_f} - 2 + \ln \left(\sqrt{1 + i_f} + 1 \right) \right]$$



Common-source characteristics

Weak inversion model




Weak inversion

$$i_{f(r)} < 1$$

$$\frac{V_G - V_{T0} - V_{S(D)}}{n} = \phi_t \left[\underbrace{\sqrt{1 + i_{f(r)}} - 2}_{-1} + \ln \left(\underbrace{\sqrt{1 + i_{f(r)}} - 1}_{i_{f(r)}/2} \right) \right]$$

$$I_D = I_0 e^{\left(\frac{V_G - V_{T0} - V_S}{n} \right) / \phi_t} \left[1 - e^{-V_{DS} / \phi_t} \right]$$
 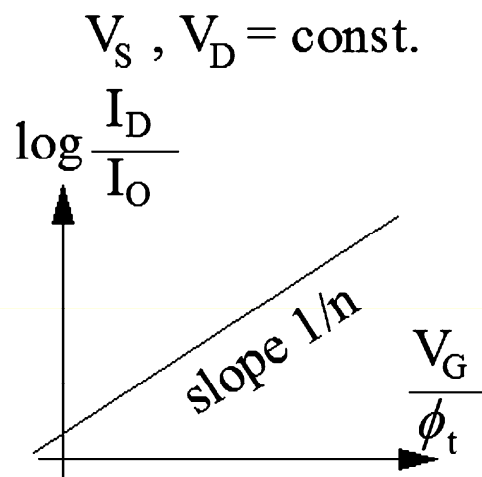 
$$I_0 = \mu_n \frac{W}{L} n C'_{ox} \phi_t^2 e^1 = 2 I_S e^1$$



Transconductances - 1


Transconductances $\Delta I_D = g_{mg} \Delta V_G - g_{ms} \Delta V_S + g_{md} \Delta V_D + g_{mb} \Delta V_B$

$$g_{mg} - g_{ms} + g_{md} + g_{mb} = 0 \quad g_{mg} = \frac{\partial I_D}{\partial \mathcal{N}_G}, g_{ms} = -\frac{\partial I_D}{\partial \mathcal{N}_S}, g_{md} = \frac{\partial I_D}{\partial \mathcal{N}_D}, g_{mb} = \frac{\partial I_D}{\partial \mathcal{N}_B}$$


Calculation of g_{ms}

$$g_{ms} = -\frac{\partial (I_F - I_R)}{\partial V_S} = -\frac{\partial I_F}{\partial V_S} = -\mu \frac{W}{L} Q'_{IS}$$

$$g_{md} = -\mu \frac{W}{L} Q'_{ID}$$

 
 
$$g_{mg} = I_S \frac{\partial (i_f - i_r)}{\partial V_G}$$



$$\begin{cases} \frac{\partial i_f}{\partial V_G} = -\frac{\partial i_f}{n \partial V_S} \\ \frac{\partial i_r}{\partial V_G} = -\frac{\partial i_r}{n \partial V_D} \end{cases}$$

$$g_{mg} = g_m = \frac{g_{ms} - g_{md}}{n}$$

$$g_m = \frac{g_{ms}}{n} \longrightarrow \text{in saturation}$$

Transconductances - 2

$$g_{ms(d)} = \frac{2I_S}{\phi_t} \left(\sqrt{1+i_{f(r)}} - 1 \right) = \frac{W}{L} \mu n C'_{ox} \phi_t \left(\sqrt{1+i_{f(r)}} - 1 \right)$$

$$g_m = \frac{g_{ms} - g_{md}}{n} \quad \frac{g_m}{I_D} = \frac{2}{n\phi_t \left(\sqrt{1+i_f} + \sqrt{1+i_r} \right)}$$


For $V_{DS}/\phi_t \ll 1$ we have $i_f \approx i_r$

In saturation

$$\frac{g_m}{I_D} \cong \frac{1}{n\phi_t \sqrt{1+i_f}}$$


$$\frac{g_m}{I_D} = \frac{2}{n\phi_t \left(\sqrt{1+i_f} + 1 \right)}$$

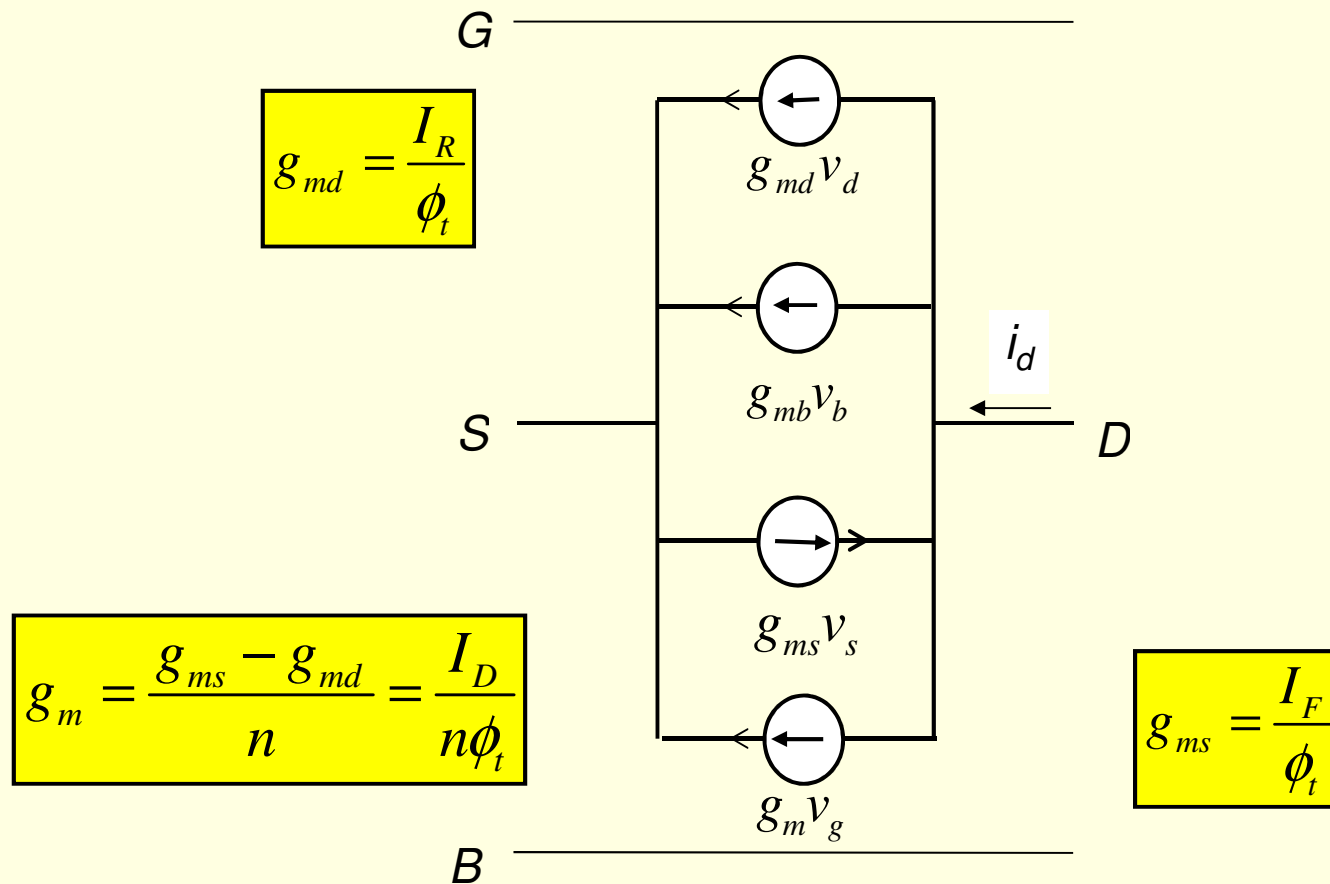MOSFET: low-frequency small-signal model in weak inversion



$$g_{ms} = g_m + g_{mb} + g_{md}$$

 Low-voltage operation of the common-source amplifier



$$|A_V| = \frac{g_m}{g_{md}} = \frac{g_{ms} - g_{md}}{ng_{md}} = \frac{1}{n} \left(\frac{g_{ms}}{g_{md}} - 1 \right)$$


$$\frac{g_{ms}}{g_{md}} = e^{\frac{V_{DS}}{\phi_t}}$$

$$|A_V| = \frac{1}{n} \left(e^{\frac{V_{DS}}{\phi_t}} - 1 \right)$$

or

$$V_{DS} = \phi_t \ln(1 + n|A_V|)$$

 Low-voltage operation of the (C)MOS inverter




$$V_{DS} = \phi_t \ln(1 + n |A_V|)$$

Minimum supply voltage for amplification $|A_V| = 1$
 'ideal' MOSFET $n = 1$

$$V_{DS} = V_{DD}$$


$$V_{DD\min} = (\ln 2)\phi_t$$

 

$$V_{DS} = V_{DD} / 2$$


$$V_{DD\min} = 2(\ln 2)\phi_t$$

 Low-voltage operation of the common-gate amplifier






$$A_{v, cg} = \frac{v_o}{v_i} = \frac{g_{ms}}{g_{md}} = e^{\frac{qV_{DS}}{kT}}$$

 The common-gate amplifier provides a voltage gain of greater than unity for $V_{DS} > 0$. → Very useful property for lowering the supply voltage limit for the operation of oscillators (later).



Common-gate Colpitts oscillator

Zero-VT MOSFETs

   

- $I_D \times V_{DS}$ ($V_S = V_B$) characteristics for a zero-VT transistor with $W/L = 2500\mu\text{m}/420\text{nm}$. For $V_{GS} = 0$ V and $V_{DS} = 25$ mV the values of the common-gate and common-source gains are 1.56 and 0.53, respectively.


ULTRA-LOW-VOLTAGE (ULV) IC DESIGN: DESIGNING FOR VDD BELOW kT/q

Chapter 2 Ultra-Low-Voltage (ULV) CMOS logic circuits

THE CMOS INVERTER

Static Analysis in weak inversion 1

$$I_{DN(P)} = I_{ON(P)} \cdot e^{\frac{V_{GB(BG)} - |V_{TN(P)}| - n_N \cdot V_{SB(BS)}}{n_{N(P)} \cdot \phi_t}} \cdot \left(1 - e^{-\frac{V_{DS(SD)}}{\phi_t}} \right)$$

 

- The strength or current capability of the transistor is given by

$$I_{N(P)} = I_{ON(P)} \cdot e^{\frac{-|V_{TN(P)}|}{n_{N(P)} \cdot \phi_t}}$$

- For the sake of simplicity let $n_N = n_P = n$. The static transfer function of the inverter is obtained from

$$I_{DN} = I_{DP}$$

$$I_{ON} \cdot e^{\frac{V_I - V_{TN}}{n \cdot \phi_t}} \cdot \left(1 - e^{-\frac{V_O}{\phi_t}} \right) = I_{OP} \cdot e^{\frac{V_{DD} - V_I - |V_{TP}|}{n \cdot \phi_t}} \cdot \left(1 - e^{-\frac{V_{DD} - V_O}{\phi_t}} \right)$$

THE CMOS INVERTER

Static Analysis in weak inversion 2

$$V_I = \frac{V_{DD}}{2} + \frac{V_{TN} - |V_{TP}|}{2} + \frac{n \cdot \phi_t}{2} \cdot \ln\left(\frac{I_{OP}}{I_{ON}}\right) + \frac{n \cdot \phi_t}{2} \cdot \ln\left(\frac{1 - e^{-\frac{V_{DD} - V_O}{\phi_t}}}{1 - e^{-\frac{V_O}{\phi_t}}}\right)$$


In the ideal case of NMOS and PMOS transistors with the same strength, i.e. $I_{ON} = I_{OP}$ and $V_{TN} = |V_{TP}|$, the VTC reduces to

$$V_I = \frac{V_{DD}}{2} + \frac{n \cdot \phi_t}{2} \cdot \ln\left(\frac{1 - e^{-\frac{V_{DD} - V_O}{\phi_t}}}{1 - e^{-\frac{V_O}{\phi_t}}}\right)$$

$$I_{SC} = \sqrt{I_{ON} \cdot I_{OP}} \cdot e^{\frac{V_{DD} - V_{TN} - |V_{TP}|}{2 \cdot n \cdot \phi_t}} \cdot \sqrt{\left(1 - e^{-\frac{V_O}{\phi_t}}\right) \cdot \left(1 - e^{-\frac{V_{DD} - V_O}{\phi_t}}\right)}$$


THE CMOS INVERTER

Static Analysis in weak inversion 3

 

- Inverter voltage and current transfer characteristics.

SCHMITT TRIGGER ANALYSIS

 


**Schmitt Trigger
Inverter**

- *2 internal nodes (V_x and V_y)*
- *Feedback transistors controlled by the output*
- *Hysteresis for $V_{DD} > 80mV$*
- *No hysteresis is desired for V_{DD} minimization*
- *For symmetric operation, corresponding NMOS and PMOS MOSFETs have the same current capability*

ST ANALYSIS – DC TRANSFER 1

MOSFET current in weak inversion:
 
$$I_{DN(P)} = I_{ON(P)} \cdot e^{\frac{V_{GB(BG)} - n_{N(P)} \cdot V_{SB(BS)}}{n_{N(P)} \cdot \phi_t}} \cdot \left(1 - e^{-\frac{V_{DS(SD)}}{\phi_t}} \right)$$



$$e^{\frac{V_Y}{\phi_t}} = \frac{I_0 \cdot e^{\frac{V_{DD}}{\phi_t}} + I_1 \cdot e^{\frac{V_O}{\phi_t}} + I_2 \cdot e^{\frac{V_I - V_O}{\phi_t}}}{I_0 + I_1 + I_2 \cdot e^{\frac{V_I - V_O}{\phi_t}}}$$

$$e^{\frac{V_I - V_X}{\phi_t}} - e^{\frac{V_I - V_O}{\phi_t}} = e^{\frac{V_Y - V_I}{\phi_t}} - e^{\frac{V_O - V_I}{\phi_t}}$$

$$e^{\frac{V_X}{\phi_t}} = \frac{I_0 + I_1 + I_2 \cdot e^{\frac{V_O - V_I}{\phi_t}}}{I_0 + I_1 \cdot e^{-\frac{V_O}{\phi_t}} + I_2 \cdot e^{\frac{V_O - V_I}{\phi_t}} \cdot e^{-\frac{V_{DD}}{\phi_t}}}$$


$$n_{N(P)} = 1$$

Solved for V_O

Shows Hysteresis

ST ANALYSIS – DC TRANSFER 2

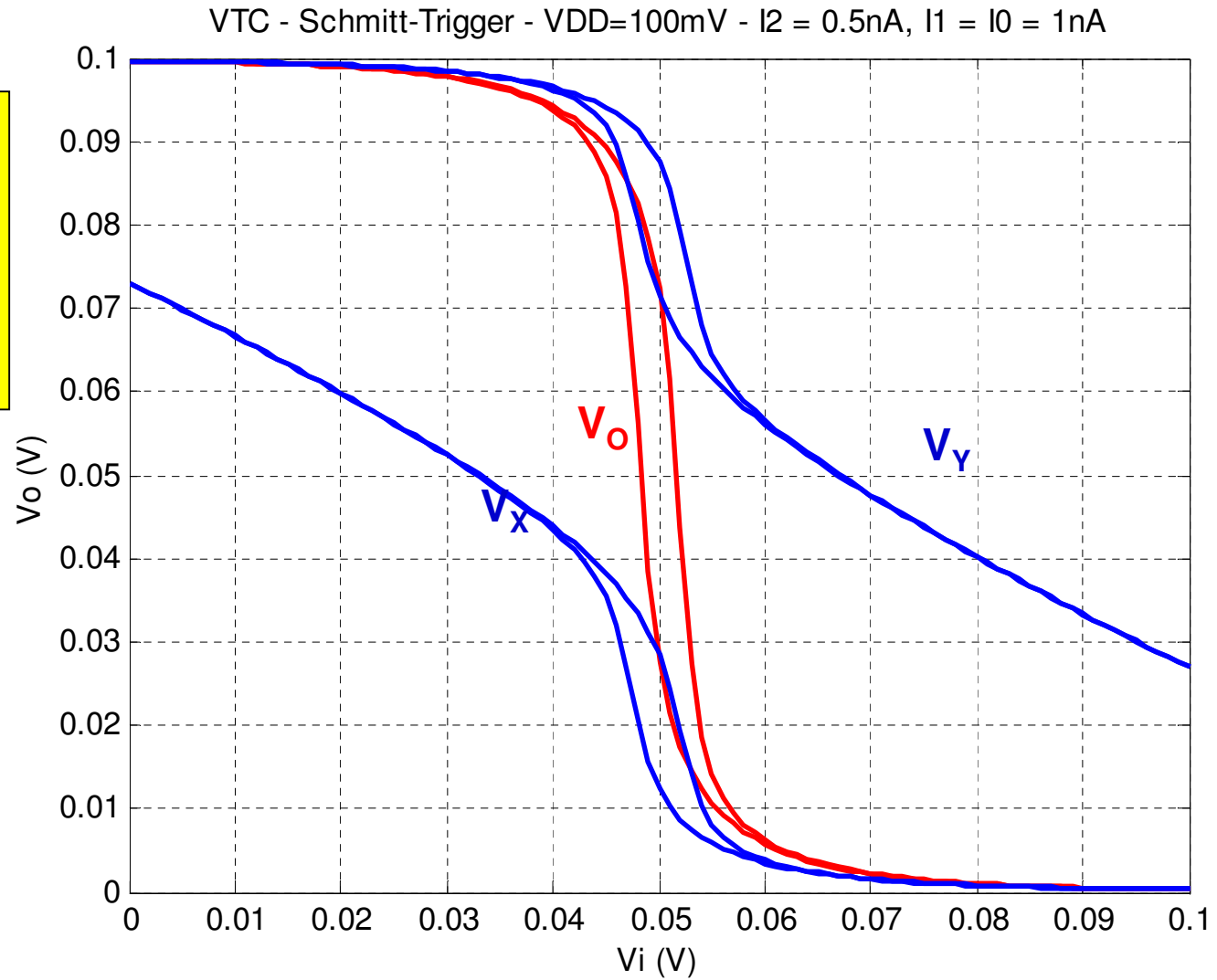
$$V_{DD} = 100mV$$
$$\frac{I_2}{I_0} = 0.5$$
$$\frac{I_1}{I_0} = 1$$



ST OPTIMIZATION 1

Series transistor: I_1/I_0

 Rearranging the AC gain equation for I_1/I_0



$$\left. \frac{v_o}{v_i} \right|_{V_O=V_I=\frac{V_{DD}}{2}} = -\frac{\frac{I_1}{I_0} A_1 + B_1}{\frac{I_1}{I_0} C_1 + D_1}$$

*Bilinear function
with negative pole*


$$\left. \frac{I_1}{I_0} \right|_{OPTIMUM} = 0$$

*Practical values of I_1/I_0 range from 0.01 to 0.1,
with only slight penalty in terms of the gain.*

ST OPTIMIZATION 2

Feedback transistors

 Rearranging the AC gain equation for I_2/I_0




$$\left. \frac{v_o}{v_i} \right|_{V_o=V_I=\frac{V_{DD}}{2}} = - \frac{\left(\frac{I_2}{I_0}\right)^2 A_2 + \left(\frac{I_2}{I_0}\right) B_2 + C_2}{\left(\frac{I_2}{I_0}\right)^2 D_2 + \left(\frac{I_2}{I_0}\right) E_2 + F_2}$$

$$\left. \frac{I_2}{I_0} \right|_{OPTIMUM} = \frac{\sqrt{1 + e^{\frac{V_{DD}}{2\phi_t}} - e^{-\frac{V_{DD}}{2\phi_t}} - 1}}{1 + e^{-\frac{V_{DD}}{2\phi_t}}}$$

ST x CMOS INVERTER 1



73 is the best number !

 

Schmitt Trigger inverter


Substituting the optimum values of I_1/I_0 and I_2/I_0 , the ST minimum operating voltage can be calculated:

$$V_{DD\min} = 2\phi_t \ln\left(\frac{1}{\sqrt{73}-8}\right) = 31.5\text{mV at } 300\text{K}$$

$$\left.\frac{I_1}{I_0}\right|_{\text{OPTIMUM}} = 0 \quad \left.\frac{I_2}{I_0}\right|_{\text{OPTIMUM}} = 0.333$$

ST structures are capable of operating at lower supply voltages than the standard static logic!!!!

ST x CMOS INVERTER 2


 


ULTRA-LOW-VOLTAGE (ULV) IC DESIGN: DESIGNING FOR VDD BELOW kT/q

Chapter 3 Ultra-Low-Voltage (ULV) rectifiers

MOTIVATION



Wirelessly powered sensors

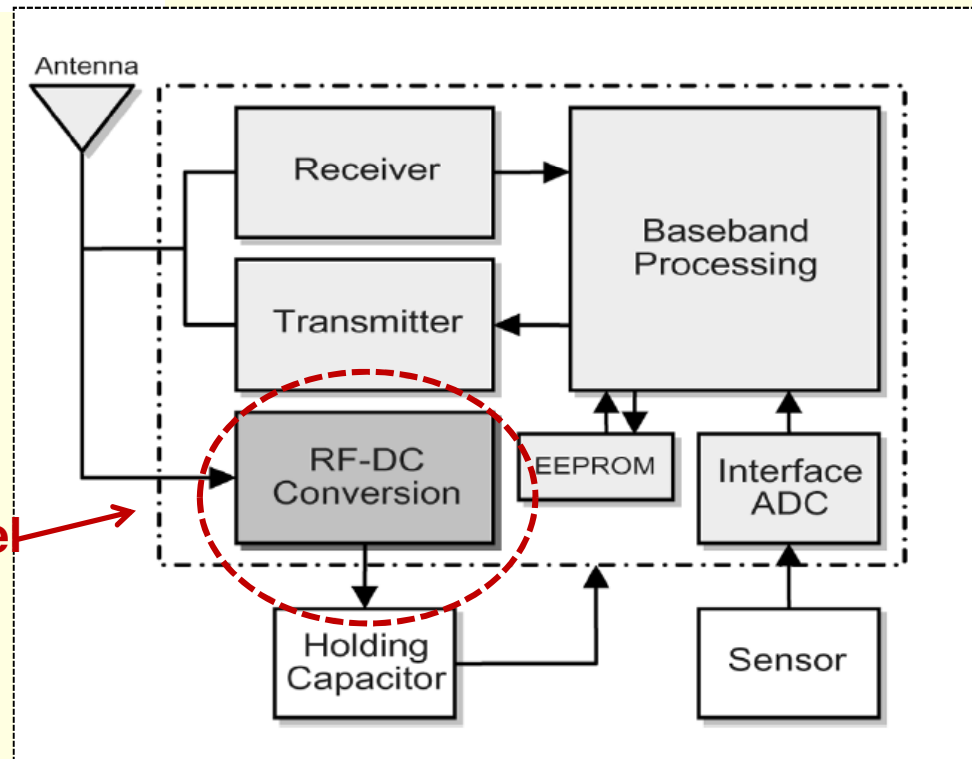 

Low power/voltage level

Ultra-low-voltage diode circuits

  Dickson analysis of voltage multipliers: constant threshold voltage diode model, but **it is not appropriate for low voltage operation**



$$V_L = V_p - V_{ON}$$

How to substitute the constant 'diode voltage drop' model?


Use the i-v characteristic of the diode and the load current

$$I_D = I_S \left[e^{\frac{V_D}{n\phi_t}} - 1 \right]$$


$$\phi_t = \frac{kT}{q}$$

$$n \sim 1 \text{ to } 1.5$$

 Voltage rectifier with pure capacitive load - 1



$$V_P \gg n\phi_t$$

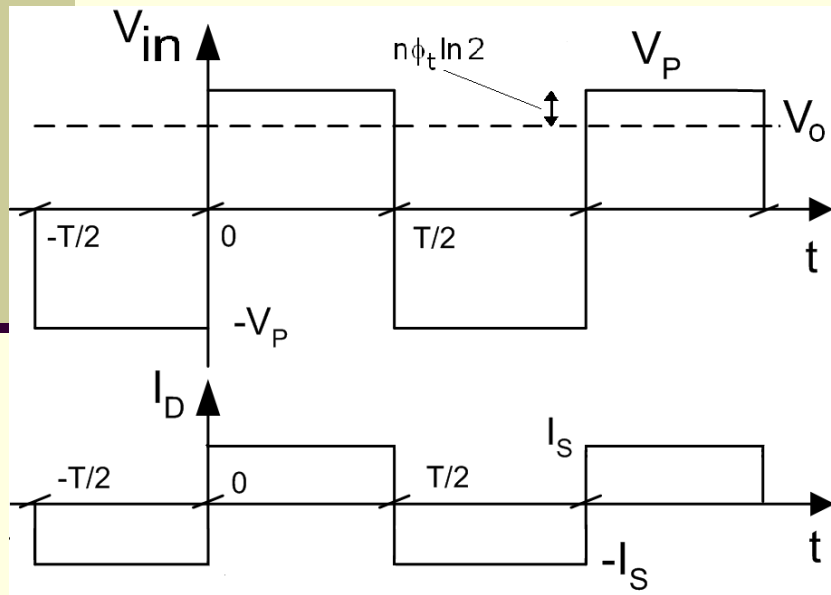

Steady-state analysis

$$\frac{1}{T} \int_{-T/2}^{T/2} I_D dt = 0 \quad I_D = I_S \left[e^{\frac{V_D}{n\phi_t}} - 1 \right]$$


$$\frac{I_S}{T} \left[\int_{-T/2}^0 \left(e^{\left(\frac{-V_P - V_o}{n\phi_t} \right)} - 1 \right) dt + \int_0^{T/2} \left(e^{\left(\frac{V_P - V_o}{n\phi_t} \right)} - 1 \right) dt \right] = 0$$

**Assumption: very low ripple
(high C)**

$\rightarrow V_o \cong \text{constant}$

$$\frac{V_o}{n\phi_t} = \ln \left[\frac{e^{V_P/n\phi_t} + e^{-V_P/n\phi_t}}{2} \right] = \ln \left[\cosh(V_P/n\phi_t) \right]$$

 Voltage rectifier with pure capacitive load - 2



$$\frac{V_o}{n\phi_t} = \ln \left[\cosh \left(\frac{V_P}{n\phi_t} \right) \right]$$


Power Detector

$$V_P \ll n\phi_t \rightarrow \frac{V_o}{n\phi_t} \cong \frac{1}{2} \left(\frac{V_P}{n\phi_t} \right)^2$$


Peak Detector Diode "ON" voltage drop

$$V_P \gg n\phi_t \rightarrow V_L \cong V_P - \underbrace{n\phi_t \ln 2}_{\text{Diode "ON" voltage drop}}$$


Input ↗

 

Application: microwave power detection

 

■ Basic detector circuit


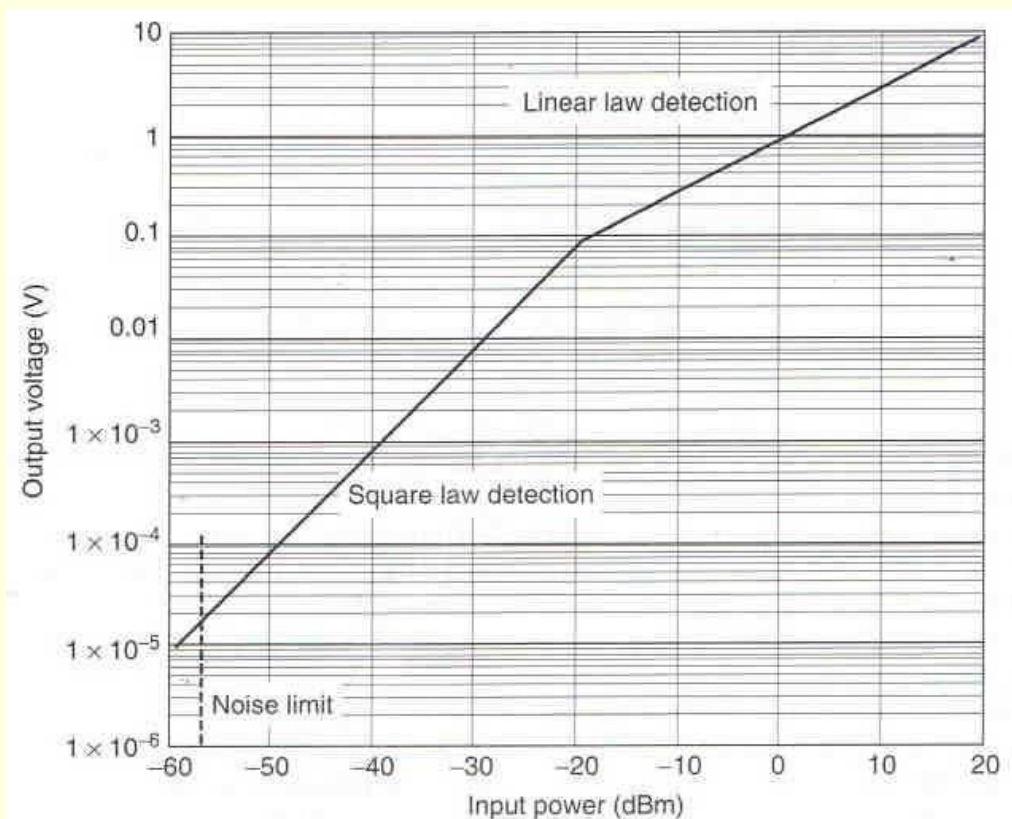


R. G. Meyer, "Low-power monolithic RF peak detector analysis," IEEE J. Solid-State Circuits, vol. 30, no. 1, pp. 65–67, Jan. 1995.

Wetenkamp, IEEE MTT-S Int. Microwave Symp. Dig., 1983

Voltage rectifier with DC load - 1

Output voltage ripple

 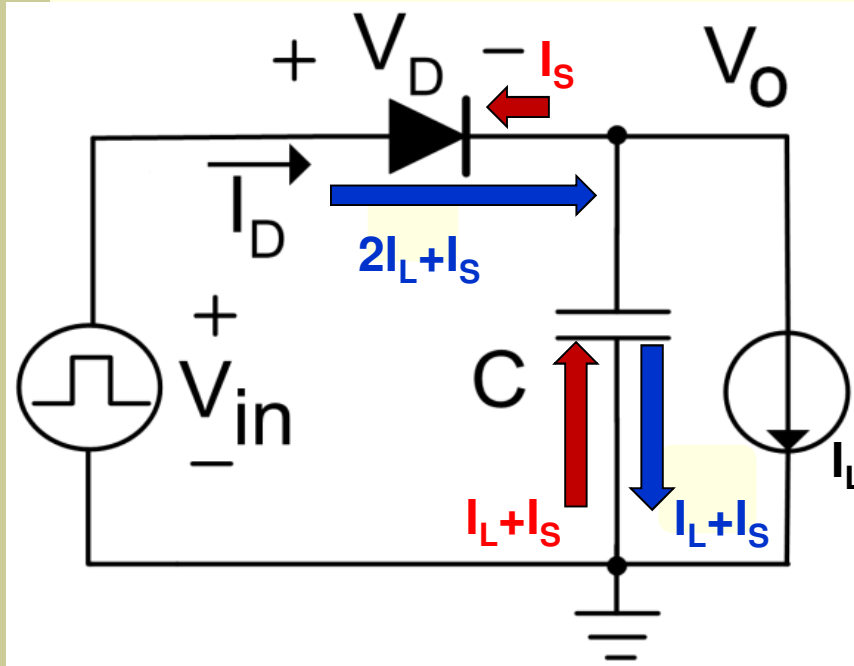


The discharge rate of the capacitor


$$I_C = \frac{dQ_C}{dt} = C \frac{dV_C}{dt} \cong I_L + I_S$$

$$\int_{-T/2}^0 dV_C = \Delta V \cong \frac{I_L + I_S}{C} \frac{T}{2} = \frac{I_L + I_S}{2fC}$$

Voltage rectifier with DC load - 2

 

Waveforms for $V_P \gg n\phi_t$

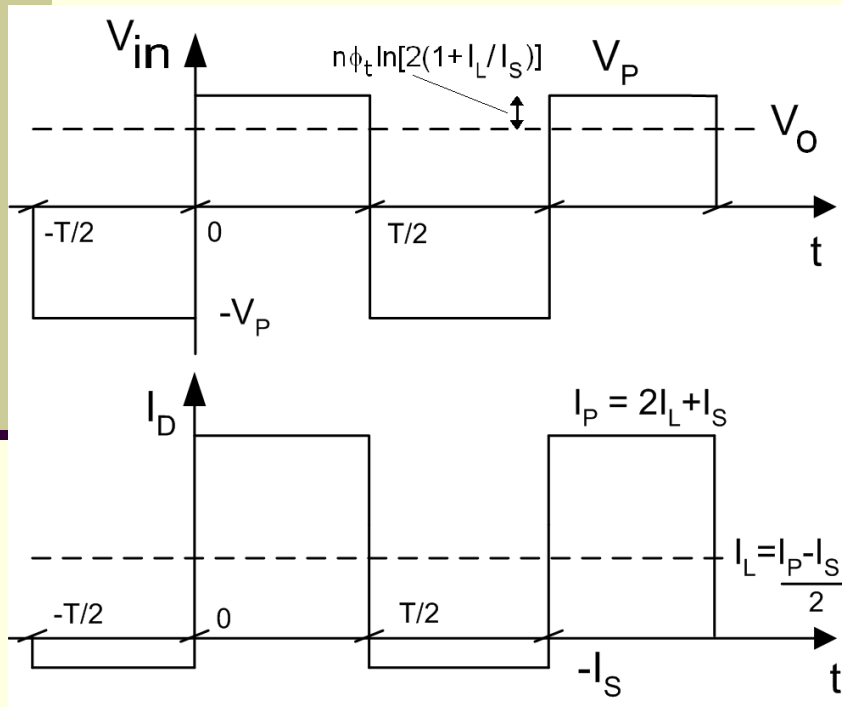


Steady-state analysis

$$\frac{I_S}{T} \left[\int_{-T/2}^0 \left(e^{\left(\frac{-V_P - V_o}{n\phi_t} \right)} - 1 \right) dt + \int_0^{T/2} \left(e^{\left(\frac{V_P - V_o}{n\phi_t} \right)} - 1 \right) dt \right] = I_L$$

Assumption: very low ripple $\rightarrow V_o \cong$ constant

$$\frac{V_o}{n\phi_t} = \ln \left[\frac{\cosh(V_P / n\phi_t)}{1 + I_L / I_S} \right]$$

Voltage rectifier with DC load - 3

 



$$V_P > n\phi_t \rightarrow$$

\rightarrow


$$V_o \cong V_P - n\phi_t \ln \left(\frac{I_P + I_0}{I_0} \right)$$

Diode "ON"
voltage drop

Waveforms for $V_P \gg n\phi_t$

  

The voltage doubler

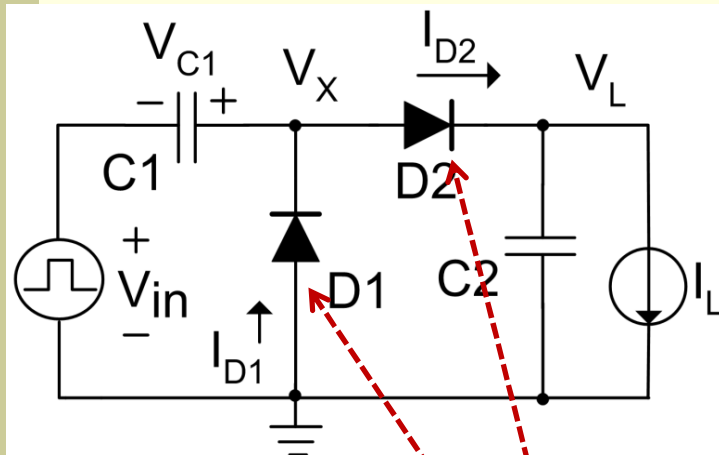

$$PCE = \frac{P_{load}}{P_{in}} = \frac{V_L I_L}{P_{load} + P_{loss}}$$

PCE: Power Conversion Efficiency

$$PCE = \frac{P_{out}}{P_{out} + P_{loss}} \cong \frac{1 - \frac{n\phi_t}{V_P} \ln [2(1 + I_L / I_S)]}{(1 + I_S / I_L)}$$


 


Fig. 3. Power conversion efficiency and load voltage of the voltage doubler versus normalized load current for values of $V_P/n\phi_t$ equal to 1.5, 3, 6, and 12.

The voltage multiplier

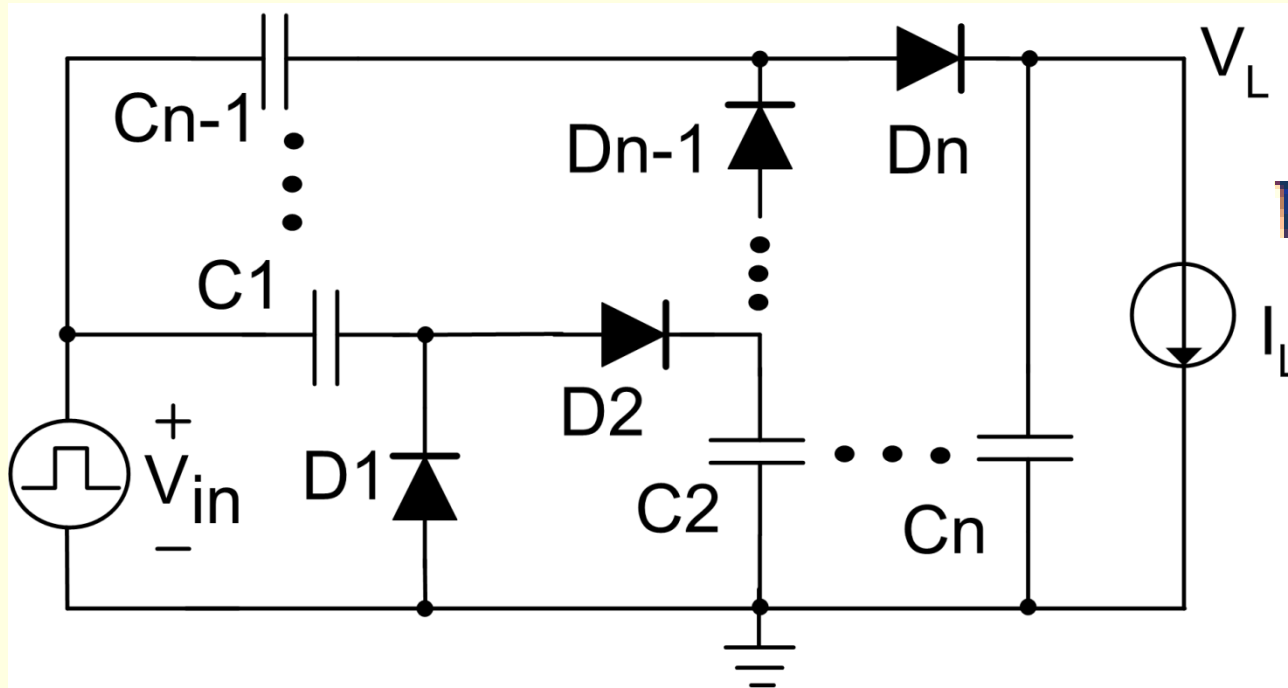



$$V_L = nV_{CI}$$

N-stage voltage multiplier

Applications:




- Generation of voltages higher than the supply voltage, for EEPROMs, flash memories
- Energy harvesting for RFID tag chips, for example

Diode connected MOSFET

  


Low-voltage I-V characteristic of a diode-connected zero-VT transistor.

   AC/DC converter in 130 nm CMOS technology




24-stage rectifier

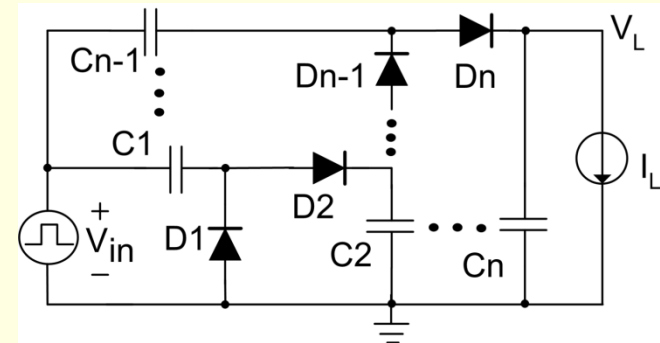

ULTRA-LOW-VOLTAGE (ULV) IC DESIGN: DESIGNING FOR VDD BELOW kT/q

Chapter 4 Ultra-Low-Voltage (ULV) oscillators

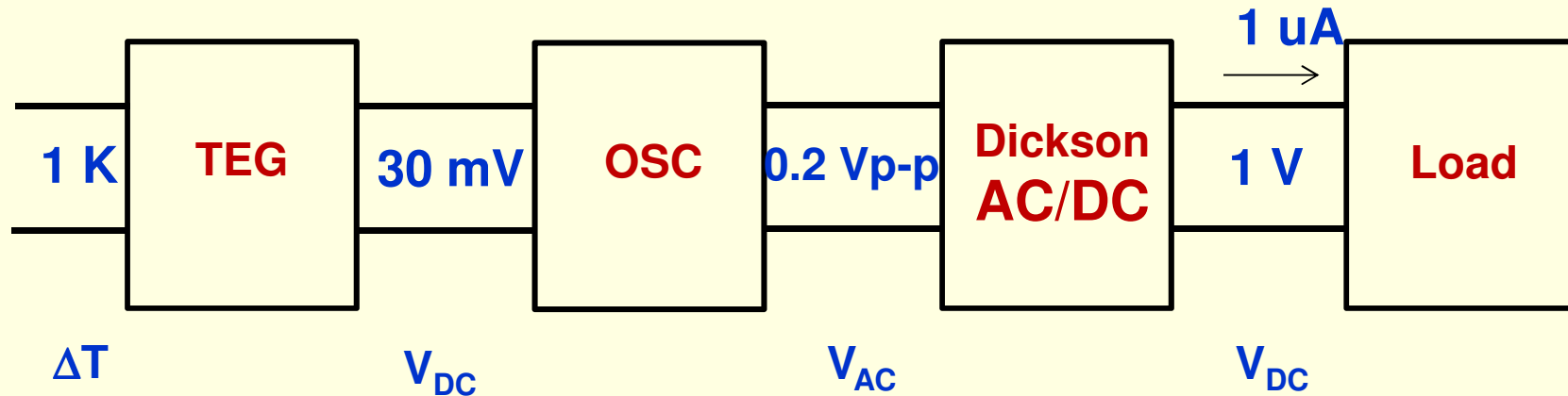
An important application of ULV oscillators




TEG – thermoelectric generator

OSC – oscillator

Inductive ring oscillator - 1

 

Cross-coupled LC oscillator

 

$$\frac{V_{out}}{V_{in}} = - \frac{g_m}{g_{md} + G_P} \frac{1}{1 - j \tan \phi}$$

$$\tan \phi = \frac{1 - LC\omega^2}{\omega L(g_{md} + G_P)}$$

Criterion for oscillation (Barkhausen)


$$\phi = 0 \quad \& \quad V_{out}/V_{in} = -1$$

$$\omega^2 LC = 1$$

$$\frac{g_m}{g_{md} + G_P} = 1$$

What's the minimum V_{DD} for oscillation?

Inductive ring oscillator - 2

 

Cross-coupled LC oscillator

Oscillation frequency $\omega^2 LC = 1$

Voltage gain $\frac{g_m}{g_{md} + G_P} = 1$

What's the minimum V_{DD} for oscillation?

Recall that $g_m = \frac{g_{ms} - g_{md}}{n}$

Voltage gain=1 \Rightarrow (i) $\frac{g_{ms}}{g_{md}} = 1 + n \left(1 + \frac{G_P}{g_{md}} \right)$

In weak inversion \Rightarrow (ii) $\frac{g_{ms}}{g_{md}} = e^{V_{DS}/\phi_t} = e^{V_{DD}/\phi_t}$ since $V_G = V_D = V_{DD}$

$$V_{DD,\min} = \phi_t \ln \left[1 + n \left(1 + \frac{G_P}{g_{md}} \right) \right] = \phi_t \ln [1 + n] \quad \text{for } \frac{G_P}{g_{md}} \ll 1$$


Similar to the result (/2) of the CMOS inverter

Inductive ring oscillator - 3


7-stage ring oscillator



 Zero-VT
 $W/L = 150 \mu\text{m} / 0.48 \mu\text{m}$




$L_{nom} = 100 \text{ nH}$

 

	Calculated	Sch. Sim.	Poslayout	Exp.
VDD,min	32.6 mV	37 mV	40 mV	53 mV
frequency	1.07 GHz	730 MHz	560 MHz	560 MHz

Inductive ring oscillator - 4

 



Questions:

1. How to reduce $V_{DD,min}$?
2. How to increase the V_{DD} -limited voltage swing?

Introduce voltage gain from drain to gate

Change topology, e. g., take advantage of CG gain




Enhanced swing IRO (ESRO)

 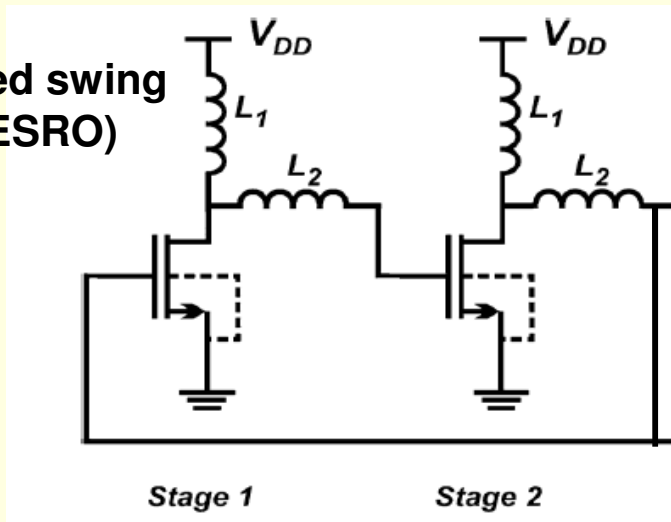

Enhanced swing Colpitts oscillator (ESCO) *

* T. W. Brown et al, *IEEE JSSC*, Aug. 2011.




ESCO: small-signal model - 1

   

$$v_s \cong \frac{v_d}{1 + \frac{C_2}{C_1}} \rightarrow g_{ms}v_s - g_{md}v_d \cong g'_m v_s$$

$$g'_m = g_{ms} - \left(1 + \frac{C_2}{C_1}\right)g_{md}$$


ESCO: small-signal model - 2

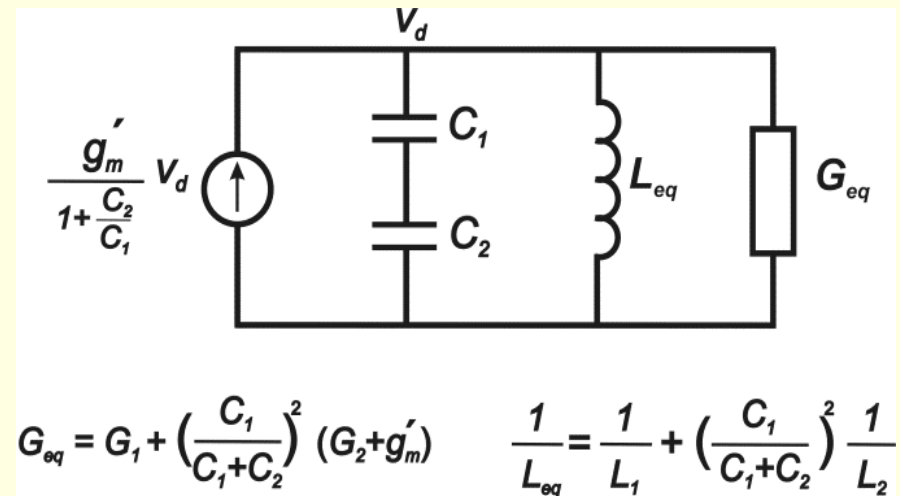 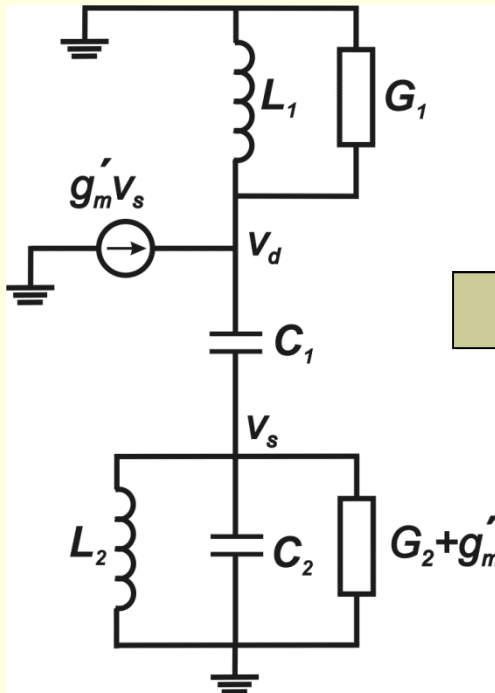


Second-order small-signal model of the ES Colpitts oscillator.

ESCO: start-up condition
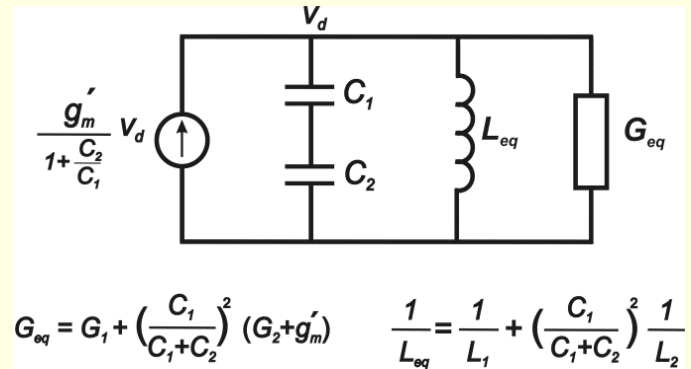
$$g_{ms} > \left(1 + \frac{C_2}{C_1}\right) g_{md} + \frac{C_1}{C_2} G_2 + \left(2 + \frac{C_1}{C_2} + \frac{C_2}{C_1}\right) G_1$$




 Optimum value of capacitors to minimize g_{ms} (for the conventional Colpitts $g_{md} = G_2 = 0$!)




$$\frac{C_2}{C_1} = \sqrt{\frac{G_1 + G_2}{g_{md} + G_1}}$$

 For ideal inductors (and capacitors) $G_1 = G_2 = 0$





 
$$g_{ms} > \left(1 + \frac{C_2}{C_1}\right) g_{md}$$



$$V_{DD\lim} = \frac{kT}{q} \ln\left(1 + \frac{C_2}{C_1}\right)$$


Colpitts oscillator: first prototype

Powered by a thermoelectric generator

 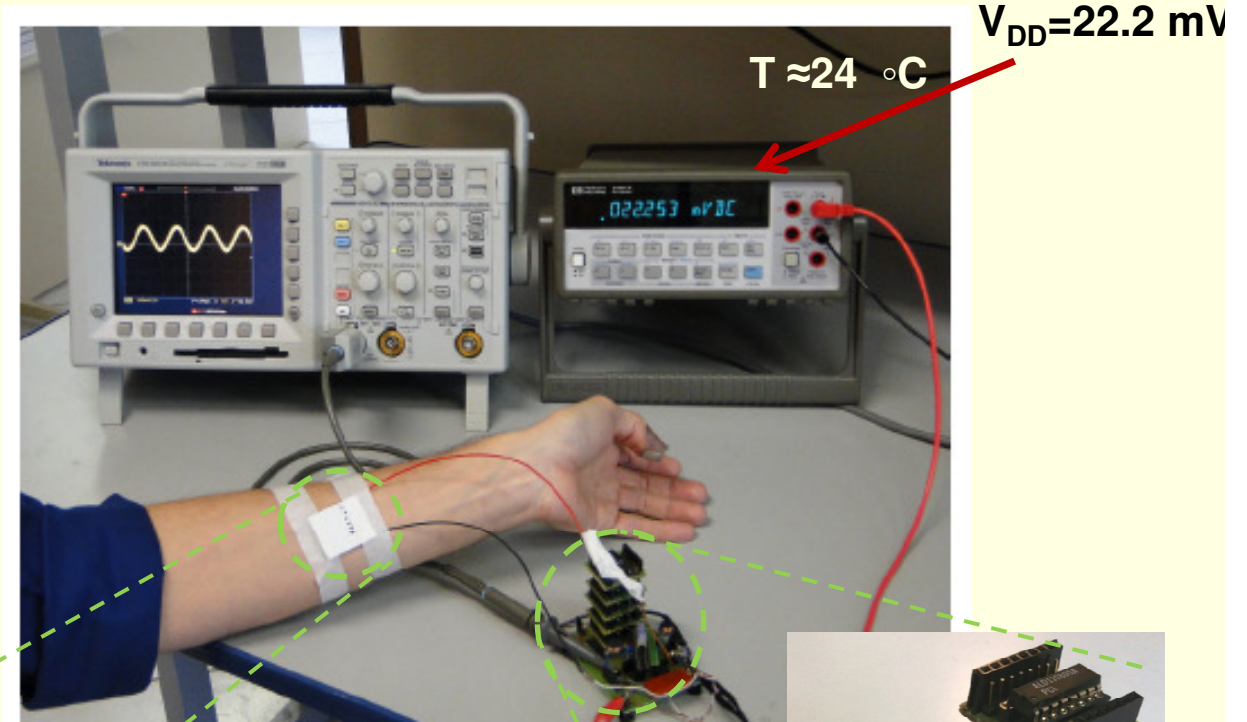 

thermoelectric generator

 24 // NMOS
Zero-VT (ALD 1108)
VT=59 mV, IS=11.2 uA




Colpitts oscillator: second prototype

$V_{DD} < 20 \text{ mV}$


Zero- V_T
IBM 130 nm

L2

 


L1

C1

 


$V_{pp} \approx 440 \text{ mV}$

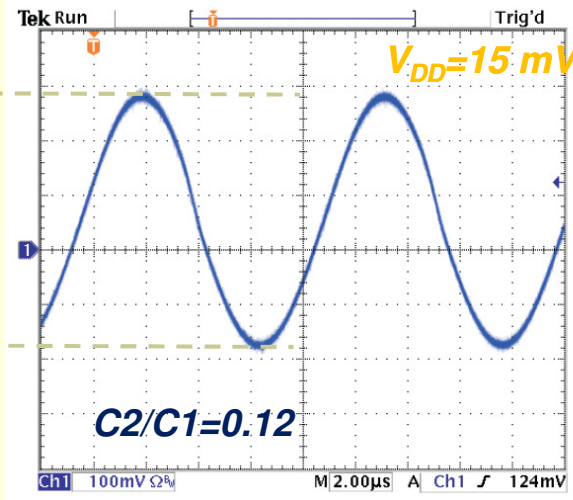

$f_{osc} \approx 110 \text{ kHz}$
 $V_{DD} = 15 \text{ mV}$


Second prototype: experimental results

$$V_{DD,min} \times C2/C1$$

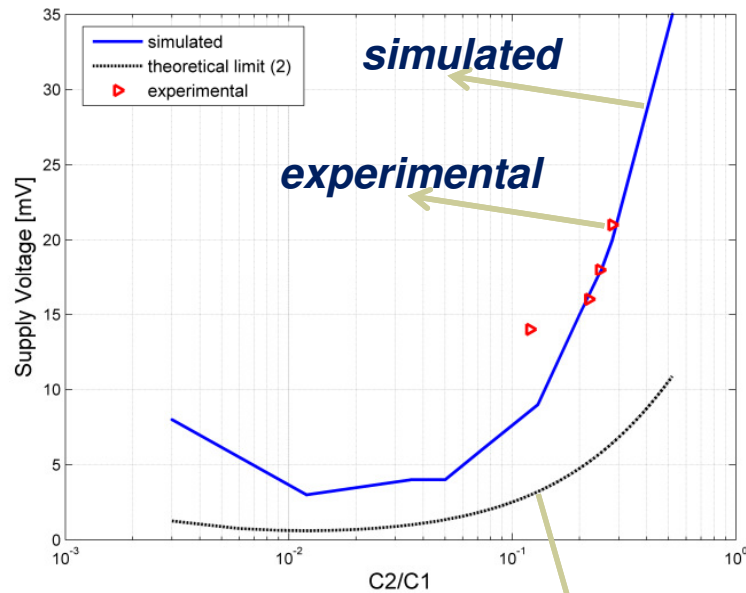

$f_{osc} \approx 110 \text{ kHz}$


weak inversion

 



$$V_{PP} \times V_{DD}$$

calculated

$$A_{d,max} = \frac{V_{DD}}{1 - 1/a}$$


 


ESCO designed for operation at 800 MHz


 
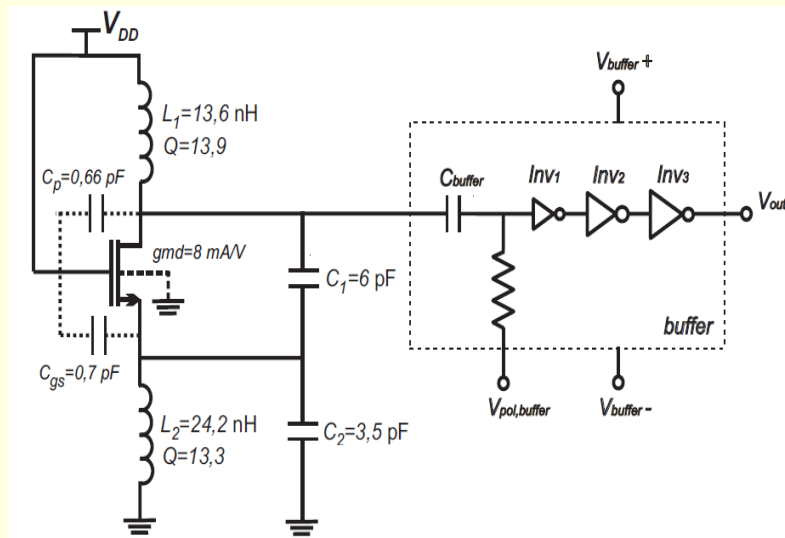


- Micrograph of the ESCO built in 130 nm technology

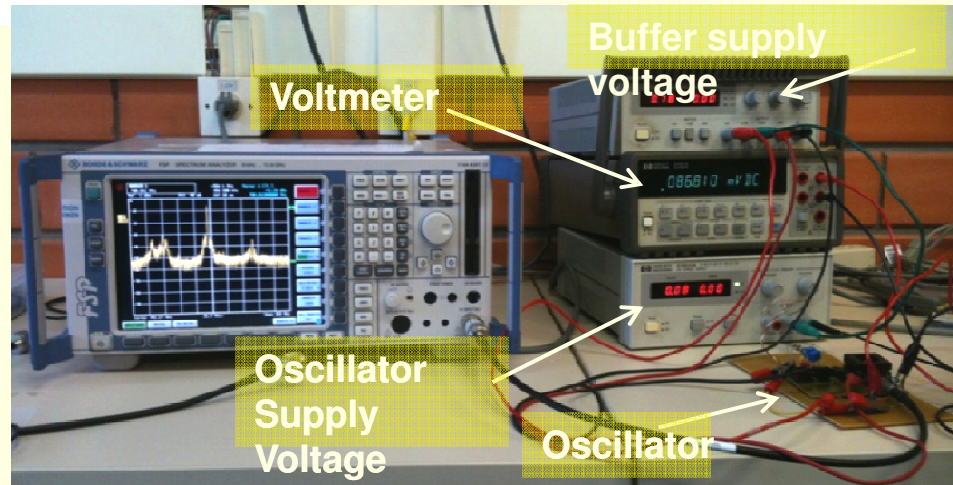 Spectral diagram of the ESCO ($V_{DD} = 86 \text{ mV}$)



Enhanced swing IRO (ESRO)-1

   

Enhanced swing IRO (ESRO)-2

 
 


Fig. 12. Simulated (dotted line) and experimental (solid line) peak-to-peak gate voltage versus supply voltage of the ES inductive-load ring oscillator.

 


Fig. 13. Picture showing the discrete prototype of the enhanced swing inductive-load oscillator and test equipment.

TABLE I
EXPERIMENTAL RESULTS FOR THE OSCILLATION FREQUENCY AND MINIMUM
SUPPLY VOLTAGE OF THE OSCILLATOR TOPOLOGIES

Topology	Theoretical $V_{dd} \text{ (min) }^*$	IC prototype 130nm CMOS		Discrete prototype	
		$V_{dd} \text{ (min)}$	f_{osc}	$V_{dd} \text{ (min)}$	f_{osc}
ILRO	$\phi_t \ln(1+n)$	53 mV	550 MHz	50 mV	11 MHz
ESILRO	$\phi_t \ln\left(1+n\frac{L_1}{L_1+L_2}\right)$	30 mV ⁺	400 MHz	3.5 mV	1.1 MHz
ESCO	$\phi_t \ln\left(1+\frac{C_2/C_1}{1+L_1/L_2}\right)$	86 mV	700 MHz	15 mV	108 kHz

* For lossless passive devices and operation of MOSFETs in weak inversion

+ Post-layout simulation

ILRO, ESILRO, and ESCO refer to inductive-load ring, enhanced swing inductive-load ring, and enhanced swing Colpitts oscillators, respectively.

Values of components:

ILRO – IC prototype – $L = 100 \text{ nH}$, $Q = 8$.

ILRO – discrete prototype – $L = 4.6 \text{ uH}$, $Q = 50$.


ESILRO – IC prototype – $L_1 = 20 \text{ nH}$, $Q_1 = 9$; $L_2 = 80 \text{ nH}$, $Q_2 = 8$.

ESILRO – discrete prototype – $L_1 = 4.6 \text{ uH}$, $Q_1 = 55$, $L_2 = 1.2 \text{ mH}$, $Q_2 = 60$.

ESCO – IC prototype – $L_1 = 13.6 \text{ nH}$, $Q_1 = 13.9$, $L_2 = 24.2 \text{ nH}$, $Q_2 = 13.3$, $C_1 = 6 \text{ pF}$, $C_2 = 3.5 \text{ pF}$.

ESCO – discrete prototype – $L_1 = L_2 = 9.8 \text{ mH}$, $Q_1 = Q_2 = 80$, $C_1 = 1.54 \text{ nF}$, $C_2 = 0.44 \text{ nF}$.

Step-up converter-1

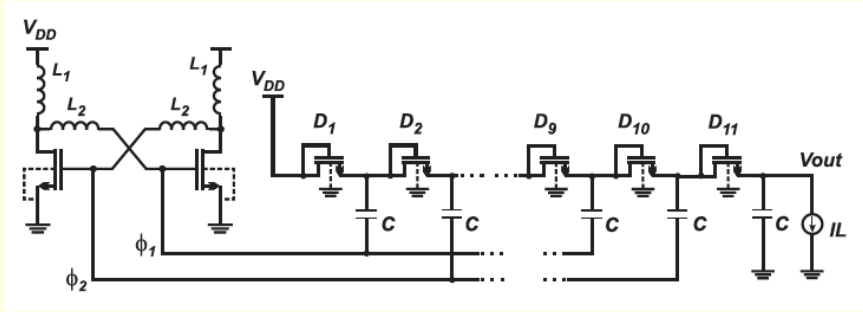

11-stage Dickson charge pump

Zero-VT transistor as a diode

$$W/L = 4.2\mu\text{m}/0.42\mu\text{m}$$

$$V_T = 76.5\text{ mV}$$

$$I_{\text{sat}} = 500\text{ nA}$$

2-stage ESRO

Zero-VT transistor


$$W/L = 500\mu\text{m}/0.42\mu\text{m}$$

$$V_T = 63\text{ mV}$$

Integrated inductors

$$L_1 = 18.8\text{ nH}, L_2 = 66\text{ nH}$$

$$Q \approx 8$$

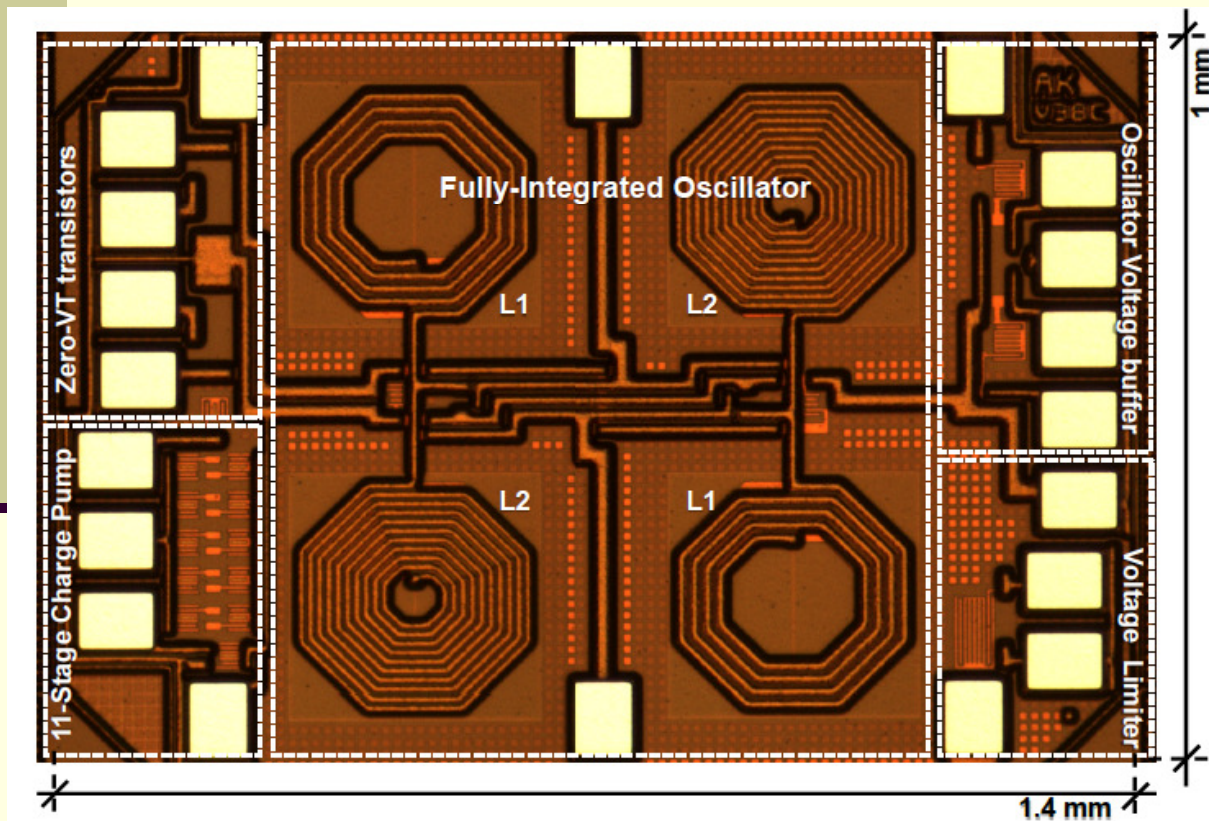


IBM 0.13 μm technology



Step-up converter-2

Experimental results

Vout

 

Pout

  

Start-up

$$V_{DD,min} = 73 \text{ mV}$$

$$\text{at } V_{out} = 1 \text{ V}$$

$$I_L = 1 \text{ uA}$$

$$V_{DD} = 86 \text{ mV}$$

References

- E. Vittoz, “Weak inversion for ultimate low-power logic”, in *Low-Power Electronics Design*, CRC Press, 2005.
- Márcio Cherem Schneider and Carlos Galup-Montoro, *CMOS Analog Design Using All-Region MOSFET Modeling*, Cambridge University Press, 2010.
- A. J. Cardoso, L. G. de Carli, C. Galup-Montoro, and M. C. Schneider, "Analysis of the rectifier circuit valid down to its low-voltage limit" , *IEEE Transactions on Circuits and Systems I: Regular Papers*, Jan. 2012.
- Y. Ramadass, “Energy harvesters and energy processing circuits,” ISSCC, San Francisco, Feb. 2013.
- M. B. Machado, M. C. Schneider, and C. Galup-Montoro , “On the minimum supply voltage for MOSFET oscillators”, *IEEE Transactions on Circuits and Systems I: Regular Papers*, Feb 2014.
- L. A. P. Malek et al., Optimized Design of the CMOS Schmitt Trigger for Ultra Low Voltage Operation, *Iberchip*, Santiago de Chile, 2014.
- M. B. Machado, M. C. Schneider, M. Sawan and C. Galup-Montoro, “Fully-Integrated 86 mV – 1V Step-up Converter for Energy Harvesting Applications”, *SBCCI*, Aracaju, Brazil, 2014