

Ultra-low-voltage CMOS circuit design

Carlos Galup-Montoro

Federal University of Santa Catarina, Florianópolis, SC, Brazil



<https://www.lci.ufsc.br/>

Outline

- **1. Introduction**
- **2. Subthreshold MOSFET model**
- **3. Ultra-low-voltage (ULV) CMOS digital circuits**
- **4. ULV LC tank oscillators**
- **5. ULV rectifiers and voltage multipliers**

Motivations for low voltage

1. Scaling

 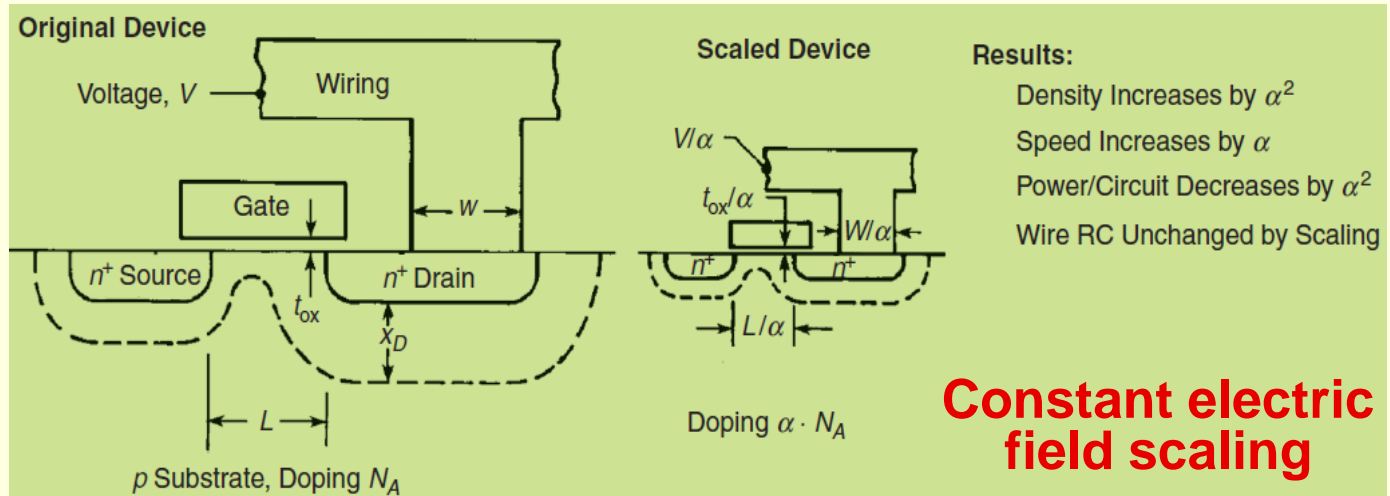

R. H. Dennard et al.
IEDM 72 & IEEE JSSC,
Oct. 1974


Motivations for low voltage

2. Power dissipation


Switching power

$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2$$

 Short-circuit power :
due to non-zero rise/fall times



Leakage power $\propto V_{DD}$

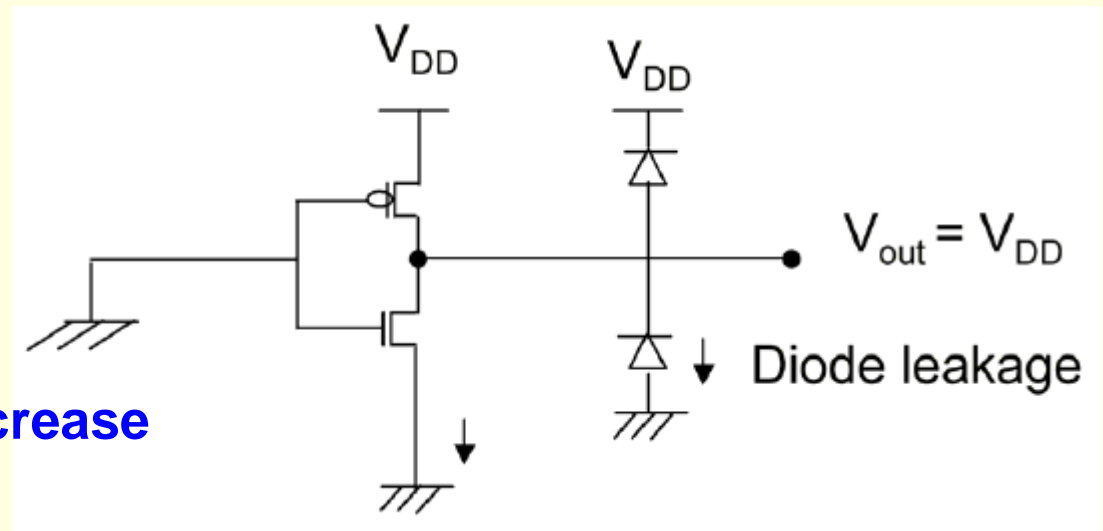

Most effective way to decrease
power is to lower V_{DD}

Sub-threshold current


Motivations for low voltage

3. Low supply voltages


Thermoelectric generator

$$V_{o(\text{body-environment})} \approx$$

30 - 50 mV

 

Photovoltaic cell

 


$$V_{o(\text{dark room})} \approx$$

100 - 200 mV

Energy provided by trees

$$V_o \approx \mathbf{20-200\ mV}$$


pH difference

 

* Love et al, "Source of sustained voltage difference between the xylem of a potted ficus benjamina tree and its soil", 2008.

The trend toward low supply voltages

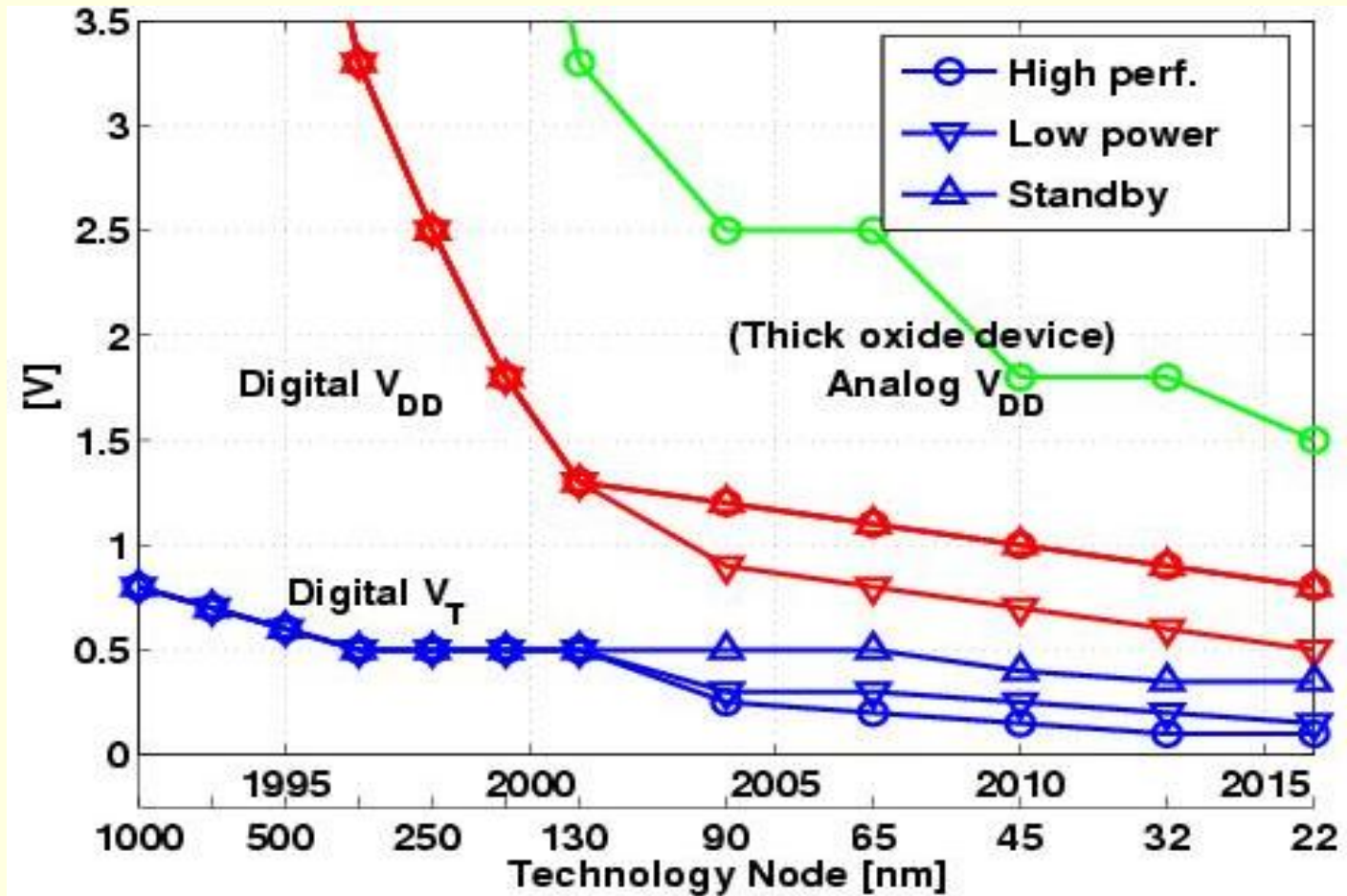- Q1-Is there a lower bound for the supply voltage?
- Q2-What are the best technologies for ULV circuits?



Voltage scaling is slowing / stopping

<http://www.cisl.columbia.edu/grads/tuku/research/>

CMOS supply voltages

- **Ultra low voltage ($V_{DD} \sim 100 \text{ mV @ } 300 \text{ K}$)**
3-parameter MOSFET model (long-channel model)
- **Low voltage**
4-parameter MOSFET model (long-channel model + DIBL)
- **Standard voltage ($V_{DD} \sim 1 \text{ V @ } 300 \text{ K}$)**
5-parameter MOSFET model (long-channel model + DIBL+ saturation velocity)



References

- J. M. Rabaey, “The power wall: are we scaling it or is it just getting higher?,” EPUSP, São Paulo, Nov. 2012.
- Y. Ramadass, “Energy harvesters and energy processing circuits,” ISSCC, San Francisco, Feb. 2013.

Outline

- 1. Introduction
- 2. **Subthreshold MOSFET model**
- 3. **Ultra-low-voltage (ULV) CMOS digital circuits**
- 4. **ULV LC tank oscillators**
- 5. **ULV rectifiers and voltage multipliers**

NTV Pentium® Processor

 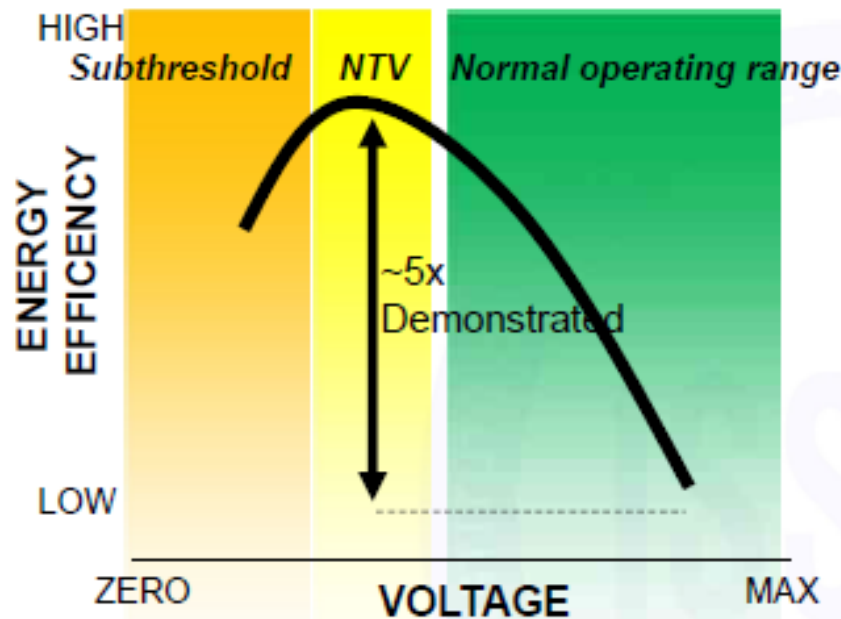



Ultra-low Power	Energy Efficient	High Performance
280 mV	0.45 V	1.2 V
3 MHz	60 MHz	915 MHz
2 mW	10 mW	737 mW
1500 Mips/W	5830 Mips/W	1240 Mips/W

Technology	32nm High-K Metal Gate
Interconnect	1 Poly, 9 Metal (Cu)
Transistors	Core:6M
Core Area	2mm ²
Package	951 Pins FCBGA11

Wide Dynamic Range

S. Jain, S. Khare et. al. "A 280mV-to-1.2V Wide-Operating-Range IA-32 Processor in 32nm CMOS," ISSCC 2012

MOS transistor

  

Inversion level

WI and SI (and the all-region) currents can be written as

$$I_D = \frac{W}{L} [f(V_{GB}, V_{SB}) - f(V_{GB}, V_{DB})]$$

Denoting $\frac{f(V_{GB}, V_{S(D)B})}{I_{SH}} = i_{f(r)}$

where I_{SH} is a (constant) normalization current $I_{SH} = \mu C_{ox} n \phi_t^2 / 2$

μ : carrier mobility

C_{ox} : oxide capacitance unit area

n : slope factor (= 1.05 - 1.3)

$$\phi_t = \frac{kT}{q} (= 26 \text{ mV @ 300K})$$

$i_{f(r)}$ is the forward (reverse) inversion level

$$I_D = \frac{W}{L} I_{SH} [i_f - i_r]$$


In saturation, $I_D \sim \text{constant}$ and $i_r \ll i_f$

The 4-parameter model

$$\frac{V_P - V_{S(D)B}}{\phi_t} = \sqrt{1 + i_{f(r)}} - 2 + \ln \left(\sqrt{1 + i_{f(r)}} - 1 \right)$$

$$I_D = I_S (i_f - i_r) = I_{SH} \frac{W}{L} (i_f - i_r)$$
 
$$V_P = \frac{V_{GB} - V_{T0} + \sigma V_{DB} + \sigma V_{SB}}{n}$$



V_P : pinchoff voltage

Specific
current

I_S

Threshold
voltage

V_{T0}

Slope
factor

n


DIBL
factor

σ

MOSFET: Weak inversion (WI) model-1

$$I_D = I_F - I_R = I_0 \left(e^{\frac{V_P - V_{SB}}{\phi_t}} - e^{\frac{V_P - V_{DB}}{\phi_t}} \right)$$
 
$$V_P \cong \frac{V_{GB} - V_{T0}}{n} \quad I_0 = \mu C_{ox} n \phi_t^2 e^1 (W/L)$$




Weak inversion MOSFET model-2

$$I_D = I_0 e^{\left(\frac{V_{GS} - V_T}{n\phi_t}\right)} \left[1 - e^{-V_{DS}/\phi_t}\right]$$


$$I_0 = \mu C_{ox} n \phi_t^2 e^1 (W/L)$$

$$V_T = V_{T0} + (n - 1)V_{SB}$$


$V_G, V_S = \text{const.}$

 


$V_S, V_D = \text{const.}$

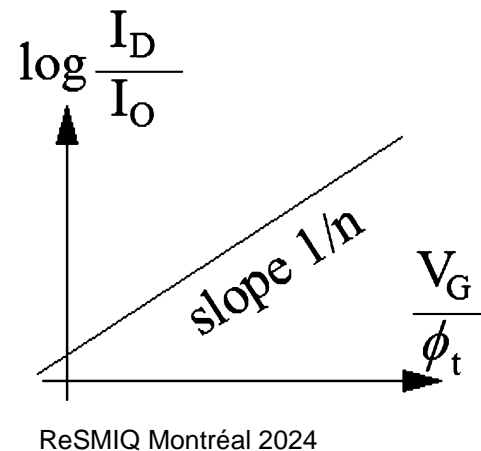

$V_G, V_D = \text{const.}$

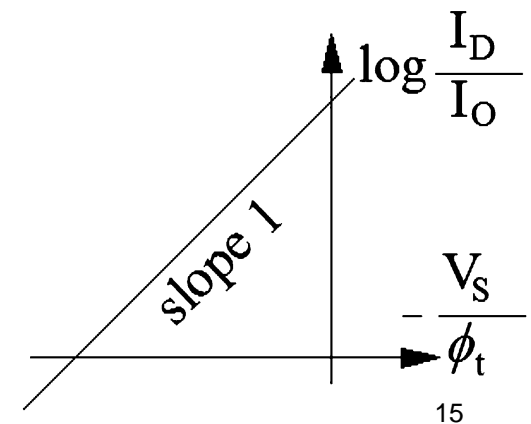


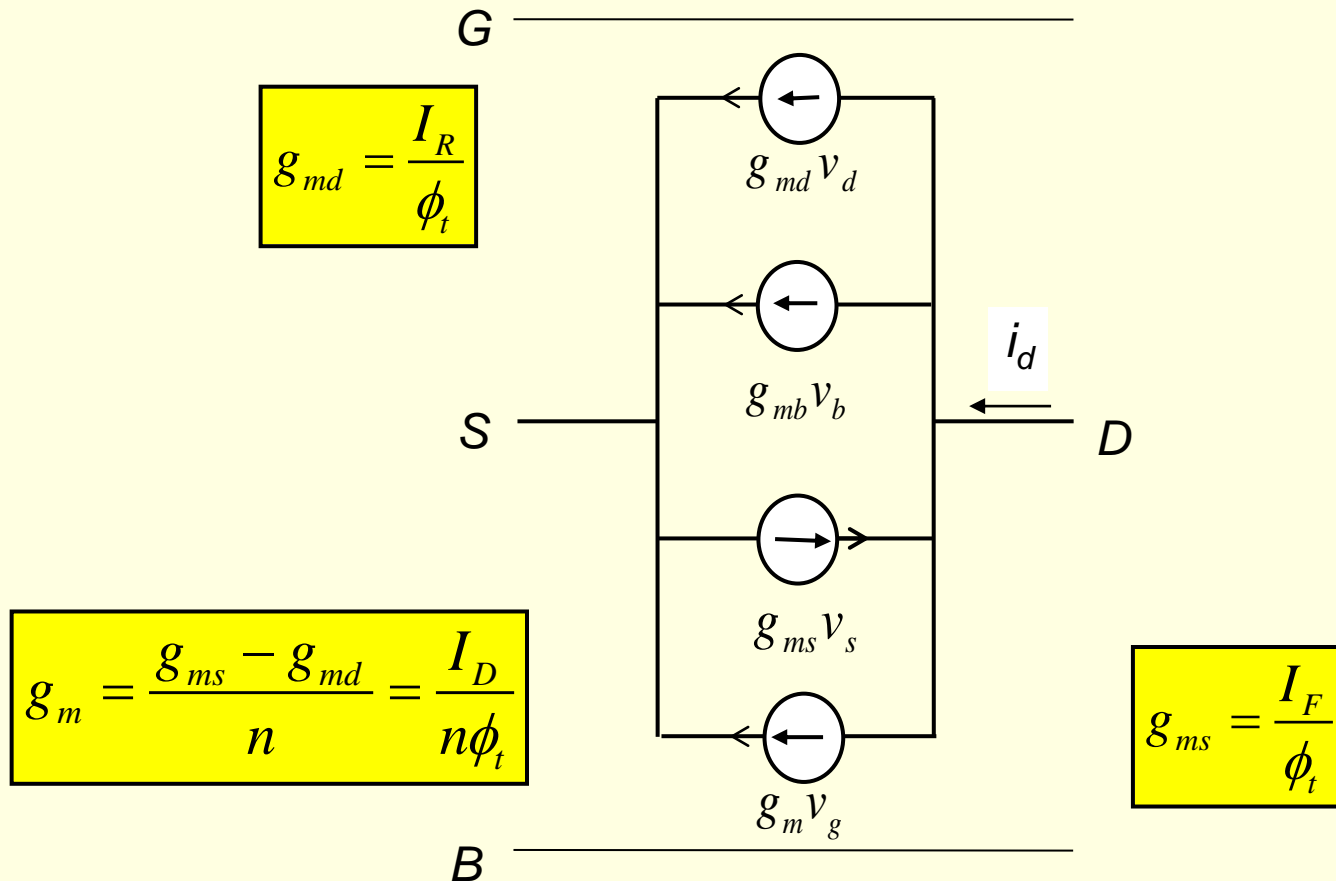MOSFET: low-frequency small-signal model in weak inversion



$$g_{ms} = g_m + g_{mb} + g_{md}$$

 Low-voltage operation of the common-source amplifier



Intrinsic gain stage
(I_B ideal current source)

weak inversion operation

$$|A_V| = \frac{g_m}{g_{md}} = \frac{g_{ms} - g_{md}}{ng_{md}} = \frac{1}{n} \left(\frac{g_{ms}}{g_{md}} - 1 \right)$$


$$\frac{g_{ms}}{g_{md}} = e^{\frac{V_{DS}}{\phi_t}}$$

$$|A_V| = \frac{1}{n} \left(e^{\frac{V_{DS}}{\phi_t}} - 1 \right)$$

or

$$V_{DS} = \phi_t \ln(1 + n|A_V|)$$

 Low-voltage operation of the (C)MOS inverter




$$V_{DS} = \phi_t \ln(1 + n|A_V|)$$

Minimum supply voltage for amplification $|A_V| = 1$

'ideal' MOSFET $n = 1$

$$V_{DS} = V_{DD}$$

$$V_{DD\min} = (\ln 2)\phi_t$$

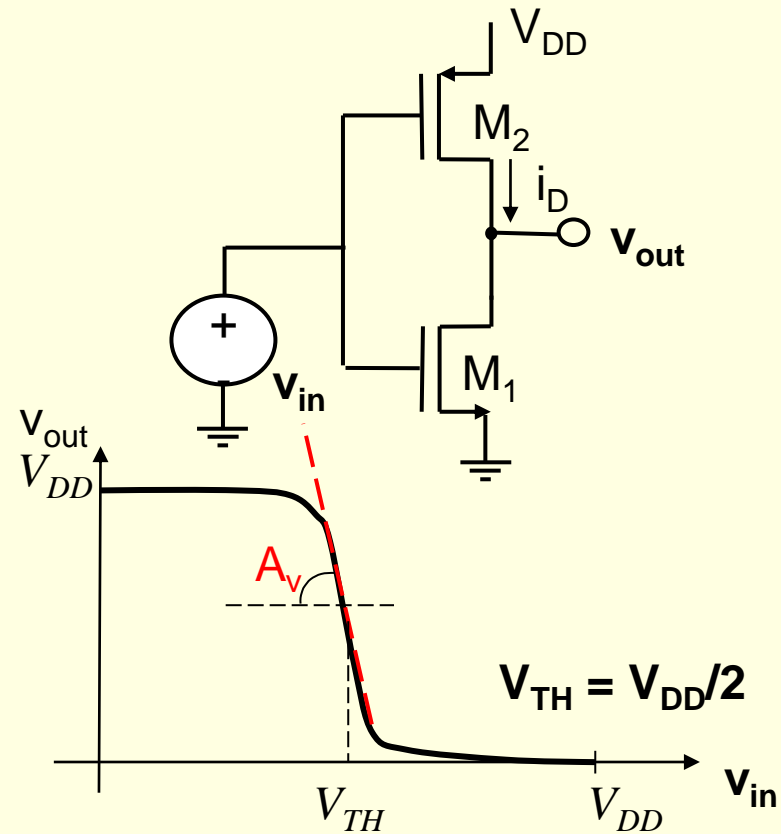


$$V_{DS} = V_{DD} / 2$$

$$V_{DD\min} = 2(\ln 2)\phi_t$$


J. Meindl, IEEE JSSC, 2000

 Low-voltage operation of the common-gate amplifier



$$A_{v, cg} = \frac{v_o}{v_i} = \frac{g_{ms}}{g_{md}} = e^{\frac{qV_{DS}}{kT}}$$

 The common-gate amplifier provides a voltage gain of greater than unity for $V_{DS} > 0$. → Very useful property for lowering the supply voltage limit for the operation of oscillators (later).



Common-gate Colpitts oscillator

References


- E. Vittoz, "Weak inversion for ultimate low-power logic", in *Low-Power Electronics Design*, CRC Press, 2005.
- Márcio Cherem Schneider and Carlos Galup-Montoro, *CMOS Analog Design Using All-Region MOSFET Modeling*, Cambridge University Press, 2010.
- C. M. Adornes *et al.* " Bridging the Gap between Design and Simulation of Low-Voltage CMOS Circuits ," *Journal of Low Power Electronics and Applications*, vol. 12, issue 2, June 2022.

Outline

- 1. Introduction
- 2. Subthreshold MOSFET model
- 3. **Ultra-low-voltage (ULV) CMOS digital circuits**
- 4. ULV LC tank oscillators
- 5. ULV rectifiers and voltage multipliers

THE CMOS INVERTER IN WEAK INVERSION 1

$$I_{DN(P)} = I_{ON(P)} \cdot e^{\frac{V_{GB(BG)} - |V_{TN(P)}| - n_{N(P)} \cdot V_{SB(BS)}}{n_{N(P)} \cdot \varphi_t}} \cdot \left(1 - e^{-\frac{V_{DS(SD)}}{\varphi_t}}\right)$$

 

- The strength or current capability of the transistor is given by

$$I_{N(P)} = I_{ON(P)} \cdot e^{\frac{-|V_{TN(P)}|}{n_{N(P)} \cdot \varphi_t}}$$

- For the sake of simplicity let $n_N = n_P = n$. The static transfer function of the inverter is obtained from

$$I_{DN} = I_{DP}$$

$$I_{ON} \cdot e^{\frac{V_I - V_{TN}}{n \cdot \varphi_t}} \cdot \left(1 - e^{-\frac{V_O}{\varphi_t}}\right) = I_{OP} \cdot e^{\frac{V_{DD} - V_I - |V_{TP}|}{n \cdot \varphi_t}} \cdot \left(1 - e^{-\frac{V_{DD} - V_O}{\varphi_t}}\right)$$



THE CMOS INVERTER IN WEAK INVERSION 2

$$V_I = \frac{V_{DD}}{2} + \frac{V_{TN} - |V_{TP}|}{2} + \frac{n \cdot \phi_t}{2} \cdot \ln\left(\frac{I_{OP}}{I_{ON}}\right) + \frac{n \cdot \phi_t}{2} \cdot \ln\left(\frac{1 - e^{-\frac{V_{DD}-V_O}{\phi_t}}}{1 - e^{-\frac{V_O}{\phi_t}}}\right)$$

In the ideal case of NMOS and PMOS transistors with the same strength, i.e. $I_{ON}=I_{OP}$ and $V_{TN}=|V_{TP}|$, the VTC reduces to

$$V_I = \frac{V_{DD}}{2} + \frac{n \cdot \phi_t}{2} \cdot \ln\left(\frac{1 - e^{-\frac{V_{DD}-V_O}{\phi_t}}}{1 - e^{-\frac{V_O}{\phi_t}}}\right)$$

THE CMOS INVERTER IN WEAK INVERSION 3

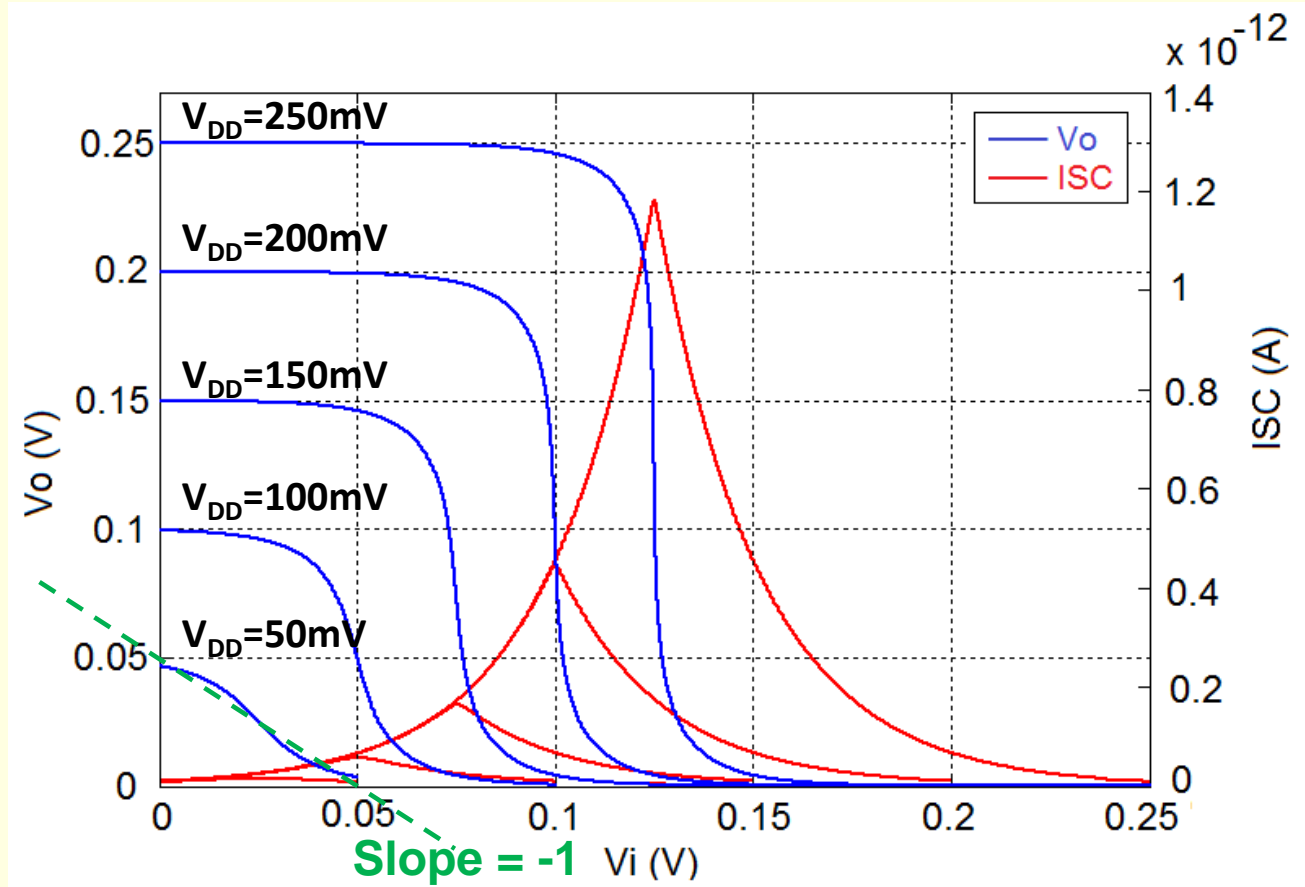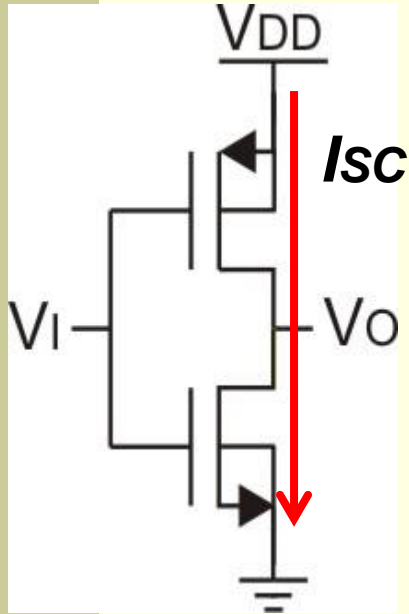

V_{DD}	V_{oH} ($V_i = 0$)	V_{oL} ($V_i = V_{DD}$)
200 mV	200 mV	0mV
50 mV	46.6 mV	3.4mV

Note that:

THE CMOS INVERTER IN WEAK INVERSION 4

- The inverter threshold voltage, V_M , is defined as the voltage such that $V_I = V_O$. In the case for which the transistors have the same strength ($I_N = I_P$) then $V_M = V_{DD}/2$. If the NMOS transistor is stronger than the PMOS transistor, $V_M < V_{DD}/2$, whereas if the PMOS transistor is stronger than the NMOS transistor, $V_M > V_{DD}/2$

$$V_M \approx \frac{V_{DD}}{2} + \frac{\frac{V_{TN} - |V_{TP}|}{2} + \frac{n \cdot \phi_t}{2} \cdot \ln\left(\frac{I_{OP}}{I_{ON}}\right)}{1 + \left. \frac{dV_I}{dV_O} \right|_{V_O = \frac{V_{DD}}{2}}}$$

$$\left. \frac{dV_O}{dV_I} \right|_{V_O = \frac{V_{DD}}{2}} = \frac{e^{\frac{V_{DD}}{2 \cdot \phi_t}} - 1}{n}$$


THE CMOS INVERTER IN WEAK INVERSION 5

- The minimum operating supply voltage of the inverter and any CMOS static logic gate must be at least equal to unity, *i.e.*

$$\left| \frac{dV_o}{dV_I} \right|_{V_o = \frac{V_{DD}}{2}} = 1 \qquad \left| \frac{dV_o}{dV_I} \right|_{V_o = \frac{V_{DD}}{2}} = \frac{e^{\frac{V_{DD}}{2 \cdot \phi_t}} - 1}{n}$$

$$V_{DD \min} = 2\phi_t \ln(2) = 36\text{mV at } 300\text{K}$$

 Minimum supply voltage for the CMOS inverter



CMOS inverter transfer characteristics
(Swanson and Meindl, IEEE JSSC 1972)

Prof. James Meindl:
Theoretically, the minimum
supply voltage for a CMOS
inverter is
 $2 (\ln 2) (kT/q) = 36 \text{ mV}$
at room temperature
(IEEE JSSC, 2000)

Minimum Energy per Operation



Predicted by von Neumann: $kT\ln(2)$

J. von Neumann,

[Theory of Self-Reproducing Automata, 1966].


- Moving one electron over $V_{DDmin} = 2\ln(2)kT/q$
 - $E_{min} = QV_{DD}/2 = q \cdot 2(\ln 2)kT/2q = kT\ln(2)$
 - Also called the *Von Neumann-Landauer-Shannon* bound
 - At room temperature (300K): **$E_{min} = 0.29 \cdot 10^{-20} \text{ J}$**
- Minimum sized CMOS inverter at 90 nm operating at 1V
 - **$E = CV_{DD}^2 = 0.8 \cdot 10^{-15} \text{ J}$** , or 5 orders of magnitude larger!

How close can one get?


from J. Rabaey, Low Power Design Essentials, Springer 2009

ReSMIQ Montréal 2024

Imbalance in the CMOS Inverter - 1

 


Classical CMOS inverter

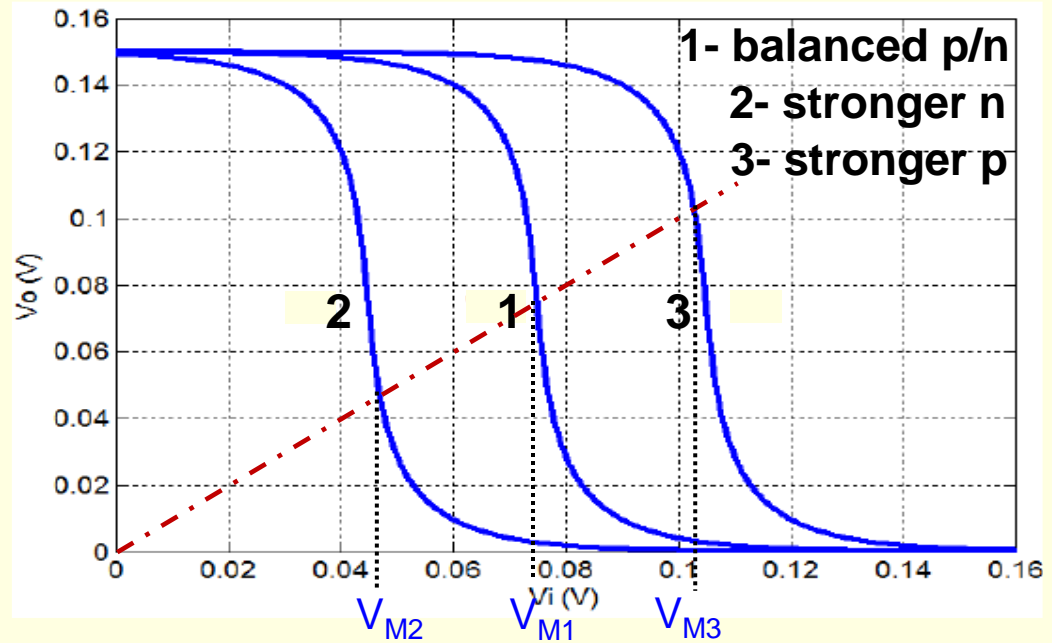

Consequences of imbalance between p/n transistors:


- **Non-centered VTC characteristic ($V_M \neq V_{DD}/2$);**
- **Unbalanced high-to-low and low-to-high transient times;**
- **Reduced noise margin;**
- **Lower gain at the inverter threshold voltage;....**

Imbalance in the CMOS Inverter¹ - 2

 


α : off current_{NMOS}/ off current_{PMOS}

$$\alpha = \frac{I_{0N}}{I_{0P}} = \frac{\mu_N \frac{W_N}{L_N}}{\mu_P \frac{W_P}{L_P}} \frac{e^{-\left(\frac{V_{TN}}{n\phi_t}\right)}}{e^{-\left(\frac{|V_{TP}|}{n\phi_t}\right)}}$$

 


Inverter threshold voltage V_M versus α

 

Minimum supply voltage for unity gain versus n/p imbalance ($n_N=n_P=1$)


BODY-BIAS COMPENSATION-1

 The VTC of an inverter is affected by process parameters such as V_T .



TT – Typical NMOS and PMOS
FS – Fast NMOS, Slow PMOS
SF – Slow NMOS, Fast PMOS

 Large difference in rise and fall times due to PMOS/NMOS asymmetry.



This asymmetry represents a waste of energy since the maximum operating frequency is given by the sum of the rise and fall times.


BODY-BIAS COMPENSATION-2

Common Techniques:


*Reverse Body Bias (RBB) – $V_{BP} > V_{DD}$,
 $V_{BN} < GND$*

*Forward Body Bias (FBB) – $V_{BP} < V_{DD}$,
 $V_{BN} > GND$*

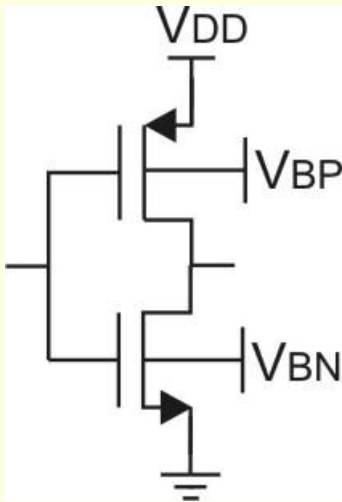
*RBB – difficult to generate bias voltages
FBB – is limited to sub-1V since two
parasitic diodes are forward biased.
Latch-up must be avoided.*



BODY-BIAS COMPENSATION-3

 


Standard inverter

 


BB inverter


V_w generators (forward body bias)

 

**“Off” Circuit
Bryant [2001]**

 

**“On”
Circuit**


 


**“Midway”
Circuit**

V_w → results from equalization of NMOS and PMOS currents


BODY-BIAS COMPENSATION-4

  Inverter transient simulation without body bias (NBB) and with the “midway” compensation circuit (FBB).





For FBB T_{HL} and T_{LH} are closer and faster than for NBB.

Gain-enhanced self-bias inverters¹

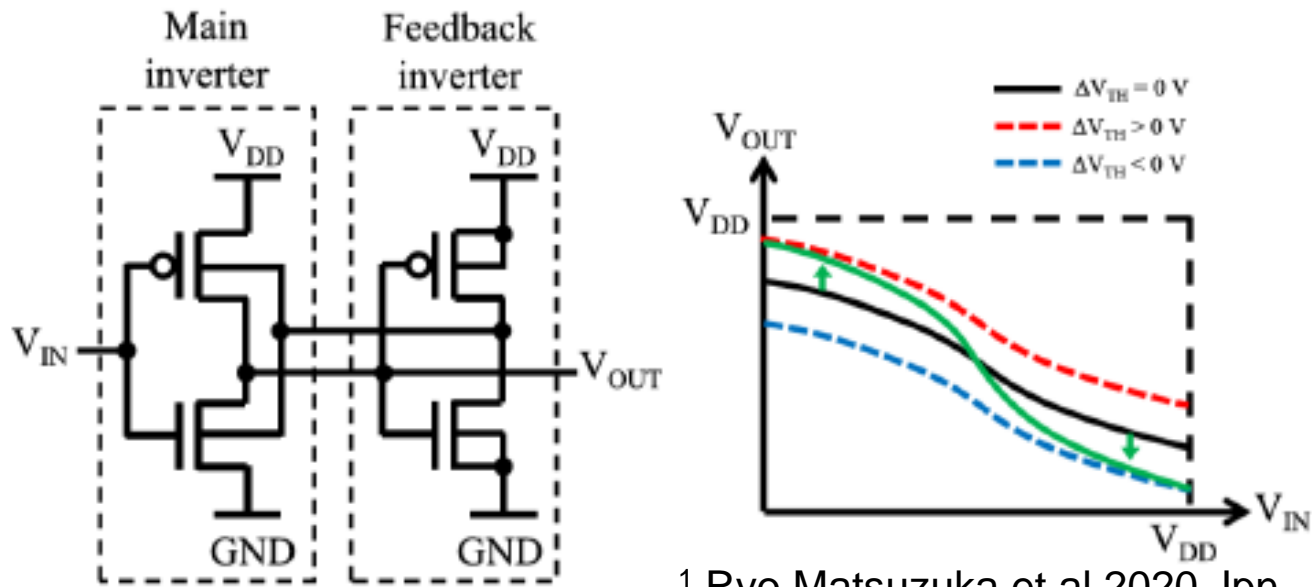

 
 
¹ Ryo Matsuzuka et al 2020 Jpn. J. Appl. Phys. 59



The Stacked-Inverter Gate (SIG)¹

$$K = I_0/I_2 \text{ and } J = I_1/I_2$$


$$N_i = P_i \quad i=0, 1, 2$$

 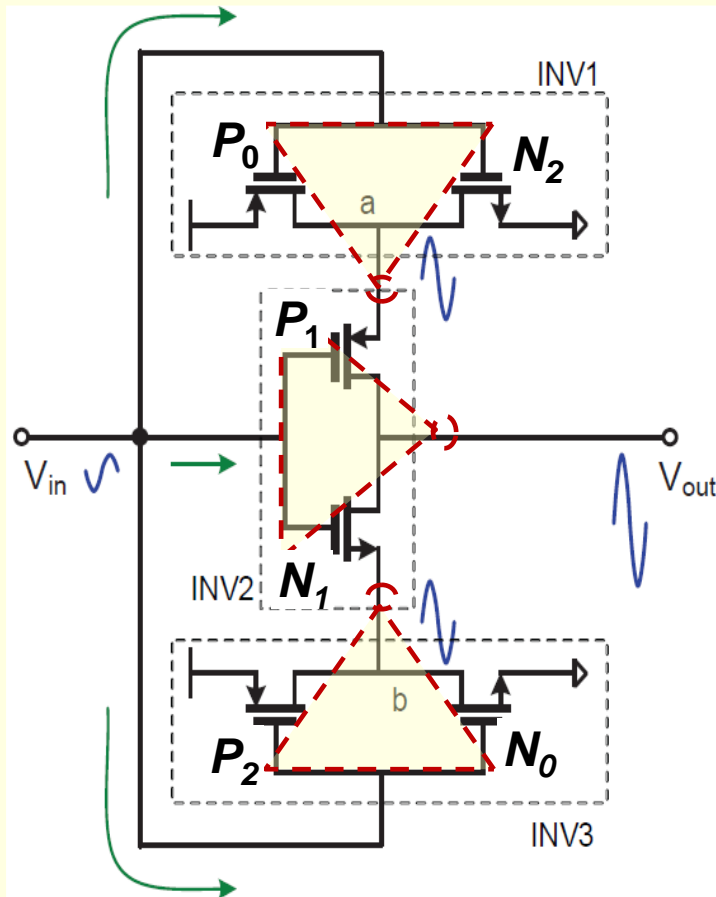

SIG V_{DDmin} for unity gain versus K
with $J = 1$

V_{DDmin} without positive feedback →
→ no hysteresis



Combining techniques¹⁻¹

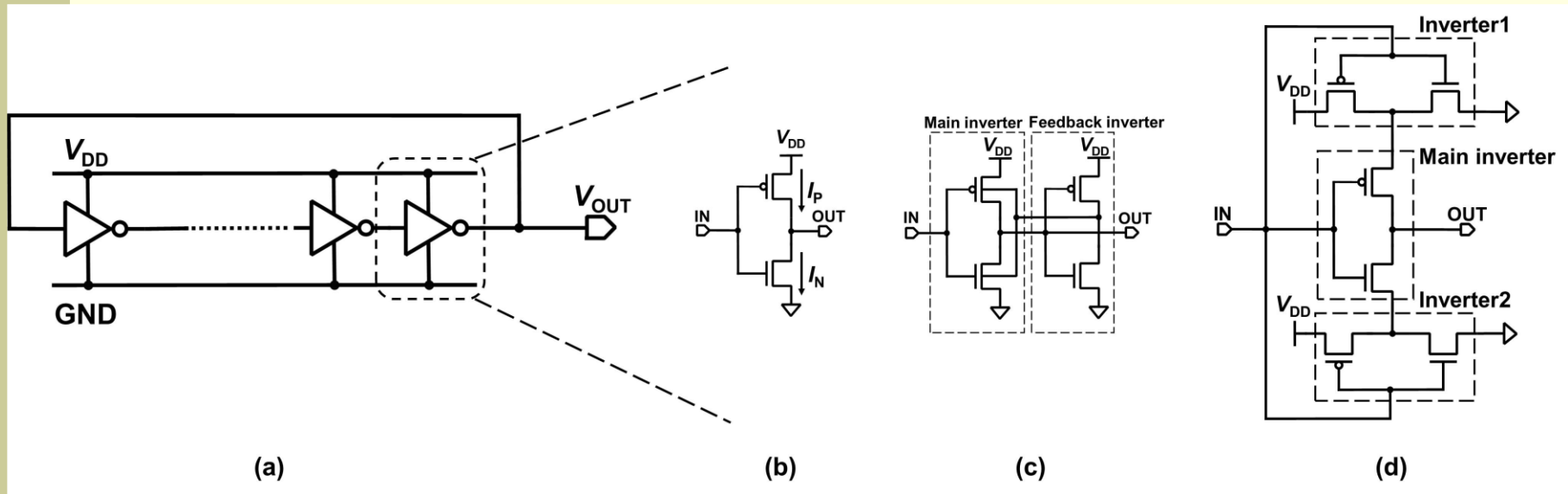

(a) ROSC, (b) normal inverter (NI), (c) self-bias inverter (SBI) and (d) stacked inverter (SI).

¹ M. Ahmed *et al.* *IEEE Access*, vol. 12, 2024


Combining techniques²-2

 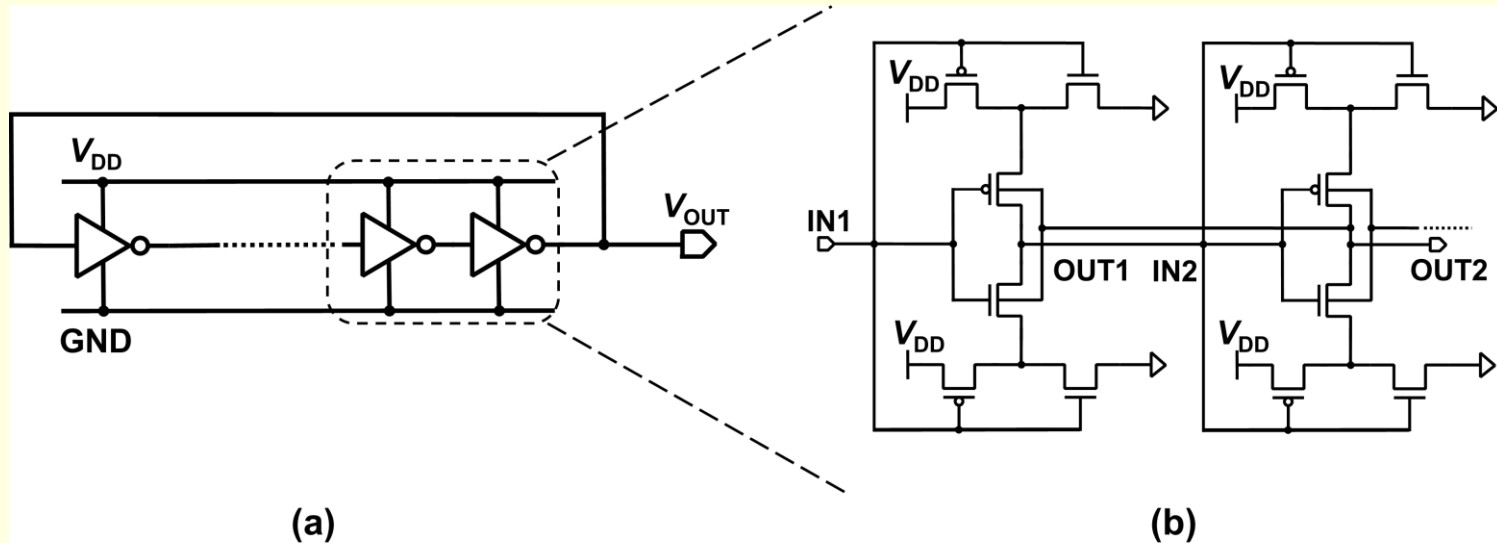

(NI) normal inverter
 (SBI) self-bias inverter
 (SI) stacked inverter

² M. Nishi *et al.* in 2020 NEWCAS





The CMOS Schmitt trigger

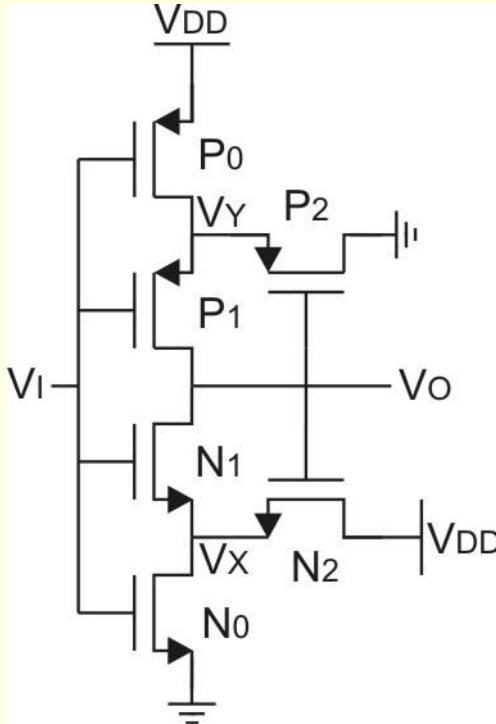



- *2 internal nodes (VX and VY)*
- *Feedback transistors (P2/N2) controlled by the output*
- *Hysteresis dependent on VDD & relative transistor strength*
- *Modeled in strong inversion but only recently (2017) in weak inversion*
 - *For symmetric operation, corresponding NMOS and PMOS MOSFETs have the same current capability.*

**6 transistors (6T)
Schmitt Trigger**



Schmitt Trigger operation 1

    



Schmitt Trigger operation 2

  



Schmitt Trigger operation 3

  



Schmitt Trigger operation 4

  



Schmitt Trigger operation 5

  



Schmitt Trigger operation 6

  



Schmitt Trigger operation 7

  

Schmitt Trigger operation 8

  



Schmitt Trigger operation 9

  

The 6-T Schmitt trigger


Hysteresis mode

Amplifier mode

 
 


ST sensitivity to p/n imbalance

 ST inverter is less sensitive to process parameters (V_T) spreading than the standard inverter.



SCHMITT TRIGGER as an amplifier

 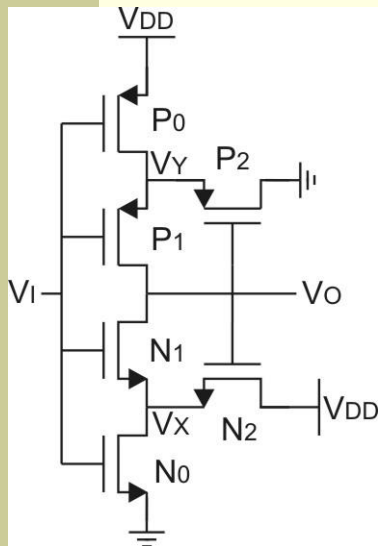

VDD (mV)	I2/I0 opt (A/A)
100	1.5479
90	1.3110
80	1.0973
75	0.9987
70	0.9051
60	0.7324
50	0.5774
40	0.4384
36	0.3869
31	0.3333

$$\left. \frac{I_1}{I_0} \right|_{OPTIMUM} = 0$$

$$\left. \frac{I_2}{I_0} \right|_{OPTIMUM} = \frac{\sqrt{1 + e^{\frac{V_{DD}}{2\phi_t}} - e^{-\frac{V_{DD}}{2\phi_t}} - 1}}{1 + e^{-\frac{V_{DD}}{2\phi_t}}}$$



Result in highest possible gain for a given VDD

$I_{0,1,2}$ is the current strength of $N_{0,1,2}$ and $P_{0,1,2}$

The ST as an ULV Logic Inverter-1

Conventional Inverter x Schmitt trigger

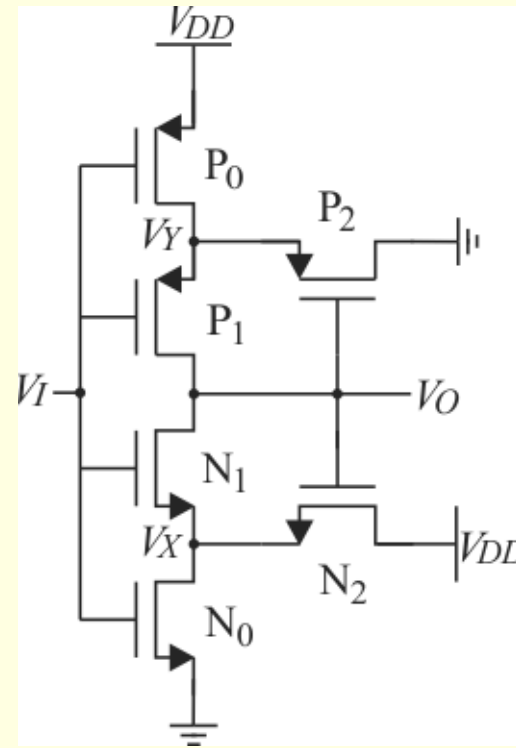 The conventional inverter is the ST with $k_2 = 0$.



$$V_{DD\min} = 2\phi_t \cdot \ln(2) = 35.9 \text{ mV, at } 300\text{K}$$



**Swanson & Meindl
1972**

$$V_{DD\min} = 2\phi_t \cdot \ln\left(\frac{8 + \sqrt{73}}{9}\right) = 31.5 \text{ mV, at } 300\text{K}$$

Pasini et al 2017

The ST as an ULV Logic Inverter-2

  
Conventional Inverter x Schmitt trigger – Experimental Results




Voltage gain transfer

6-T Schmitt trigger logic


NOR gate

 

ST-NOR gate

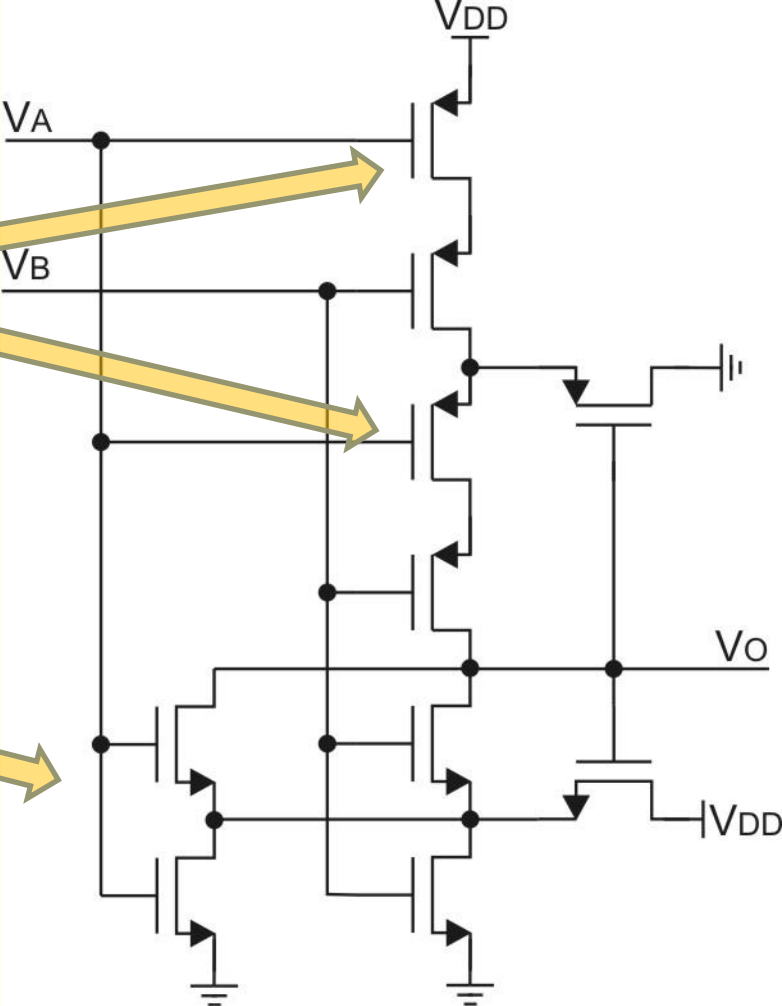


Inverter, SIG, and standard ST

 


|Voltage gain|: Stacked Inverter > Standard ST > Inverter

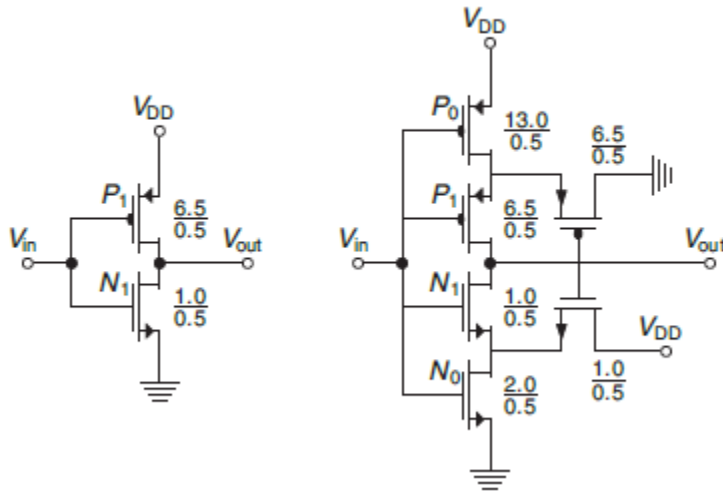Ultra-low-voltage CMOS ring oscillators-1




 W/L PMOS and NMOS transistors to balance the current strengths of the transistors for a supply voltage of 60 mV. The four types of ROs : INV (standard inverters), INVB (standard inverters, substrates to the gate), ST (conventional ST), and STB (conventional ST, substrates to gates)




$$\omega_{osc} C / g_o = \tan(\pi/N)$$

 
$$g_m / g_o = \sqrt{1 + \tan^2(\pi/N)} \approx 1 + \frac{1}{2}(\pi/N)^2$$



 Ultra-low-voltage CMOS ring oscillators¹⁻²



 
Waveforms of the buffer outputs (top) and differential output voltage of the buffers (bottom) for the STB with the gates connected to the substrates and $V_{DD} = 48\text{mV}$




Single and differential output voltages for the STB, with $V_{DD} = 80\text{mV}$. Differential output (diff.) is 20 mV/div

¹J. Ferreira and C. Galup-Montoro, "Ultra-low-voltage CMOS ring oscillators," *Electronics Letters*, March 2019.

 
Ultra-low-voltage CMOS ring oscillators-3



 The peak-to-peak amplitude of oscillation for four types of ROs




 
Measured oscillation frequency as a function of the supply voltage




Histogram of the minimum supply voltage for the start-up of the STB oscillator (40 samples)

ST-Based Divide-by-Two Frequency Divider^{1, 2}

ST-based frequency divider with 2 stages

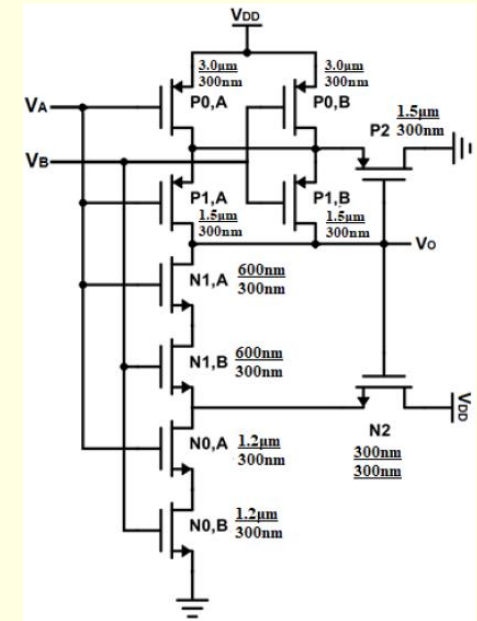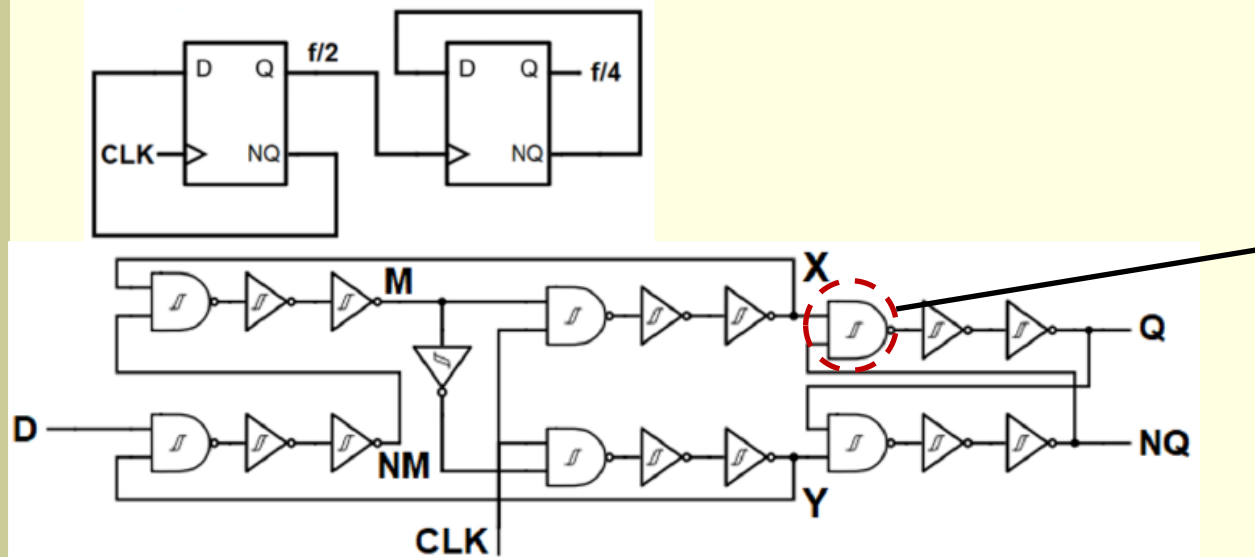

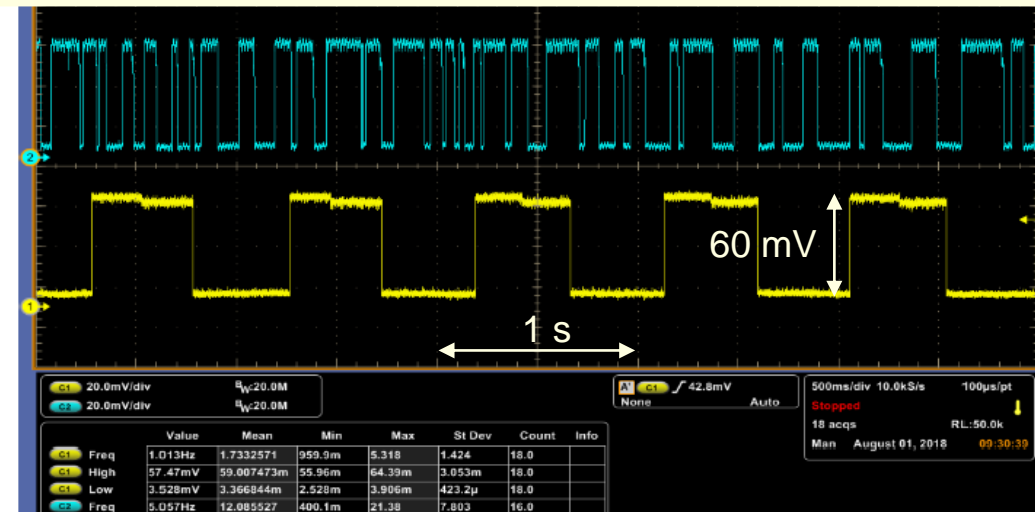Output signals of frequency divider (2^{15}) at $f_{in} = 32768$ Hz, $V_{DD} = 76$ mV.
 Classical logic: upper wave
 ST logic: lower wave





¹ D.G. Alves Neto, C. Galup-Montoro, ISCAS 2020

² N. Lotze, Y. Manoli, JSSC 2012


ST Pierce Oscillator¹

130 nm CMOS

Parameter	Oscillator A	Oscillator B
Crystal part number	ABS07W-32.768kHz-D1	AB38T-32.768kHz-12.5pF-E-7
$C_1 = C_2$ [pF]	6	25
C_3 [pF]	1.15	1.60
R_F [GΩ]	5	5

  

Minimum supply voltage for starting up

 

Waveforms of oscillators A and B

¹ M.Siniscalchi, F. Silveira, C. Galup-Montoro, IEEE TCAS-I, 2020.


References

- R. M. Swanson and J. D. Meindl, "Ion-implanted complementary MOS transistors in low voltage circuits," *IEEE J. Solid State Circuits*, vol. 7, pp. 146-153, Apr. 1972.
- J. D. Meindl and A. J. Davis, "The fundamental limit on binary switching energy for terascale integration (TSI)," *IEEE J. Solid-State Circuits*, vol. 35, no. 10, pp. 1515-1516, Oct. 2000.
- E. Vittoz, "Weak inversion for ultimate low-power logic", in *Low-Power Electronics Design*, CRC Press, 2005.
- N. Lotze and Y. Manoli, "A 62mV 0.13um CMOS standard-cell-based design technique using Schmitt-Trigger logic", *IEEE Journal of Solid-State Circuits*, Jan 2012.
- L. A. P. Malek *et al.*, Ultra-Low Voltage CMOS Logic Circuits, *2014 Argentine Conference on Micro-Nanoelectronics, Technology and Applications (EAMTA)*, Mendoza, Argentina 2014.
- L. A. P. Melek *et al.*, "Analysis and design of the classical CMOS Schmitt trigger in subthreshold operation", *IEEE Trans. Circuits and Systems-I: Reg. Papers*, April 2017.
- L. A. P. Melek *et al.*, "Operation of the Classical CMOS Schmitt Trigger as an Ultra-Low-Voltage Amplifier," *IEEE Transactions on Circuits and Systems II-Express Briefs*, Sep. 2018.

Outline

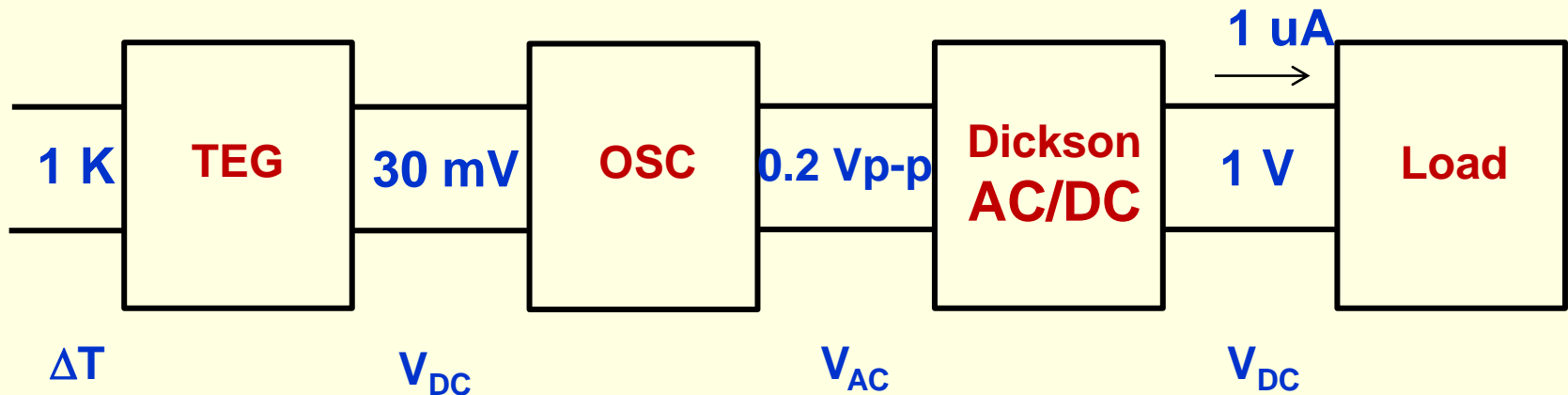- **1. Introduction**
- **2. Subthreshold MOSFET model**
- **3. Ultra-low-voltage (ULV) CMOS digital circuits**
- **4. ULV LC tank oscillators**
- **5. ULV rectifiers and voltage multipliers**

An important application of ULV oscillators




TEG – thermoelectric generator




OSC – oscillator

Zero-V_T MOSFETs-1

2 – high g_m/C (f_T) for low voltages

 

Zero-VT MOSFETs-2

 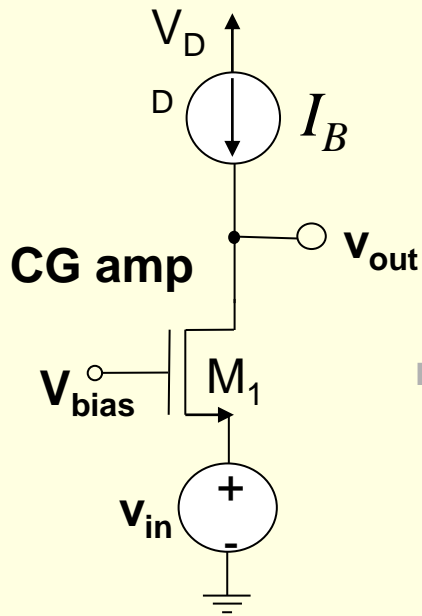 

- $I_D \times V_{DS}$ ($V_S = V_B$) characteristics for a zero-VT transistor with $W/L=2500\mu\text{m}/420\text{nm}$. For $V_{GS} = 0$ V and $V_{DS} = 25$ mV the values of the common-gate and common-source gains are 1.56 and 0.53, respectively (moderate inversion operation).

The pioneer of zero-VT MOSFETs and ULV digital

Cryogenic Ultra Low Power CMOS


James B. Burr

Department of Electrical Engineering, Stanford University, Stanford CA 94305
burr@mojave.stanford.edu


This paper reports 7-stage 1.5 μ m zero Vt CMOS ring oscillators operating at 170MHz/V down to $V_{DD} = 70$ mV at room temperature, and 360MHz/V down to $V_{DD} = 27$ mV at 77degK.

Stanford's Space, Telecommunications, and Radioscience Laboratory has been working on an energy-efficient CMOS technology since December 1990 which can achieve good performance at extremely low supply voltages. Early theoretical work predicted minimum energy at supply and threshold voltages around 120mV at room temperature.

 Inductive ring (X-coupled) oscillator - 1



Cross-coupled LC oscillator

 

$$\frac{V_{out}}{V_{in}} = - \frac{g_m}{g_{md} + G_P} \frac{1}{1 - j \tan \phi} = -1$$

$$\tan \phi = \frac{1 - LC\omega^2}{\omega L(g_{md} + G_P)}$$

Criterion for oscillation (Barkhausen)


$$\phi = 0 \quad \& \quad V_{out}/V_{in} = -1$$

$$\omega^2 LC = 1$$

$$\frac{g_m}{g_{md} + G_P} = 1$$

What's the minimum V_{DD} for oscillation?

Inductive ring oscillator - 2

 

Cross-coupled LC oscillator

Oscillation frequency $\omega^2 LC = 1$

Voltage gain $\frac{g_m}{g_{md} + G_P} = 1$

What's the minimum V_{DD} for oscillation?

Recall that $g_m = \frac{g_{ms} - g_{md}}{n}$


Voltage gain=1 \Rightarrow (i) $\frac{g_{ms}}{g_{md}} = 1 + n \left(1 + \frac{G_P}{g_{md}} \right)$

In weak inversion \Rightarrow (ii) $\frac{g_{ms}}{g_{md}} = e^{V_{DS}/\varphi_t} = e^{V_{DD}/\varphi_t}$ since $V_G = V_D = V_{DD}$

$$V_{DD,\min} = \varphi_t \ln \left[1 + n \left(1 + \frac{G_P}{g_{md}} \right) \right] = \varphi_t \ln [1 + n] \quad \text{for } \frac{G_P}{g_{md}} \ll 1$$

Similar to the result (1/2) of the CMOS inverter

Inductive ring oscillator - 3

 



Questions:

1. How to reduce $V_{DD,min}$?
2. How to increase the V_{DD} -limited voltage swing?

Introduce voltage gain from drain to gate

Change topology, e. g., take advantage of CG gain




Enhanced swing IRO (ESRO)

 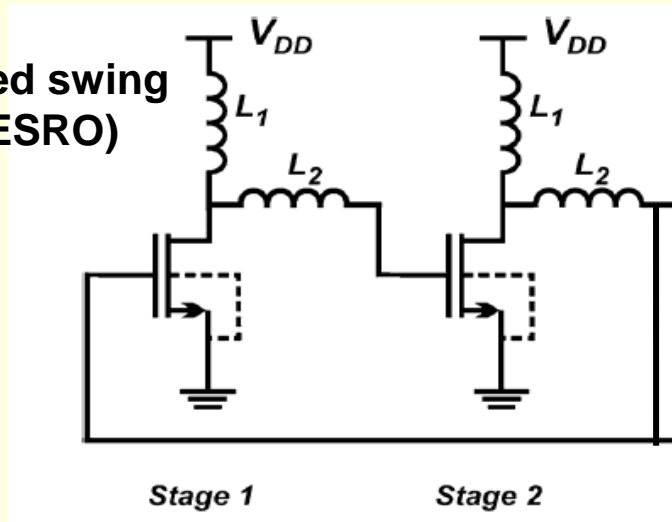

Enhanced swing Colpitts oscillator (ESCO) *

* T. W. Brown et al, *IEEE JSSC*, Aug. 2011.

Enhanced swing IRO (ESRO)-1

   

Enhanced swing IRO (ESRO)-2

 
 


Fig. 13. Picture showing the discrete prototype of the enhanced swing inductive-load oscillator and test equipment.


 
 


Fig. 12. Simulated (dotted line) and experimental (solid line) peak-to-peak gate voltage versus supply voltage of the ES inductive-load ring oscillator.

ESCO: small-signal model

 


$$v_s \cong \frac{v_d}{1 + \frac{C_2}{C_1}} \rightarrow g_{ms} v_s - g_{md} v_d \cong g'_m v_s$$


$$g'_m = g_{ms} - \left(1 + \frac{C_2}{C_1}\right) g_{md}$$

ESCO: start-up condition
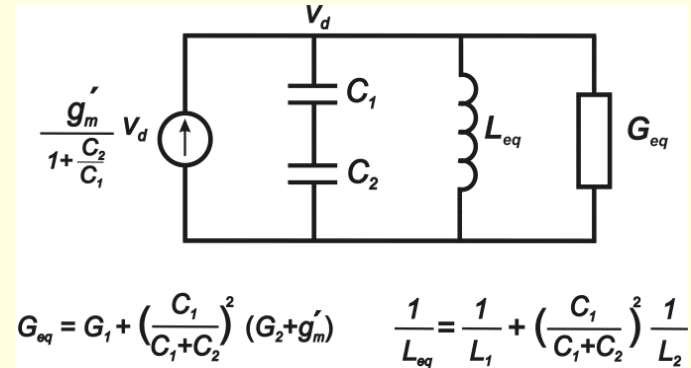
$$g_{ms} > \left(1 + \frac{C_2}{C_1}\right) g_{md} + \frac{C_1}{C_2} G_2 + \left(2 + \frac{C_1}{C_2} + \frac{C_2}{C_1}\right) G_1$$




 Optimum value of capacitors to minimize g_{ms} (for the conventional Colpitts $g_{md} = G_2 = 0$!)




$$\frac{C_2}{C_1} = \sqrt{\frac{G_1 + G_2}{g_{md} + G_1}}$$

 For ideal inductors (and capacitors) $G_1 = G_2 = 0$




 
$$g_{ms} > \left(1 + \frac{C_2}{C_1}\right) g_{md}$$



$$V_{DD\lim} = \frac{kT}{q} \ln\left(1 + \frac{C_2}{C_1}\right)$$


Colpitts oscillator: first prototype

Powered by a thermoelectric generator

  


$V_{DD}=22.2 \text{ mV}$

$T \approx 24 \text{ }^\circ\text{C}$

 

thermoelectric generator

 24 // NMOS
Zero-VT (ALD 1108)
VT=59 mV, IS=11.2 uA




Colpitts oscillator: second prototype

$V_{DD} < 20 \text{ mV}$


Zero- V_T
IBM 130 nm

L2

 


L1

C1


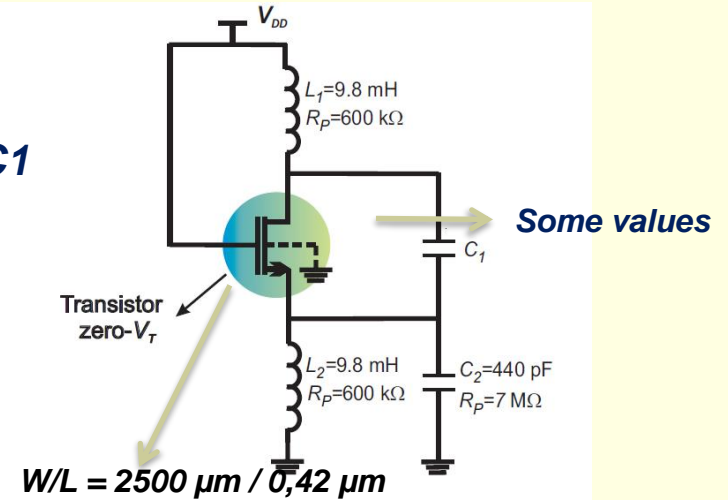


$V_{PP} \approx 440 \text{ mV}$

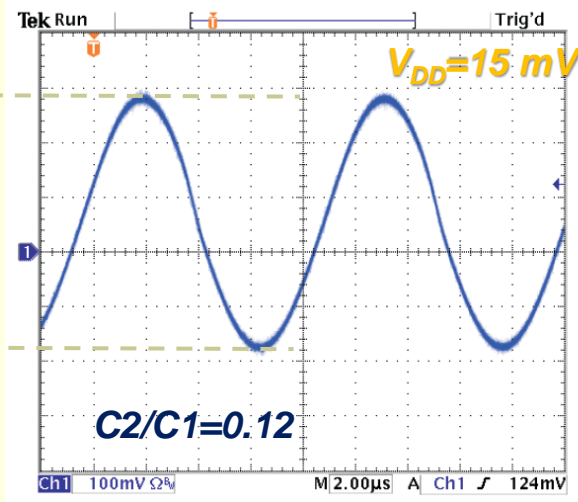

$f_{osc} \approx 110 \text{ kHz}$
 $V_{DD} = 15 \text{ mV}$

ESCO designed for operation at 800 MHz

 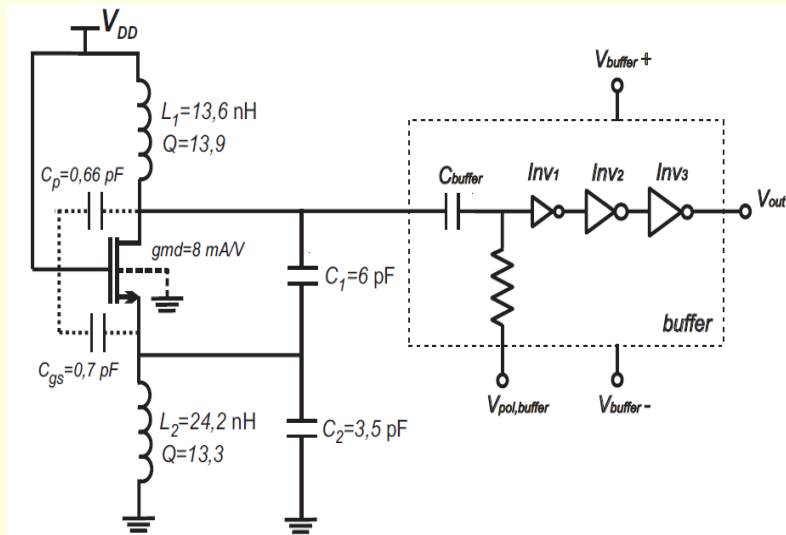

- Micrograph of the ESCO built in 130 nm technology

Spectral diagram of the ESCO ($V_{DD} = 86 \text{ mV}$)

 
 


TABLE I
EXPERIMENTAL RESULTS FOR THE OSCILLATION FREQUENCY AND MINIMUM
SUPPLY VOLTAGE OF THE OSCILLATOR TOPOLOGIES

Topology	Theoretical $V_{dd} (min) *$	IC prototype 130nm CMOS		Discrete prototype	
		$V_{dd} (min)$	f_{osc}	$V_{dd} (min)$	f_{osc}
ILRO	$\phi_t \ln(1+n)$	53 mV	550 MHz	50 mV	11 MHz
ESRO	$\phi_t \ln\left(1+n\frac{L_1}{L_1+L_2}\right)$	32 mV	400 MHz	3.5 mV	1.1 MHz
ESCO	$\phi_t \ln\left(1+\frac{C_2/C_1}{1+L_1/L_2}\right)$	86 mV	700 MHz	15 mV	108 kHz

* For lossless passive devices and operation of MOSFETs in weak inversion

Values of components:

ILRO – IC prototype – $L = 100$ nH, $Q = 8$.

ILRO – discrete prototype – $L = 4.6$ uH, $Q = 50$.

ESRO – IC prototype – $L_1 = 20$ nH, $Q_1 = 9$; $L_2 = 80$ nH, $Q_2 = 8$.

ESRO – discrete prototype – $L_1 = 4.6$ uH, $Q_1 = 55$,
 $L_2 = 1.2$ mH, $Q_2 = 60$.

ESCO – IC prototype – $L_1 = 13.6$ nH, $Q_1 = 13.9$, $L_2 = 24.2$ nH,
 $Q_2 = 13.3$, $C_1 = 6$ pF, $C_2 = 3.5$ pF.

ESCO – discrete prototype – $L_1 = L_2 = 9.8$ mH, $Q_1 = Q_2 = 80$,
 $C_1 = 1.54$ nF, $C_2 = 0.44$ nF.

References


- C. Galup-Montoro, M. C. Schneider, and M. B. Machado, “Ultra-low-voltage operation of CMOS analog circuits: amplifiers, oscillators, and rectifiers,” *IEEE Trans. on Circuits and Syst. II, Exp. Briefs*, Dec. 2012.
- M. B. Machado *et al.* , “On the minimum supply voltage for MOSFET oscillators”, *IEEE Transactions on Circuits and Systems I: Regular Papers*, Feb 2014.
- M. B. Machado *et al.*,"Fully integrated inductive ring oscillators operating at VDD below $2kT/q$," , *Analog Integrated Circuits and Signal Processing*, Jan 2015.

Outline


- **1. Introduction**
- **2. Subthreshold MOSFET model**
- **3. Ultra-low-voltage (ULV) CMOS digital circuits**
- **4. ULV LC tank oscillators**
- **5. ULV rectifiers and voltage multipliers**

Motivation

Wirelessly powered sensors

 


Low power/voltage level

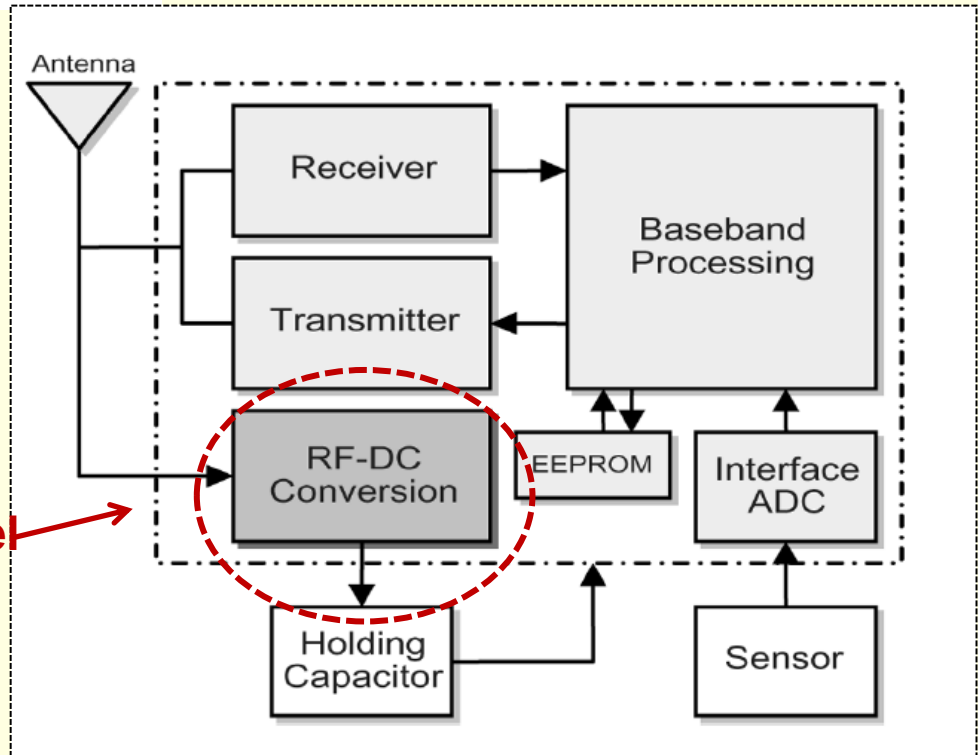


Low-voltage diode circuits

 Dickson analysis of voltage multipliers: constant threshold voltage diode model, **not appropriate for low voltage operation**



$$V_L = V_P - V_{ON}$$

 


How to substitute the constant 'diode voltage drop' model?
Use the i-v characteristic of the diode and the load current


$$I_D = I_S \left[e^{\frac{V_D}{n\phi_t}} - 1 \right] \quad \phi_t = \frac{kT}{q}$$

$n \sim 1 \text{ to } 1.5$

Classical rectifier analysis

 

High V_P
 $V_P \gg V_{on}$
correct

 


$$I_P \cong I_L \left(1 + 2\pi \sqrt{\frac{2V_P}{\Delta V}} \right)$$

$$\Delta V \cong \frac{I_L}{fC}$$

wrong


Low V_P

 $\Delta V \rightarrow 0, I_P \rightarrow \infty !!$



The diode does not have a constant voltage drop, diode current is LIMITED!

Physics-based rectifier model

 

$$V_L \cong V_P - n\phi_t \ln(1 + I_P / I_S) \quad V_P > n\phi_t$$

$$I_P \cong I_L \sqrt{\frac{2\pi V_P}{n\phi_t}}$$



$$\theta_C = 4\sigma = 4 \sqrt{\frac{n\phi_t}{V_P}}$$

$$I_P \theta_C \cong 4 I_L \sqrt{2\pi}$$


$$\Delta V \cong \frac{I_L T}{C} \left(1 - \frac{\theta_C}{2\pi}\right) \cong \frac{I_L T}{C}$$

I_P : peak current
 θ_C : conduction angle

  $V_P = 4.5$ V, $f=120$ Hz and $I_L=4\mu\text{A}$. $I_S = 4.4$ nA and $n\phi_t= 50$ mV. $C=150$ nF and 600 nF.



 ULV rectifier with pure capacitive load - 1




$$V_P \gg n\phi_t$$

Steady-state analysis

$$\frac{1}{T} \int_{-T/2}^{T/2} I_D dt = 0 \quad I_D = I_S \left[e^{\frac{V_D}{n\phi_t}} - 1 \right]$$
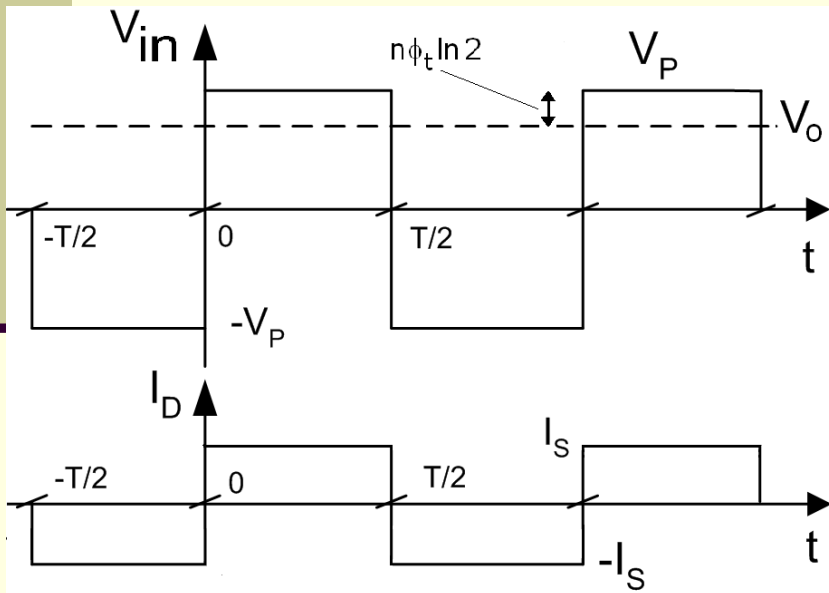
$$\frac{I_S}{T} \left[\int_{-T/2}^0 \left(e^{\left(\frac{-V_P - V_o}{n\phi_t} \right)} - 1 \right) dt + \int_0^{T/2} \left(e^{\left(\frac{V_P - V_o}{n\phi_t} \right)} - 1 \right) dt \right] = 0$$




Assumption: very low ripple

(high C)

→ $V_o \cong \text{constant}$

$$\frac{V_o}{n\phi_t} = \ln \left[\frac{e^{V_P/n\phi_t} + e^{-V_P/n\phi_t}}{2} \right] = \ln \left[\cosh(V_P/n\phi_t) \right]$$

 ULV rectifier with pure capacitive load - 2



$$\frac{V_o}{n\phi_t} = \ln \left[\cosh \left(\frac{V_P}{n\phi_t} \right) \right]$$


Power Detector

$$V_P \ll n\phi_t \rightarrow \frac{V_o}{n\phi_t} \cong \frac{1}{2} \left(\frac{V_P}{n\phi_t} \right)^2$$


Peak Detector Diode "ON" voltage drop

$$V_P \gg n\phi_t \rightarrow V_L \cong V_P - \underbrace{n\phi_t \ln 2}_{\text{Diode "ON" voltage drop}}$$


Input \nearrow

 

Application: microwave power detection

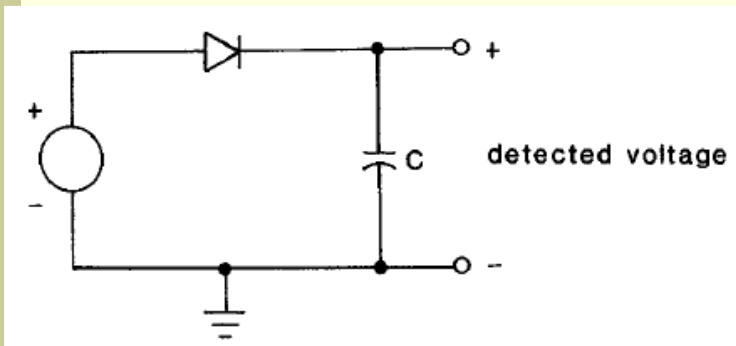

■ Basic detector circuit


 


R. G. Meyer, "Low-power monolithic RF peak detector analysis," IEEE J. Solid-State Circuits, vol. 30, no. 1, pp. 65–67, Jan. 1995.

Wetenkamp, IEEE MTT-S Int. Microwave Symp. Dig., 1983

ULV rectifier with DC load - 1

Output voltage ripple

 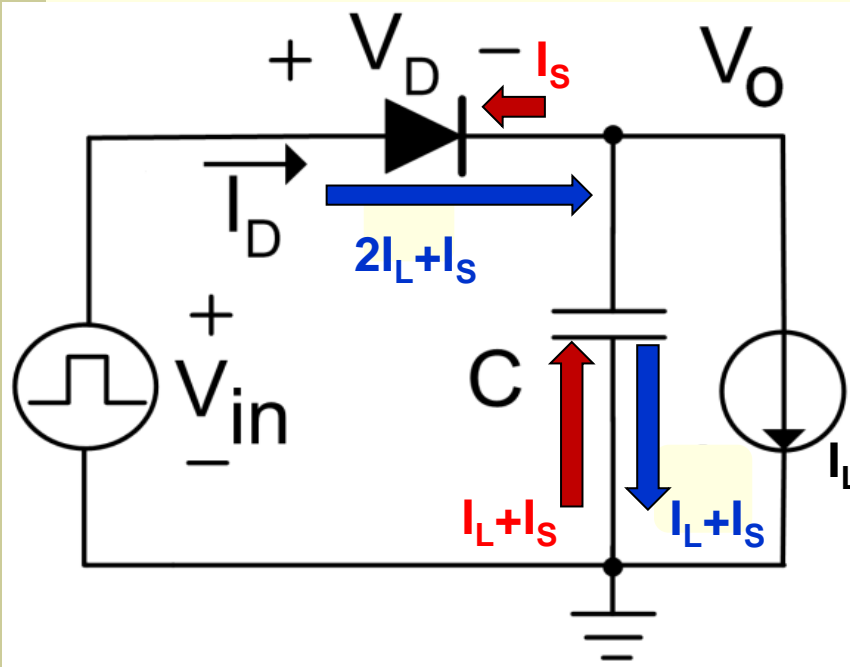


The discharge rate of the capacitor


$$I_C = \frac{dQ_C}{dt} = C \frac{dV_C}{dt} \cong I_L + I_S$$

$$\int_{-T/2}^0 dV_C = \Delta V \cong \frac{I_L + I_S}{C} \frac{T}{2} = \frac{I_L + I_S}{2fC}$$

ULV rectifier with DC load - 2

 

Waveforms for $V_P \gg n\phi_t$

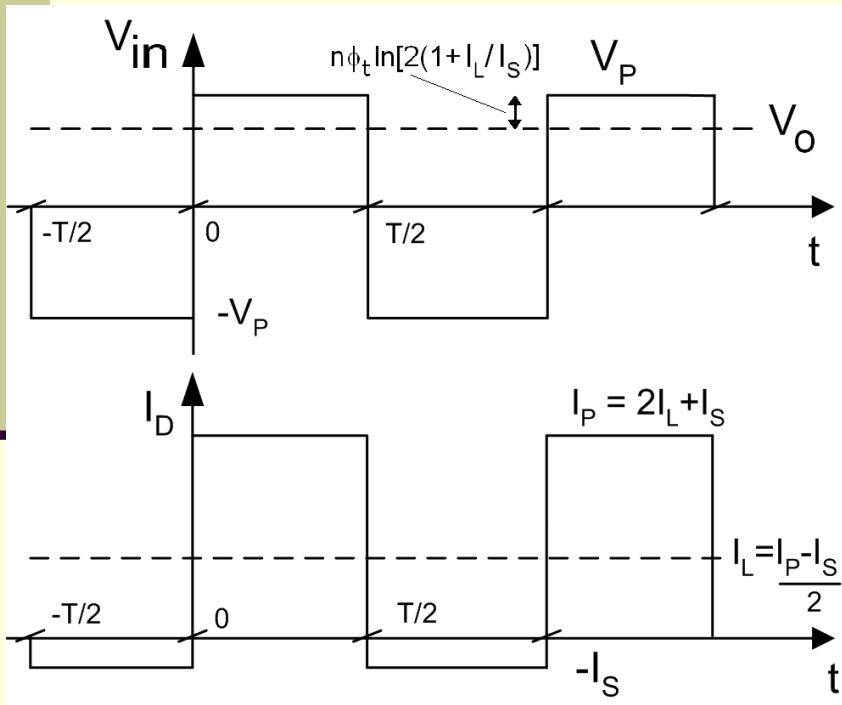


Steady-state analysis

$$\frac{I_S}{T} \left[\int_{-T/2}^0 \left(e^{\left(\frac{-V_P - V_o}{n\phi_t} \right)} - 1 \right) dt + \int_0^{T/2} \left(e^{\left(\frac{V_P - V_o}{n\phi_t} \right)} - 1 \right) dt \right] = I_L$$

Assumption: very low ripple $\rightarrow V_o \cong$ constant

$$\frac{V_o}{n\phi_t} = \ln \left[\frac{\cosh(V_P / n\phi_t)}{1 + I_L / I_S} \right]$$

ULV rectifier with DC load - 3

 



$$V_P > n\phi_t$$

→

$$V_o \cong V_P - n\phi_t \ln \left(\frac{I_P + I_0}{I_0} \right)$$



Diode "ON"
voltage drop

Waveforms for $V_P \gg n\phi_t$

 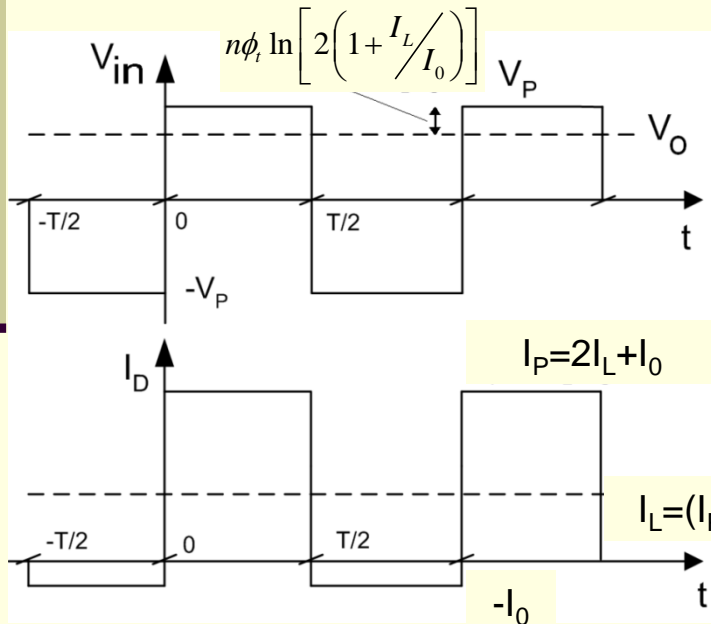


The voltage doubler
  
$$\text{PCE} = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{loss}}} \approx \frac{1 - \frac{n\phi_t}{V_P} \ln [2(1 + I_L/I_S)]}{(1 + I_S/I_L)}$$




Power conversion efficiency and load voltage of the voltage doubler versus normalized load current

What about diodes?

 



 
- Low (zero)-VT
- Standard-VT
- pn junction




Diode-connected zero-VT MOSFET
- high drive capability

AC/DC converter in 130 nm CMOS technology

24-stage rectifier

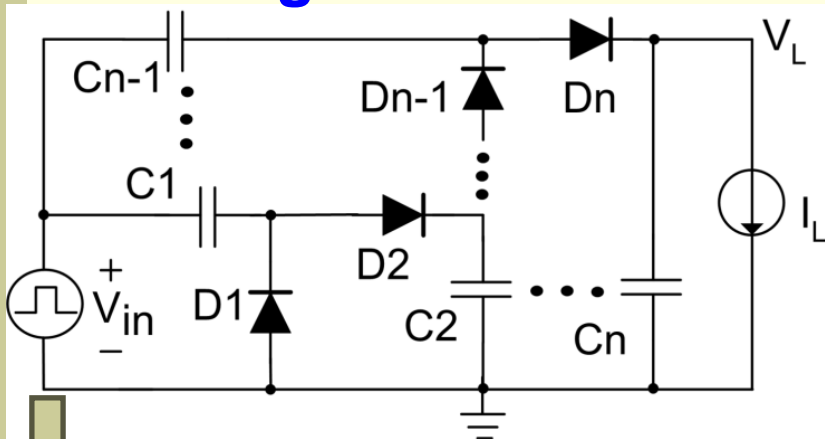  

Matching network

 


$$P_{AV} \cong 10 \mu\text{W} \quad \rightarrow \quad V_{in,peak} \cong 63 \text{ mV}$$


$$V_L \cong 1 \text{ V} \quad I_L \cong 1 \mu\text{A}$$

$$P_L = V_L I_L \cong 1 \mu\text{W}$$

$$\eta = \frac{P_L}{P_{AV}} \cong 10\%$$

 

Step-up converter

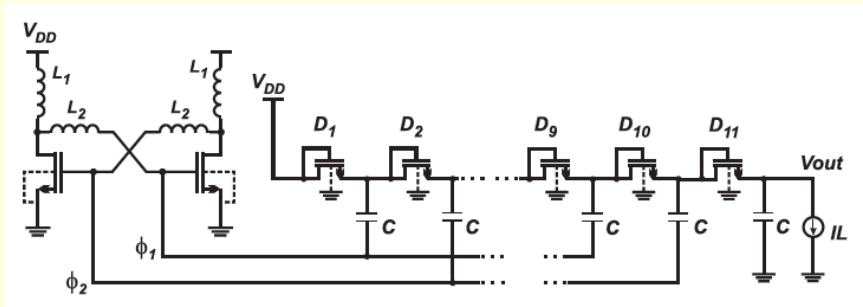


11-stage Dickson charge pump

Zero-VT transistor as a diode

$$W/L = 4.2\mu\text{m}/0.42\mu\text{m}$$

$$V_T = 76.5\text{ mV}$$

$$I_{\text{sat}} = 500\text{ nA}$$

 

IBM 0.13 μm technology

2-stage ESRO

Zero-VT transistor

$$W/L = 500\mu\text{m}/0.42\mu\text{m}$$




$$V_T = 63\text{ mV}$$

Integrated inductors

$$L_1 = 18.8\text{ nH}, L_2 = 66\text{ nH}$$

$$Q \approx 8$$

   Wire-bonded prototype designed with off-chip inductors



Output voltage of the DC/DC converter for increasing and decreasing input voltages

Design parameters and experimental results for the ULV step-up converters

		Fully integrated design	Design with off-chip inductors
Design parameters	Oscillator	$W/L = 500\mu\text{m}/0.42\mu\text{m}$ $g_{md} = 7.08 \text{ mA/V}$ $L_1 = 18.8 \text{ nH}, Q_{L1} = 8.7$ $L_2 = 66 \text{ nH}, Q_{L2} = 8.1$	$W/L = 2000\mu\text{m}/0.42\mu\text{m}$ $g_{md} = 19 \text{ mA/V}$ $L_1 = 220 \text{ nH}, Q_{L1} = 58$ $L_2 = 594 \text{ nH}, Q_{L2} = 67$
	Charge Pump	$W/L = 4.2 \mu\text{m}/0.42\mu\text{m}$ $I_S = 550 \text{ nA}; n = 1.4$ $C = 2 \text{ pF}$	$W/L = 4.2 \mu\text{m}/0.42\mu\text{m}$ $I_S = 550 \text{ nA}; n = 1.4$ $C = 2 \text{ pF}$
Experimental results	f_{osc}	550 MHz	50 MHz
	Active area	1 mm ²	20 mm ²
	Start-up at $I_L=10\text{nA}; V_I=1\text{V}$	$V_{DD,min} = 77.6 \text{ mV}$	$V_{DD,min} = 17.4 \text{ mV}$
	At $I_L=1\mu\text{A}; V_L=1\text{V}$	$V_{DD} = 86 \text{ mV}$	$V_{DD} = 23 \text{ mV}$
	At $V_{DD}=50\text{mV}; V_L=1\text{V}$	-	$I_L = 9.4 \mu\text{A}$ PCE = 9.4%
	At $V_{DD}=0.1\text{V}; V_L=1\text{V}$	$I_L = 3.3 \mu\text{A}$ PCE = 1 %	$I_L = 30 \mu\text{A}$ PCE = 6.2 %

References

- A. Jair Cardoso *et al.*; "Design of very low voltage CMOS rectifier circuits"; *IEEE Circuits and Systems for Medical and Environmental Applications Workshop (CASME 2010)*, Mérida, Dec. 2010.
- Adilson Jair Cardoso, Marcio Cherem Schneider, Carlos Galup-Montoro; "Teaching low voltage electronics: the case of the rectifier circuit", IEEE International Conference on Microelectronic Systems Education (MSE), San Diego, USA, June 2011.
- A. J. Cardoso *et al.* , "Analysis of the rectifier circuit valid down to its low-voltage limit", *IEEE Transactions on Circuits and Systems I: Regular Papers*, Jan. 2012.
- C. Galup-Montoro, M. C. Schneider, and M. B. Machado, "Ultra-low-voltage operation of CMOS analog circuits: amplifiers, oscillators, and rectifiers," *IEEE Trans. on Circuits and Syst. II, Exp. Briefs*, Dec. 2012.
- L . G. de Carli *et al.* , "Maximizing the Power Conversion Efficiency of Ultra-Low-Voltage CMOS Multi-Stage Rectifiers," *IEEE Transactions on Circuits and Systems I: Regular Papers*, April 2015.
- M. B. Machado *et al.* "Analysis and design of the Dickson charge pump for sub-50 mV energy harvesting," *Microelectronics Journal*, August 2019.
- F. Nornberg *et al.* "Design of Oscillator and Charge Pump for the Startup of Ultra-Low-Voltage Energy Harvesters" , 36th SBC/SBMicro/IEEE/ACM Symposium on Integrated Circuits and Systems Design (SBCCI), Rio de Janeiro, 2023.

Summary

Minimum V_{DD} for voltage gain = -1

Inverter

$$2\varphi_t \ln 2 = 36 \text{ mV at } 300 \text{ K}$$

Stacked Inverter

$$2\varphi_t \ln 1.77 = 29.8 \text{ mV at } 300 \text{ K}$$

Standard ST

$$2\varphi_t \ln \left(\frac{8 + \sqrt{73}}{9} \right) = 31.5 \text{ mV at } 300 \text{ K}$$

Minimum V_{DD} for hysteresis

Three-Inverter ST

$$2\varphi_t \ln 2 = 36 \text{ mV at } 300 \text{ K}$$

Standard ST

$$2\varphi_t \ln(2 + \sqrt{5}) = 75 \text{ mV at } 300 \text{ K}$$

z

NMOS Oscillators

Minimum V_{DD} for oscillation

Cross-coupled

$$\varphi_t \ln(1 + n)$$

Enhanced-Swing Cross-Coupled

$$\varphi_t \ln \left[1 + nL_1 / (L_1 + L_2) \right]$$

L_1 - load capacitance
 L_2 - coupling capacitance

Enhanced-Swing Colpitts

$$\varphi_t \ln \left[1 + C_2 / C_1 / (1 + L_1 / L_2) \right]$$

L_1, L_2 - drain and source capacitances