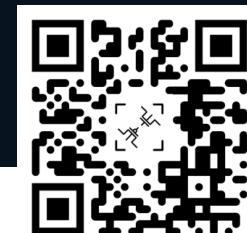




Design and simulation of analog/RF circuits with the single-piece ACM2 MOSFET model



"Scan me"



Carlos Galup-Montoro
Deni Germano Alves Neto
Sylvain Bourdel



Part 1

Advanced Compact MOSFET Model: ACM2



“Scan me”



Carlos Galup-Montoro

https://github.com/ACMmodel/MOSFET_model

Outline

- **Introduction: ACM timeline**
- **ACM2 model**
- **Long-channel: I_D and g_m/I_D models**
- **Long-channel: MOS basic amplifier design**


ACM timeline

- 1993 φ s model (SBMICRO, Campinas, Br)
- 1995 Long-channel charge-based model (SSE, Nov.)
- 1996 gm/ID model (SBMICRO, Aguas de Lindoia, Br)
- 1997 Unified current control model (ISCAS, Hong Kong)
- 1998 Most referenced ACM paper (JSSC, Oct.)
- 2000 ACM model in SMASH simulator (CICC, Orlando)
- 2021 4-parameter single-piece model (NorCAS, Oslo)
- 2023 ACM2 in VERILOG-AMS (NEWCAS, Edinburgh)

Outline

- Introduction: ACM timeline
- ACM2 model
- Long-channel: I_D and g_m/I_D models
- Long-channel: MOS basic amplifier design

The capacitive model of the MOSFET

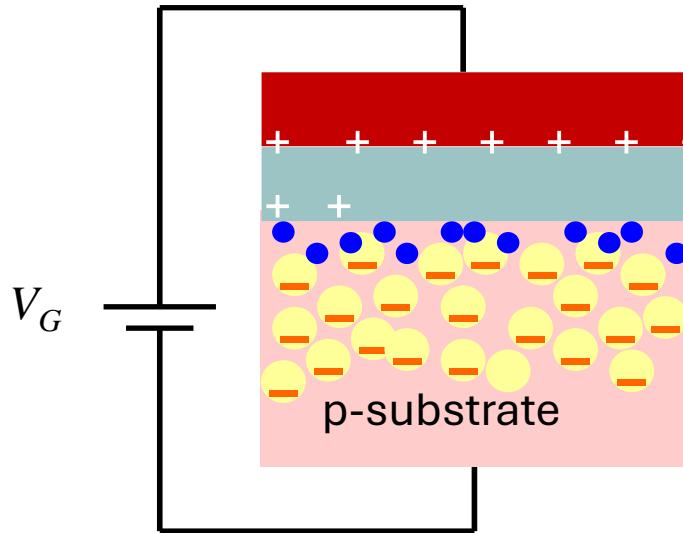


ϕ_s surface potential

C_{ox} oxide capacitance per unit area

C_b depletion capacitance per unit area

Q_i carrier charge density

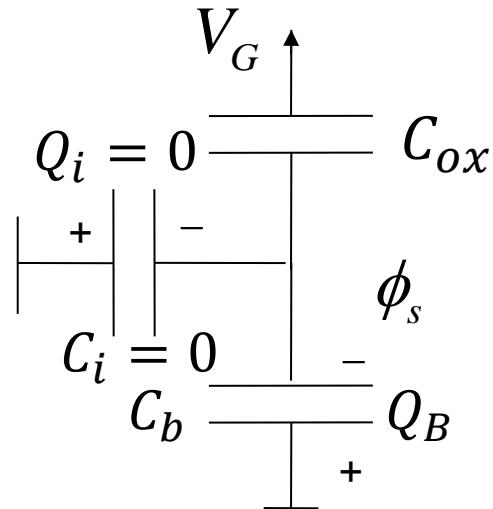

$$\frac{\Delta\phi_s}{\Delta V_G} = \frac{C_{ox}}{C_{ox} + C_b} = \frac{1}{n}$$

$$\phi_s = 2\phi_F + \frac{V_G - V_{T0}}{n} = 2\phi_F + V_P$$

Drain current model: main simplifications


First approximation ACM2

$$dQ_I = nC_{ox}d\phi_s$$

Second approximation ACM2

$$I_D = \mu W \left(-Q_I \frac{d\phi_s}{dy} + \phi_t \frac{dQ_I}{dy} \right)$$

↑
drift ↑
Diffusion

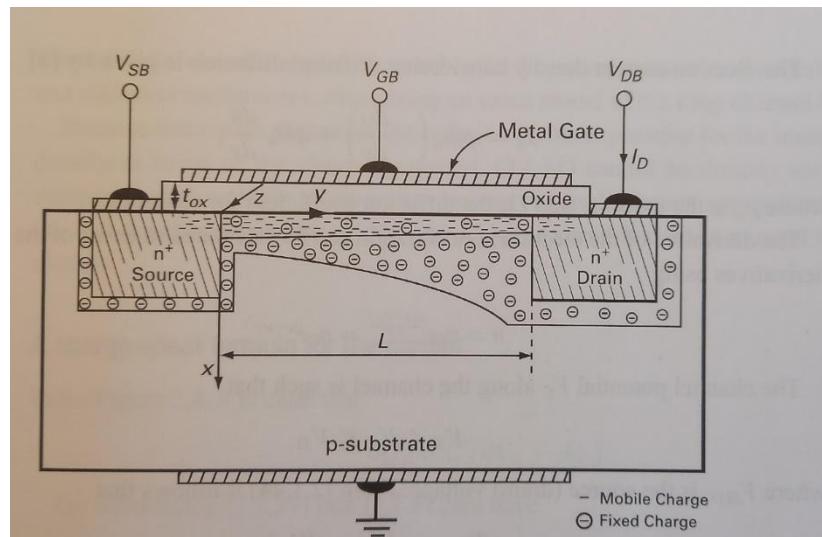


Q_I carrier charge density

W transistor width

μ carrier mobility

ϕ_t thermal voltage
26 mV @ 300K

Velocity saturation

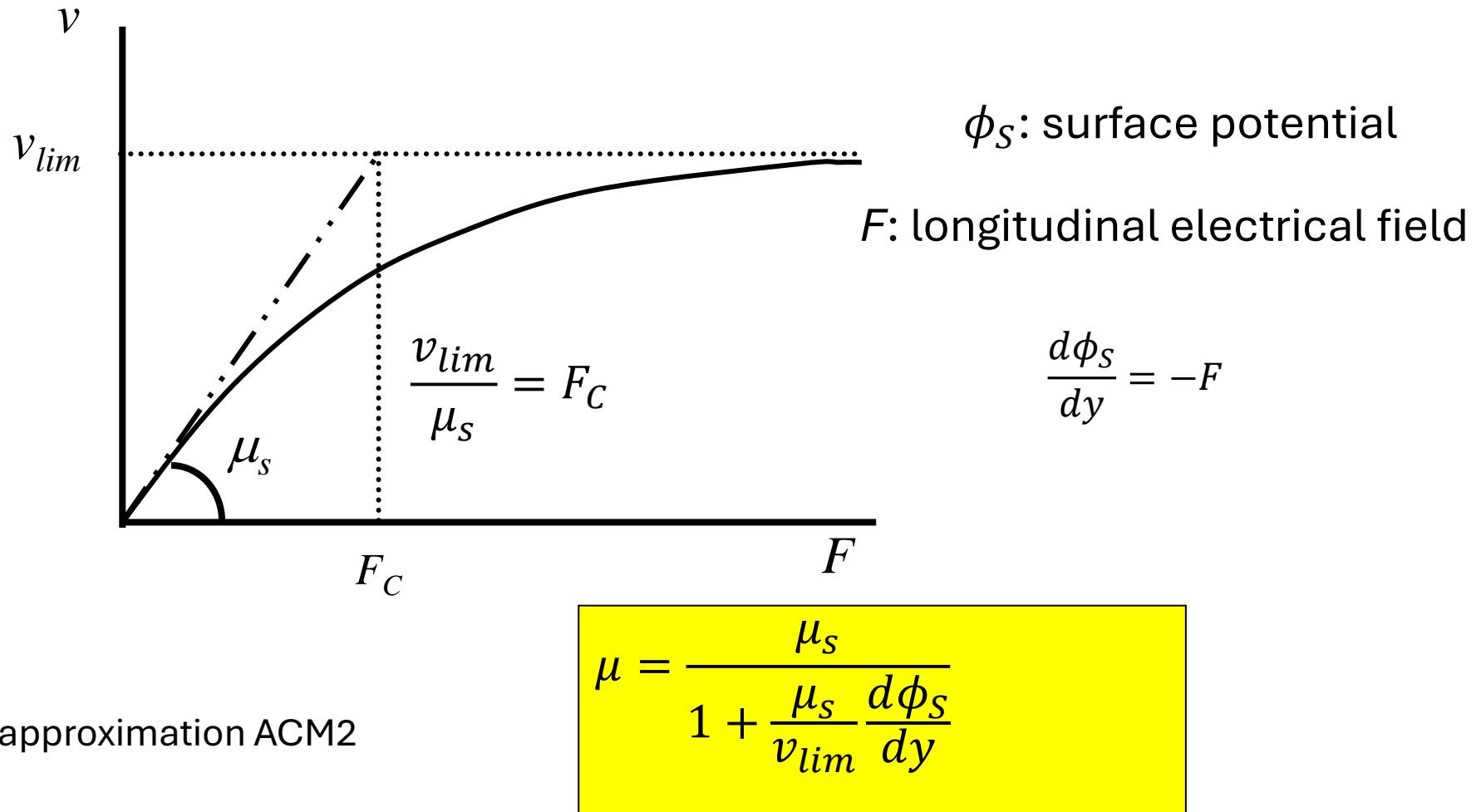

Allows analytical integration for I_D

ACM2 current law

From the 3 approximations normalized current vs. normalized charge densities at source and drain

$$i_D = \frac{(q_S + q_D + 2)}{1 + \zeta(q_S - q_D)} (q_S - q_D)$$

$$i_D = I_D / I_S$$

$$I_S = \frac{W}{L} \mu_s n C_{ox} \frac{\phi_t^2}{2}$$

normalization (specific) current

$$q_{S(D)} = Q_{S(D)} / (-n C_{ox} \phi_t)$$

$-n C_{ox} \phi_t$ thermal charge


$$SI : q_{S(D)} \gg 1 \quad WI : q_{S(D)} \ll 1$$

Short-channel parameter ζ :

$$\zeta = \frac{(\mu_s \phi_t / L)}{v_{lim}}$$

ratio of diffusion-related velocity to saturation velocity

Physics-based saturation

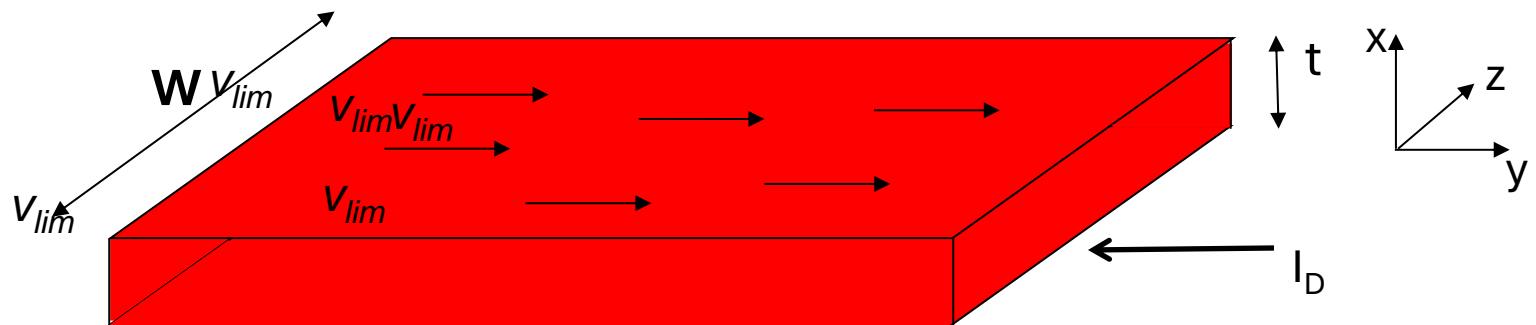

Saturation current due to saturation velocity of the carriers

$$I_{Dsat} = -W Q_{Dsat} v_{lim}$$

Q_{Dsat} is the saturation inversion charge per unit area

or, using normalized variables

$$i_{Dsat} = \frac{2}{\zeta} q_{dsat}$$

“Carrier velocity approaches v_{sat} , but never reaches v_{sat} ”

Y.Taur TED March 2019

Physics-based saturation: design model

$$i_{Dsat} = \frac{2}{\zeta} q_{dsat}$$

$$i_{Dsat} = \frac{(q_s + q_{Dsat} + 2)}{1 + \zeta(q_s - q_{Dsat})} (q_s - q_{Dsat})$$

$$q_{Dsat} = q_s + 1 + \frac{1}{\zeta} - \sqrt{\left(1 + \frac{1}{\zeta}\right)^2 + \frac{2q_s}{\zeta}}$$

or equivalently


$$q_s = \sqrt{1 + \frac{2}{\zeta} q_{dsat}} - 1 + q_{dsat}$$

*Unified Charge Control Model including
the effect of velocity saturation*


$$\frac{V_P - V_{SB}}{\phi_t} = q_s - 1 + \ln q_s$$

$$\frac{V_{DS}}{\phi_t} = q_s - q_D + \ln \frac{q_s - q_{Dsat}}{q_D - q_{Dsat}}$$

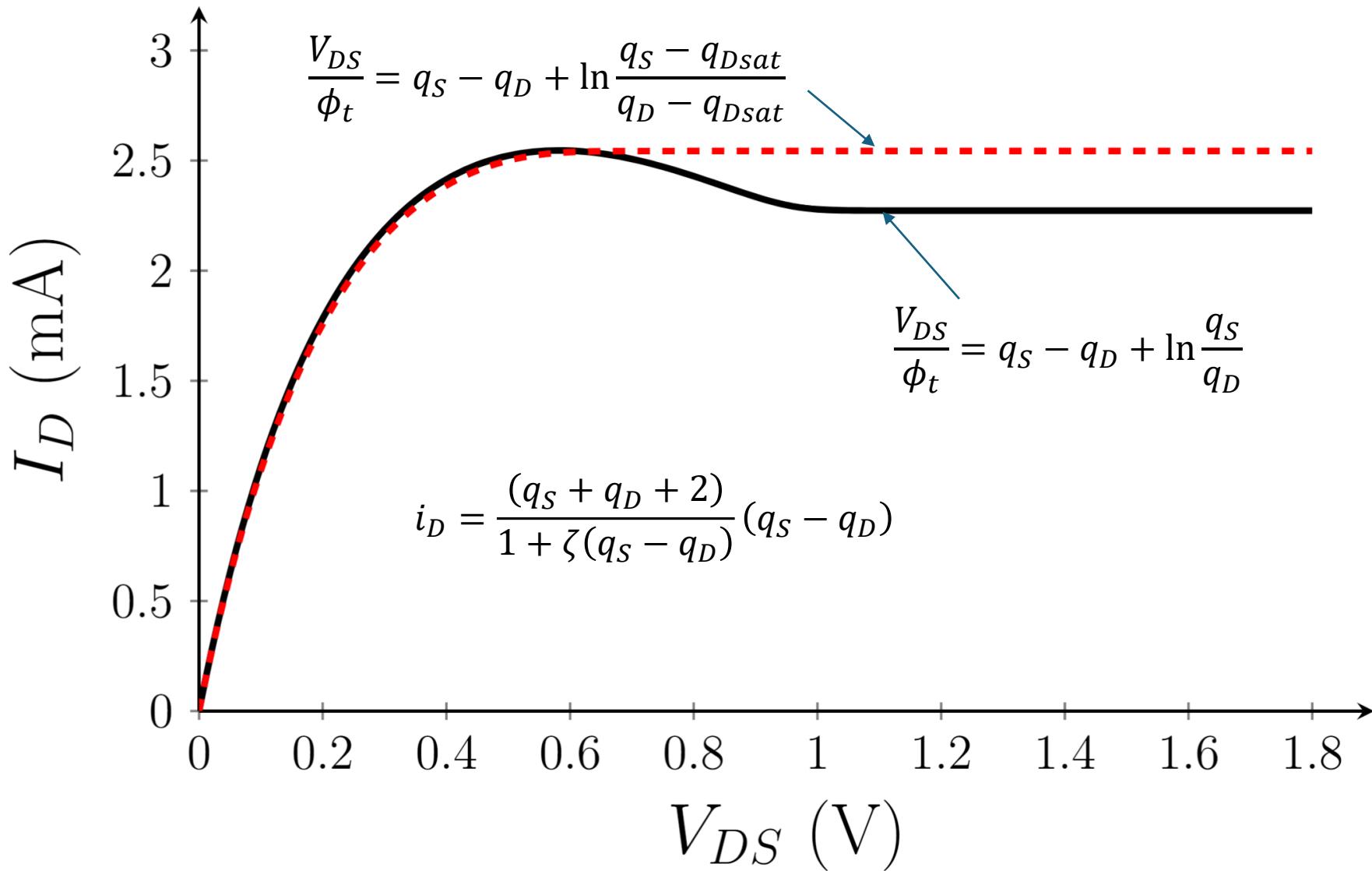Effect of the maximum of $i_D(q_D)$ on the output characteristic $i_D(v_D)$



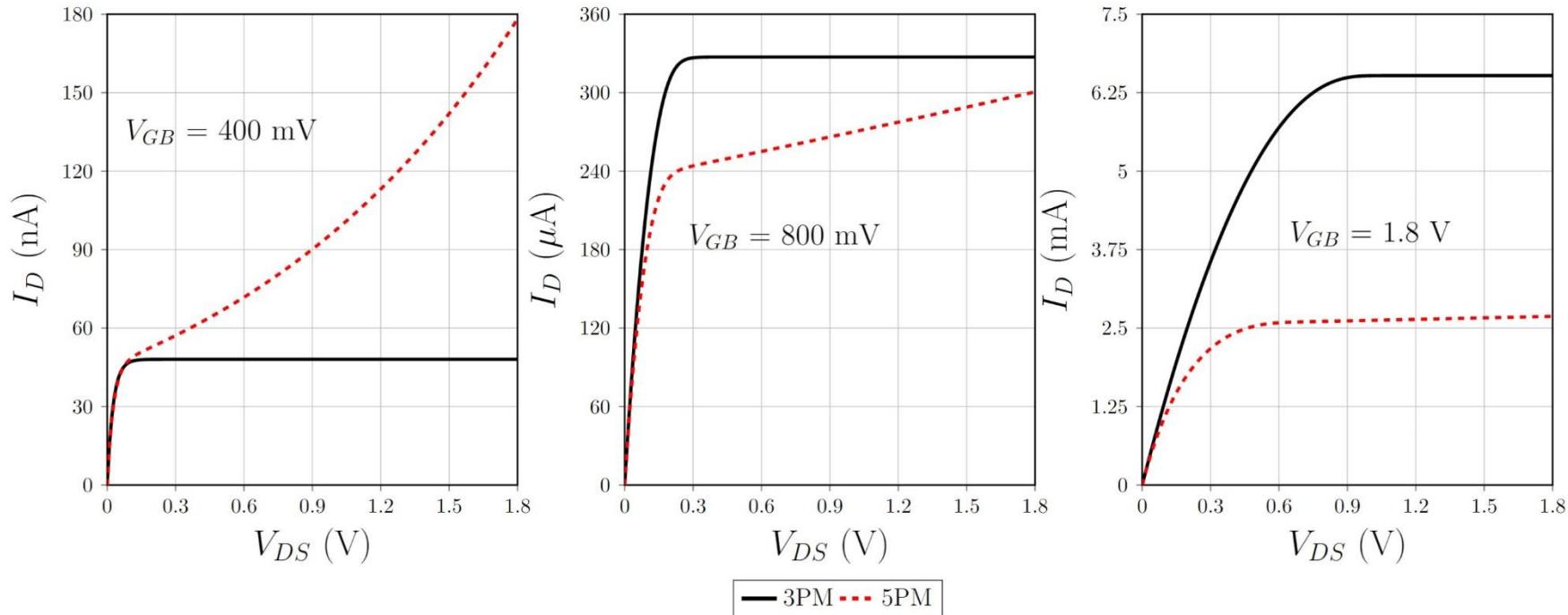Output characteristics including DIBL and v_{sat}



$$DIBL \text{ model: } V_T = V_{T0} - \sigma(V_{SB} + V_{DB})$$

Transistor	W/L ($\mu\text{m}/\mu\text{m}$)	V_{T0} (mV)	I_S (μA)	n	σ	ζ
NMOS2V	5/0.18	528	5.52	1.37	0.025	0.056

Outline

- Introduction: ACM timeline
- ACM2 model
- Long-channel: I_D and g_m/I_D models
- Long-channel: MOS basic amplifier design

Unified Current Control Model (UICM)-I

$$I_D = I_S[(q_S^2 + 2q_S) - (q_D^2 + 2q_D)] \quad (\text{A})$$

(A) can also be written as

$$I_D = I_F - I_R = I_S[i_f - i_r] \quad (\text{B})$$

I_F, I_R : forward and reverse currents

$i_{f(r)} = q_{S(D)}^2 + 2q_{S(D)}$: forward (reverse) inversion coefficients

Unified Current Control Model (UICM)-II

$$i_{f(r)} = q_{S(D)}^2 + 2q_{S(D)}$$

$$q_{S(D)} = \sqrt{1 + i_{f(r)}} - 1$$

Normalized UCCM

$$\frac{V_P - V_{S(D)B}}{\varphi_t} = q_{S(D)} - 1 + \ln q_{S(D)}$$

Normalized UICM

$$\frac{V_P - V_{S(D)B}}{\varphi_t} = \sqrt{1 + i_{f(r)}} - 2 + \ln \left(\sqrt{1 + i_{f(r)}} - 1 \right)$$

$$\frac{V_{DS}}{\varphi_t} = q_S - q_D + \ln \frac{q_S}{q_D} = \sqrt{1 + i_f} - \sqrt{1 + i_r} + \ln \left(\frac{\sqrt{1 + i_f} - 1}{\sqrt{1 + i_r} - 1} \right)$$

$$g_m/I_D$$

$$g_{ms(d)} = \frac{2I_S}{\phi_t} \left(\sqrt{1 + i_{f(r)}} - 1 \right) = \frac{W}{L} \mu C_{ox} n \phi_t \left(\sqrt{1 + i_{f(r)}} - 1 \right)$$

$$g_m = \frac{g_{ms} - g_{md}}{n}$$

$$\frac{g_m}{I_D} = \frac{2}{n \phi_t (\sqrt{1 + i_f} + \sqrt{1 + i_r})}$$

For $V_{DS}/\phi_t \ll 1$ we have $i_f \approx i_r$

$$\frac{g_m}{I_D} \cong \frac{1}{n \phi_t \sqrt{1 + i_f}}$$


In saturation $i_f \gg i_r$

$$\frac{g_m}{I_D} \cong \frac{2}{n \phi_t (\sqrt{1 + i_f} + 1)}$$



Outline

- Introduction: ACM timeline
- ACM2 model
- Long-channel: I_D and g_m/I_D models
- Long-channel: MOS basic amplifier design

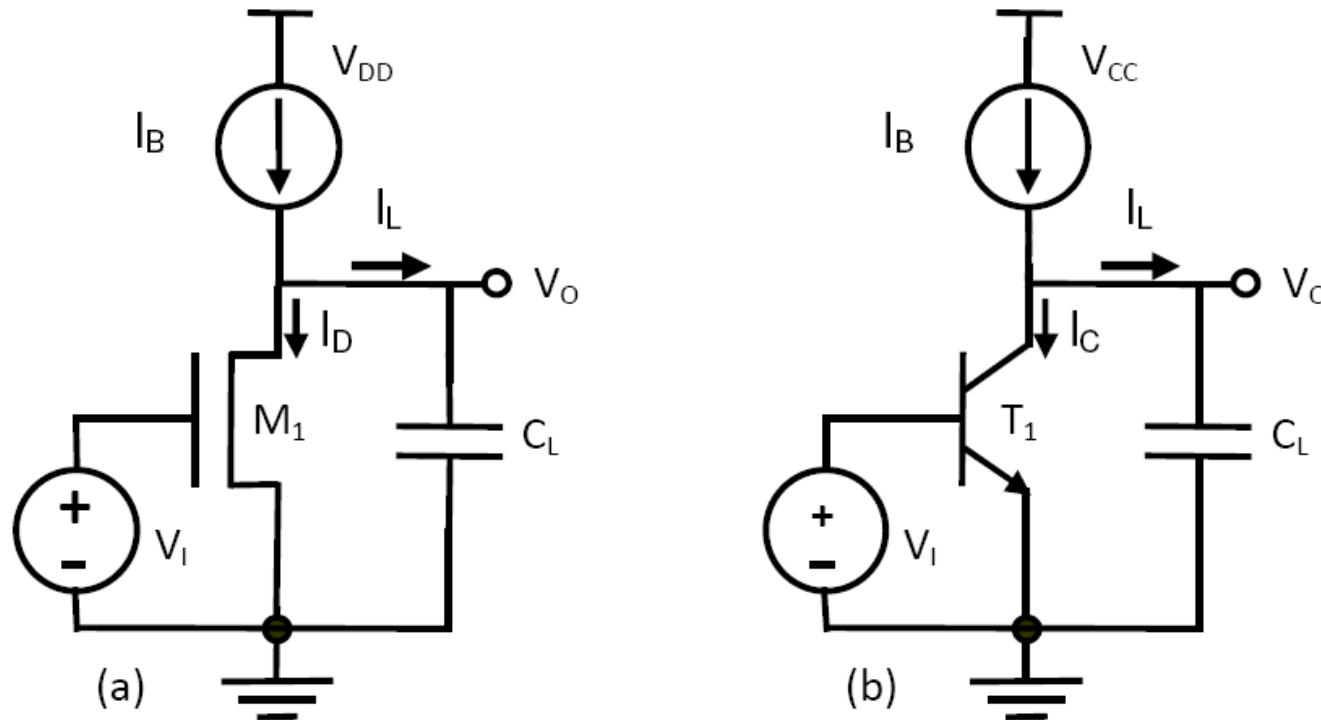Intrinsic gain stages: common-source and common-emitter amplifiers



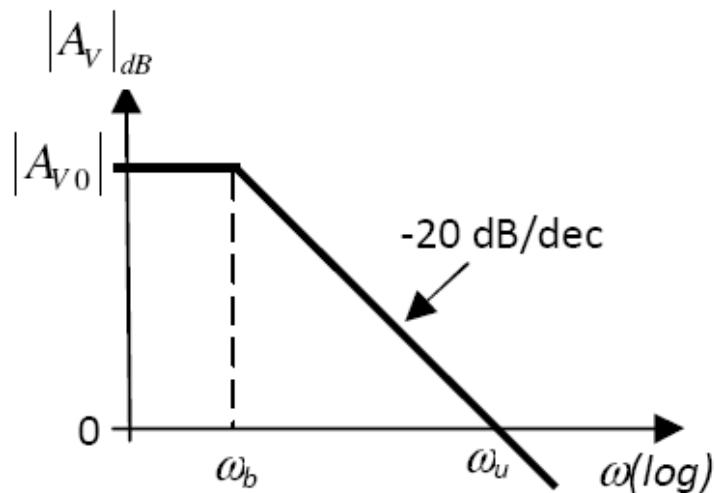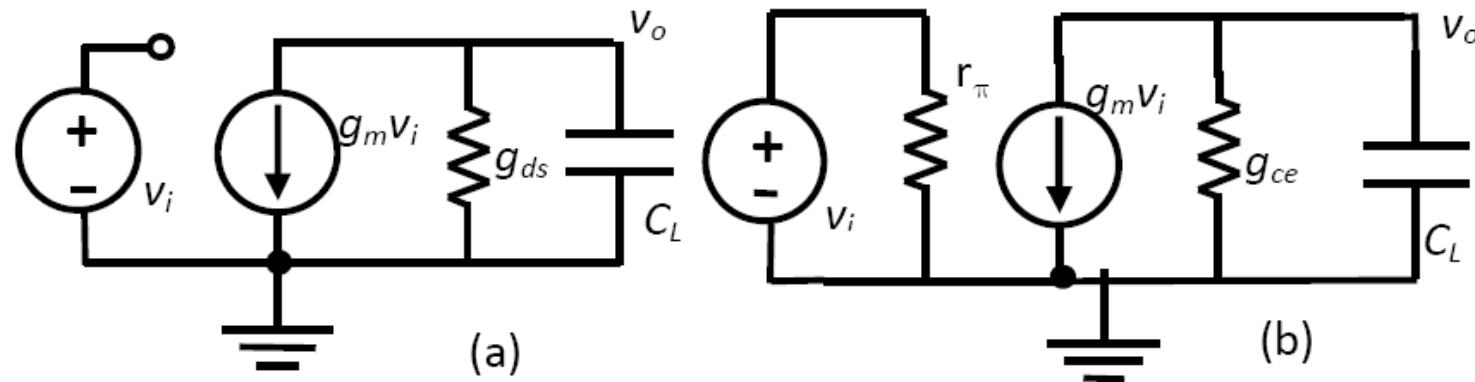Small-signal circuit and frequency response of the CS and CE amplifiers



$$v_o \cong -\frac{g_m}{j\omega C_L} v_i; \quad \omega \gg \omega_b$$

$$\omega_u = \frac{g_m}{C_L}$$

Design of the CE and CS amplifiers

$$|A_v(\omega_u)| = 1$$

$$g_m = \omega_u C_L = 2\pi \cdot GB \cdot C_L$$


BJT in the direct active region

$$I_C = I_S e^{V_{BE}/\phi_t} \quad \rightarrow \quad I_C = g_m \phi_t = 2\pi \cdot GB \cdot C_L \cdot \phi_t$$

MOSFET in saturation

$$I_D = n g_m \phi_t \frac{(\sqrt{1 + i_f} + 1)}{2} = n g_m \phi_t \left[1 + \frac{g_m}{2\mu C_{ox} \phi_t (W/L)} \right]$$

Aspect ratio vs. current excess in MOSFET design

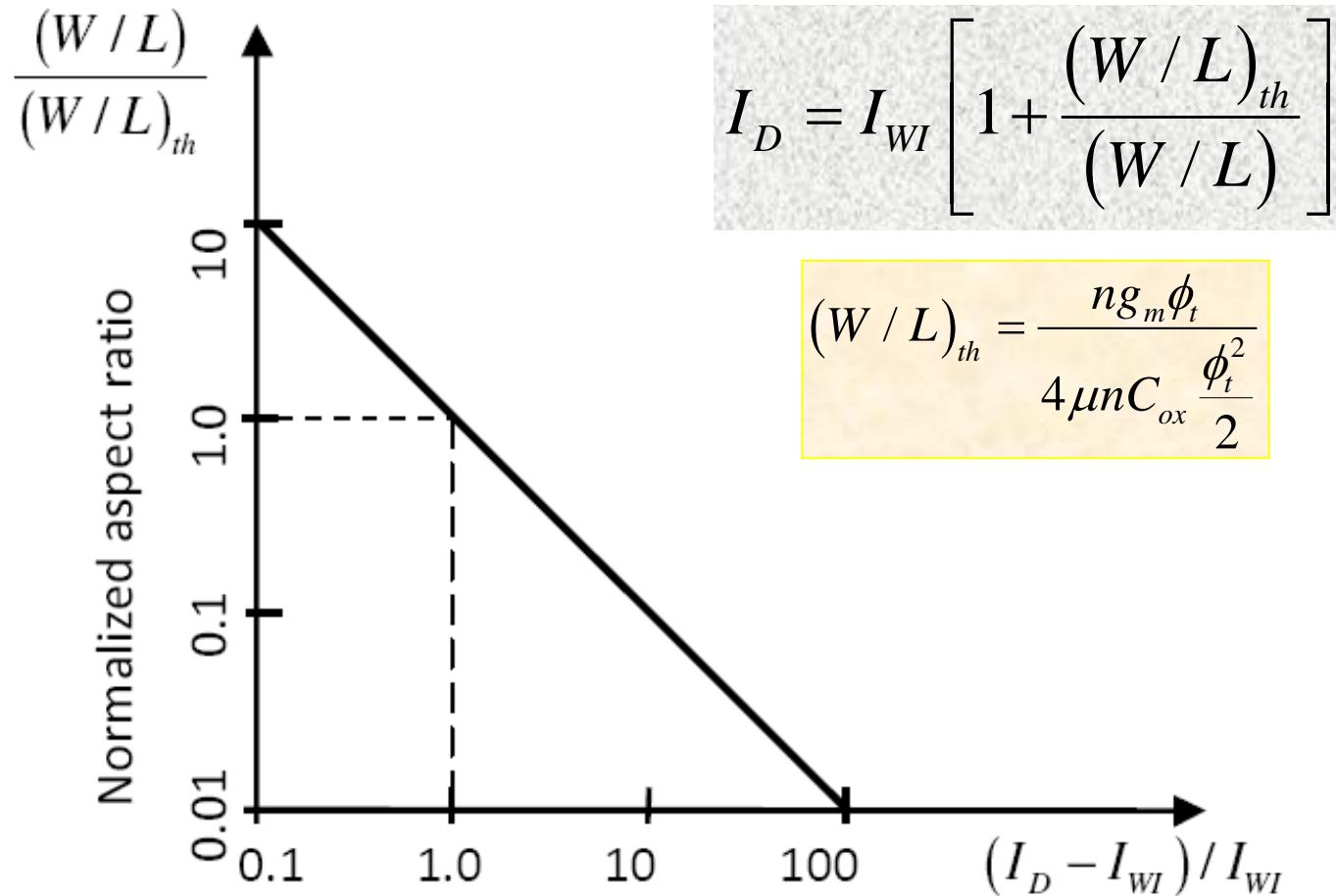



Part 2

Advanced Compact MOSFET Model: Parameter extraction



“Scan me”



Deni Germano Alves Neto

https://github.com/ACMmodel/MOSFET_model

About me

- Universidade Federal de Santa Catarina – UFSC - Brazil
- Undergrad and Masters in IC design - 2022
 - Subject : Ultra-Low-Voltage IC circuits $V_{DD} < 100 \text{ mV}$
 - Dissertation: Ultra-Low-Voltage Standard Cell Library
 - ACM (4PM) for low voltage circuits
- First contact with open-source IC design :
 - Chipathon - SSCS 2021 :)
 - Analog-front-end for Biosignals – AFEbio
- Start PhD in 2023 : MOSFET Modeling
- Joint PhD between UFSC and Université Grenoble Alpes (Currently based)
 - Chipathon-SSCS & UNIC-CASS 2023/2024 – Analog IC design
 - Live demonstration of the ACM2 at ISCAS 2024 with the open-source tools (XSCHEM+Ngspice)



Outline

- ACM2 – Transconductances in Saturation
- ACM2 - Parameter Extraction
 - VT0, IS and n
 - Sigma
 - Zeta
- Introduction to Qucs-S
 - Automatic parameter extraction

ACM2: A simple 5-DC-parameter MOSFET model

$$V_P = \frac{V_{GB} - V_{T0} + \sigma(V_{DB} + V_{SB})}{n}$$

$$\frac{V_P - V_{SB}}{\phi_t} = q_s - 1 + \ln(q_s)$$

$$q_{dsat} = q_s + 1 + \frac{1}{\zeta} - \sqrt{\left(1 + \frac{1}{\zeta}\right)^2 + \frac{2q_s}{\zeta}}$$

$$\frac{V_{DS}}{\phi_t} = q_s - q_d + \ln\left(\frac{q_s - q_{dsat}}{q_d - q_{dsat}}\right)$$

$$I_D = I_s \frac{(q_s + q_d + 2)}{1 + \zeta(q_s - q_d)} (q_s - q_d)$$

Specific current
 I_s (W,L)

Threshold voltage
 V_{T0} (W,L)

Slope factor
 n (W,L)

DIBL factor
 σ (W,L)

V_{sat} effect
 ζ (W,L)

Used to calculate q_s

Used to calculate q_d

5PM-ACM2 : Transconductances in saturation

$$I_{Dsat} = \frac{2I_S}{\zeta} q_{dsat} \quad \text{where} \quad \left\{ \begin{array}{l} I_S = \mu C_{ox} n \frac{\phi_t^2 W}{2 L} = I_{SH} \frac{W}{L} \\ q_{dsat} = q_s + 1 + \frac{1}{\zeta} - \sqrt{\left(1 + \frac{1}{\zeta}\right)^2 + \frac{2q_s}{\zeta}} \end{array} \right.$$

Definitions



$$\left[\begin{array}{l} g_m \triangleq \frac{\partial I_{Dsat}}{\partial V_G} \quad g_d \triangleq \frac{\partial I_{Dsat}}{\partial V_D} \quad g_{msat3} \triangleq \frac{\partial^3 I_{Dsat}}{\partial V_G^3} \end{array} \right]$$

Transconductances in terms of q_s :





$$g_{msat} = \frac{2I_S}{n\phi_t} \frac{q_s}{1 + \zeta(q_s + 1)} \quad g_{dsat} = \sigma \frac{2I_S}{n\phi_t} \frac{q_s}{1 + \zeta(q_s + 1)} \quad \rightarrow \quad g_{dsat} = \sigma g_{msat}$$

$$g_{msat3} = \frac{16I_S}{(n\phi_t)^3} \frac{q_s}{(q_s + 1)^3} \frac{2 - 2\zeta q_s - 3\zeta q_s^2}{(\zeta q_s + 2)^4}$$

5PM-ACM2 : Transconductance gm

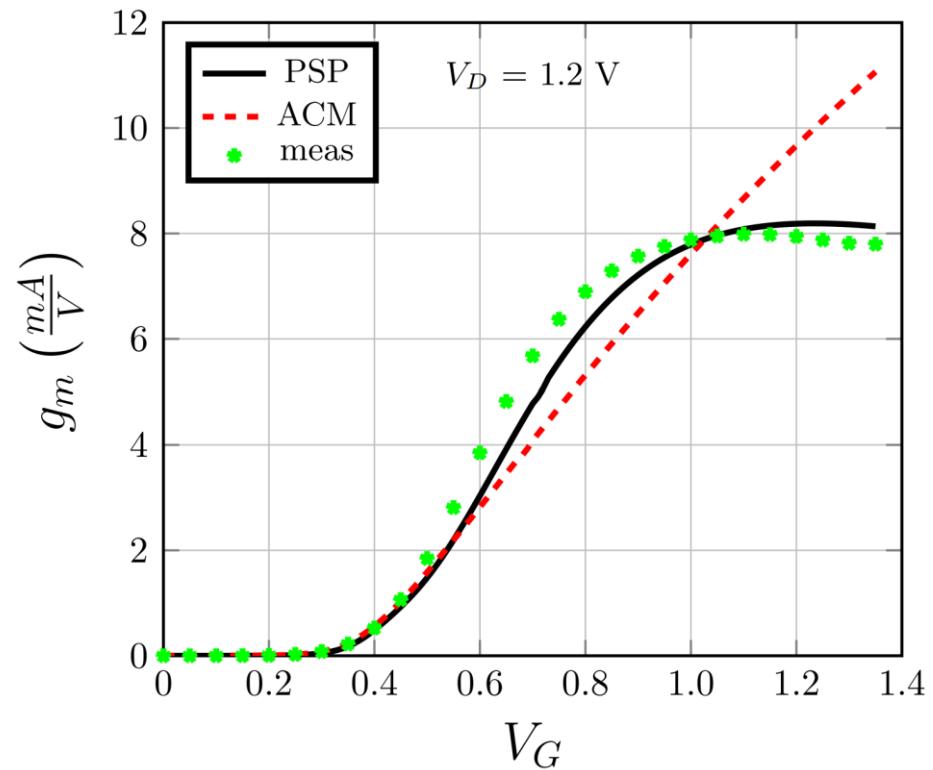
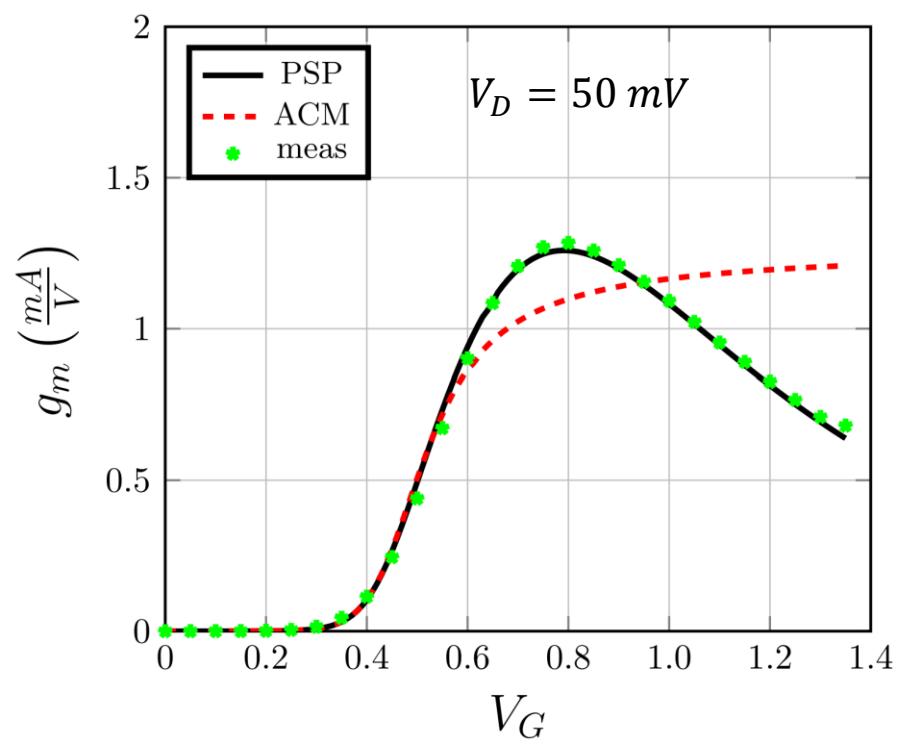


5PM-ACM2 : gds -Transconductances

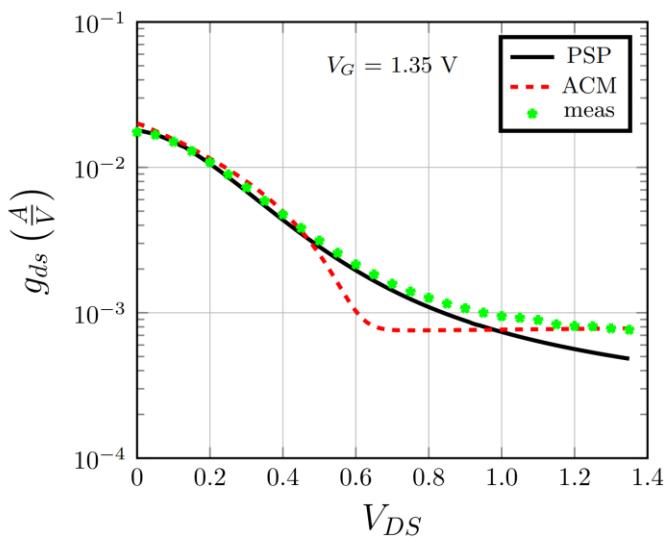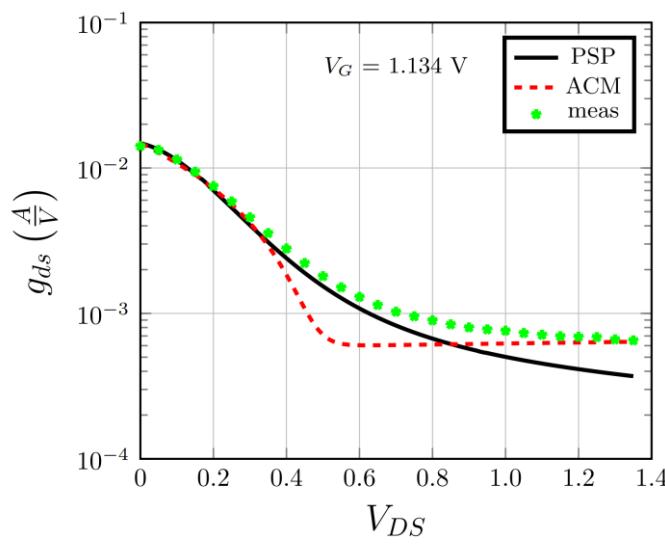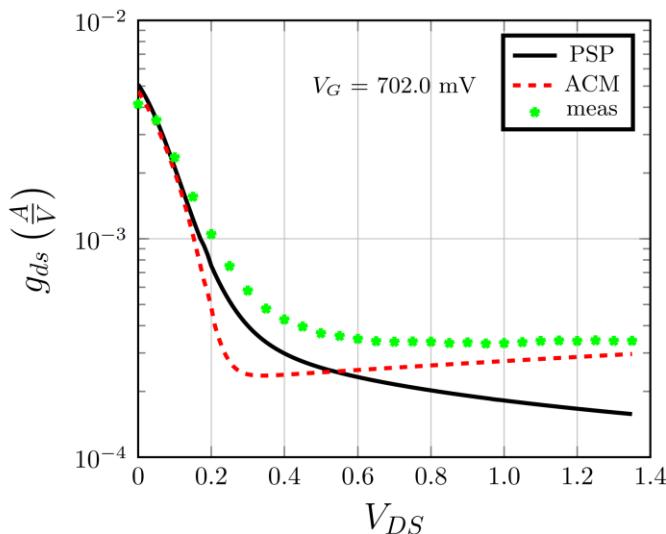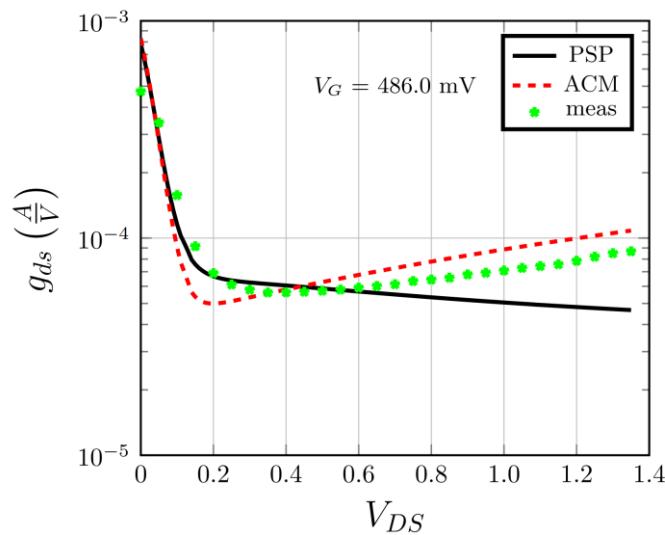

5PM-ACM2 : Transconductance gmsat3

$$V_D = 1.8 \text{ V}$$

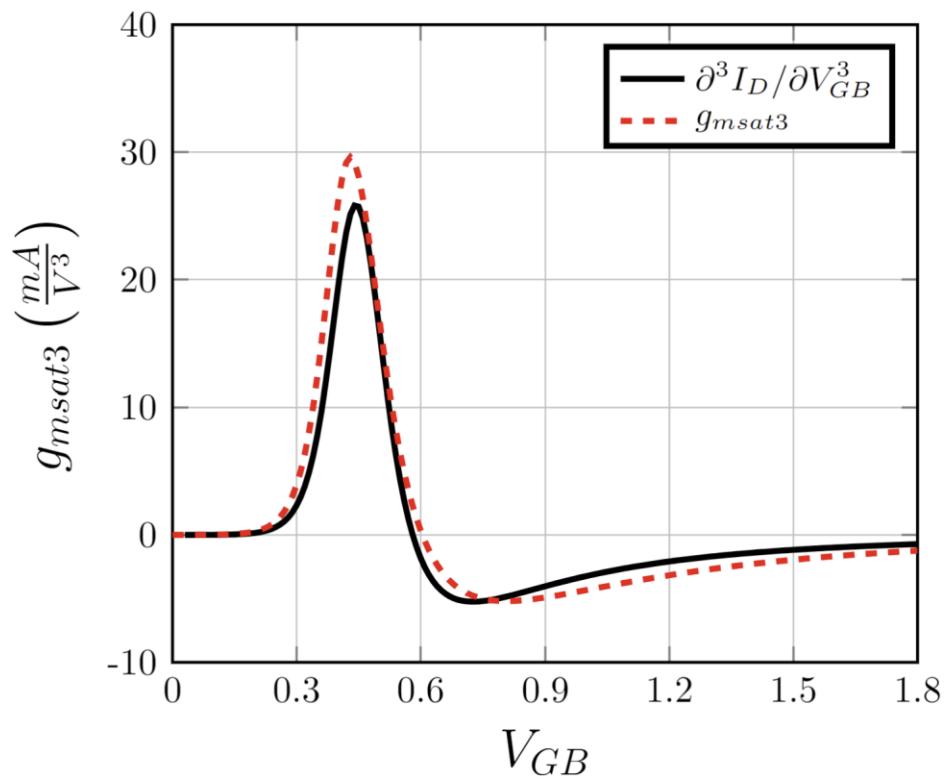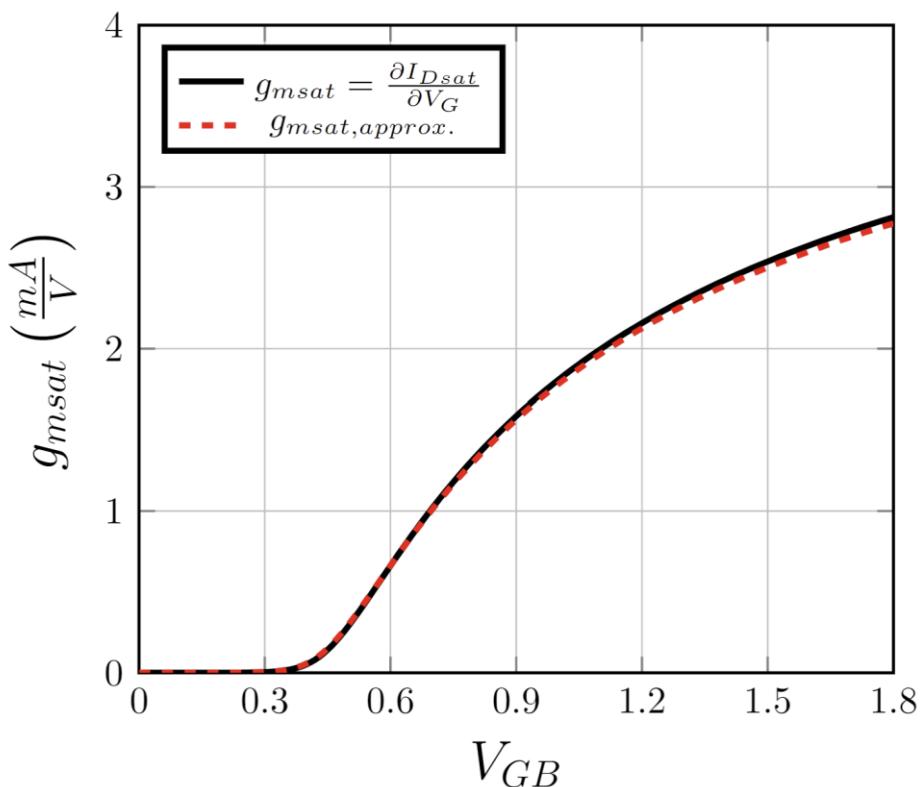

Outline

- ACM2 – Transconductances in Saturation
- ACM2 - Parameter Extraction
 - VT0, IS and n
 - Sigma
 - Zeta
- Introduction to Qucs-S
 - Automatic parameter extraction

3PM-ACM model in a nutshell

$$I_D = I_S [i_f - i_r] \quad \text{where} \quad I_S = \mu C_{ox} n \frac{\phi_t^2}{2} \frac{W}{L} = I_{SH} \frac{W}{L}$$

$$\frac{V_P - V_{S(D)B}}{\phi_t} = \sqrt{1 + i_{f(r)}} - 2 + \ln \left(\sqrt{1 + i_{f(r)}} - 1 \right) \quad V_P \cong \frac{V_{GB} - V_{T0}}{n}$$

If we choose $i_f = 3$ \rightarrow $RHS = 0$ \rightarrow $V_{GB} = V_{T0}$

$$\frac{V_{DS}}{\phi_t} = \sqrt{1 + i_f} - \sqrt{1 + i_r} + \ln \left(\frac{\sqrt{1 + i_f} - 1}{\sqrt{1 + i_r} - 1} \right)$$

$$g_{ms(d)} = \frac{2I_S}{\phi_t} \left(\sqrt{1 + i_{f(r)}} - 1 \right) \rightarrow \frac{W}{L} = \frac{g_{ms(d)} \phi_t}{2I_{SH} (\sqrt{1 + i_{f(r)}} - 1)}$$

$$g_m = \frac{g_{ms} - g_{md}}{n}$$

$$\frac{g_m}{I_D} = \frac{d(\ln I_D)}{dV_G} = \frac{2}{n \phi_t (\sqrt{1 + i_f} + \sqrt{1 + i_r})}$$

DC eqs

Small-signal
eqs

I_S , V_{TO} and n extraction

The g_m/I_D method

Let us choose: $V_{DS} = \phi_t/2$ and $i_f = 3$

$$\rightarrow \frac{V_{DS}}{\phi_t} = \sqrt{1 + i_f} - \sqrt{1 + i_r} + \ln\left(\frac{\sqrt{1 + i_f} - 1}{\sqrt{1 + i_r} - 1}\right)$$



Thus : $i_r = 2.12$

$$\rightarrow \frac{g_m}{I_D} = \frac{d(\ln I_D)}{dV_G} = \frac{2}{n\phi_t(\sqrt{1 + i_f} + \sqrt{1 + i_r})}$$

$$\frac{g_m}{I_D} = \frac{0.531}{n\phi_t} = 0.531 \left(\frac{g_m}{I_D} \right)_{max}$$

$$\rightarrow I_D = I_S(i_f - i_r)$$

$$I_D = (3 - 2.12) I_S = 0.88 I_S$$

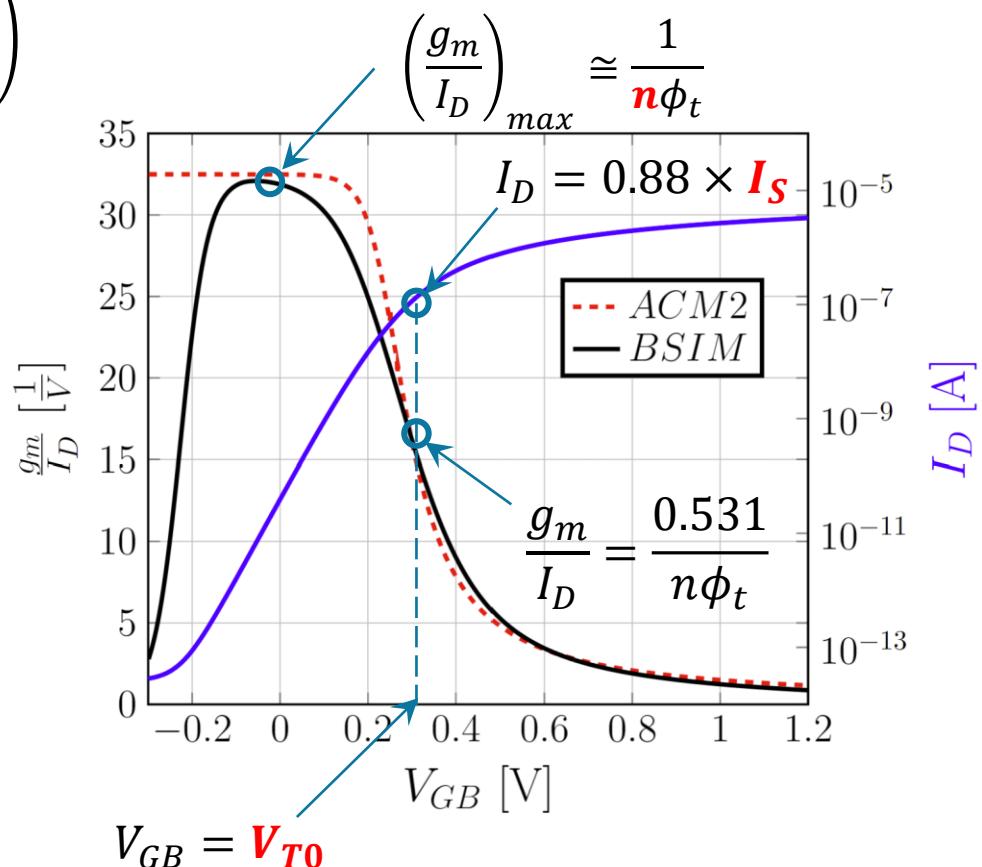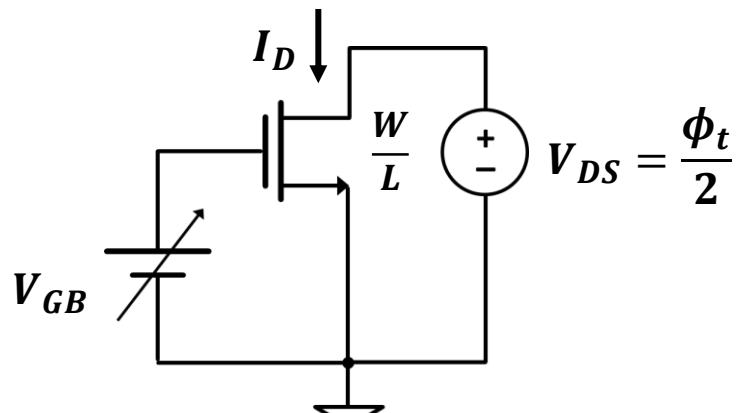


Outline



- ACM2 – Transconductances in Saturation
- ACM2 - Parameter Extraction
 - VT0, IS and n
 - Sigma
 - Zeta
- Introduction to Qucs-S
 - Automatic parameter extraction

Extraction of σ

Common-Source Intrinsic-Gain method

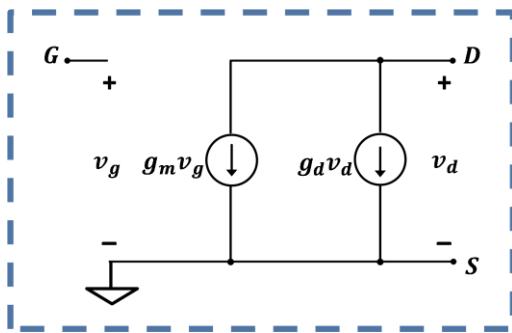
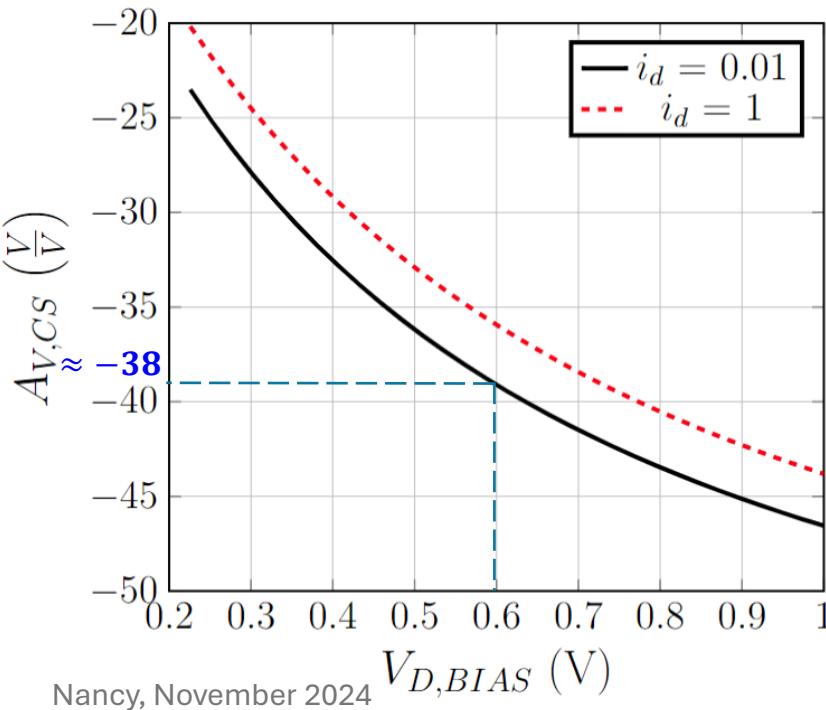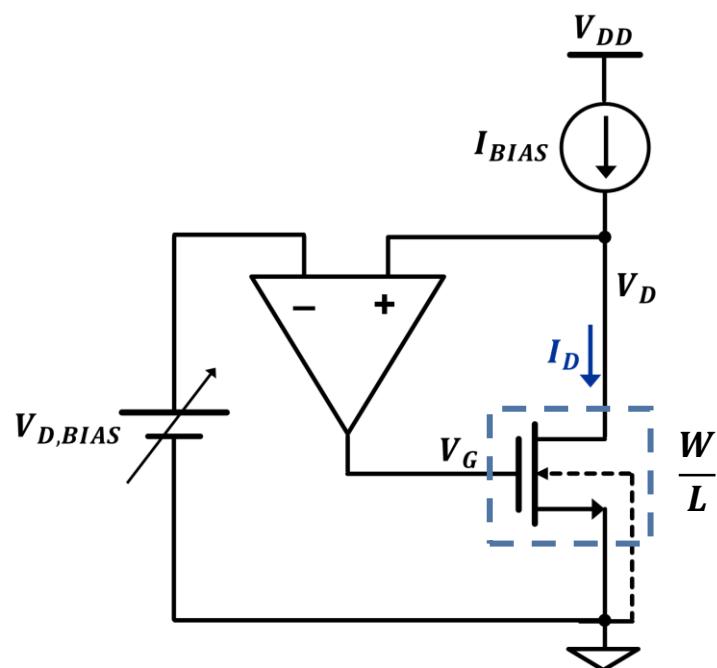
$$A_{V,CS} = \frac{\Delta v_D}{\Delta v_G} = -\frac{g_m}{g_d} = \frac{\frac{\partial I_{Dsat}}{\partial V_G}}{\frac{\partial I_{Dsat}}{\partial V_D}} = -\frac{\frac{2I_S}{n\phi_t} \frac{q_s}{1 + \zeta(q_s + 1)}}{\sigma \frac{2I_S}{n\phi_t} \frac{q_s}{1 + \zeta(q_s + 1)}} = -\frac{1}{\sigma}$$



$$A_{V,CS} = -\frac{1}{\sigma}$$

$$\sigma = -\frac{1}{(-38)}$$

$$\sigma = 0.026$$

Outline

- ACM2 – Transconductances in Saturation
- ACM2 - Parameter Extraction
 - VT0, IS and n
 - Sigma
 - Zeta
- Introduction to Qucs-S
 - Automatic parameter extraction


ζ extraction

- q_s calculated using parameters (V_{T0} , n , σ) and UCCM.



$$V_P = \frac{V_{GB} - V_{T0} + \sigma(V_{DB} + V_{SB})}{n}$$
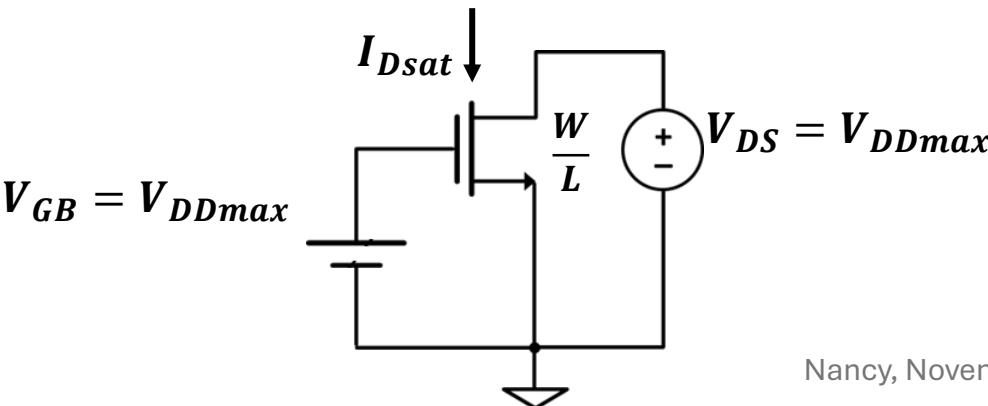
$$\frac{V_P - V_{S(D)B}}{\phi_t} = q_s - 1 + \ln(q_s)$$



$$i_{dsat} = \frac{2}{\zeta} q_{dsat}$$


$$q_s = \sqrt{1 + \frac{2}{\zeta} q_{dsat}} - 1 + q_{dsat}$$

$$\zeta = \frac{2(q_s + 1 - \sqrt{1 + i_{dsat}})}{i_{dsat}}$$

- Measure

$$I_{Dsat} = I_D(V_G = V_D = V_{DDmax} \text{ and } V_S = V_B)$$

$$i_{dsat} = I_{Dsat}/I_S.$$


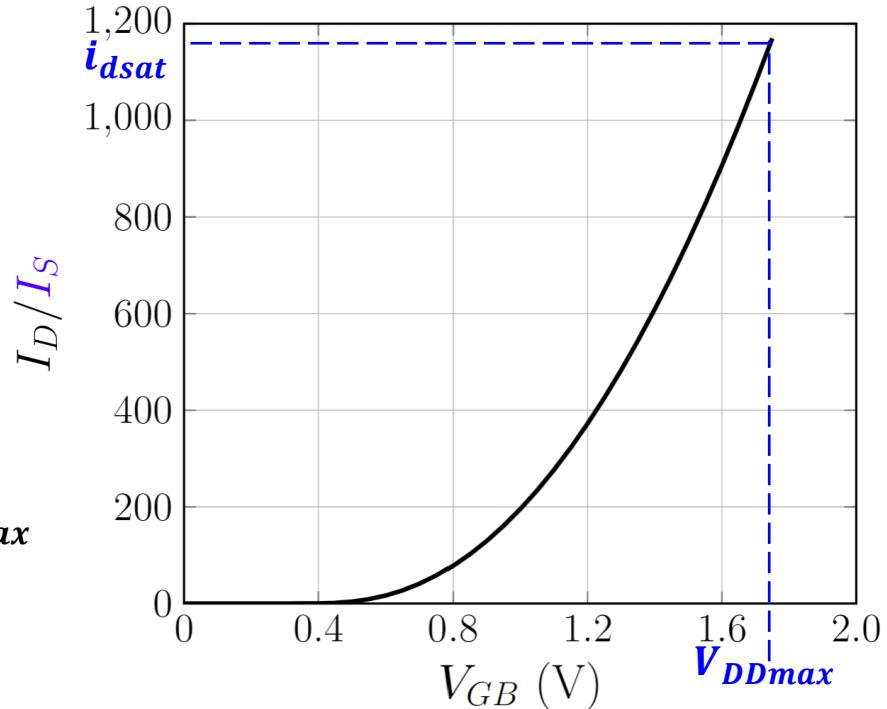


Outline

- ACM2 – Transconductances in Saturation
- ACM2 - Parameter Extraction
 - VT0, IS and n
 - Sigma
 - Zeta
- **Introduction to Qucs-S**
 - Automatic parameter extraction

Qucs-S: Quite universal circuit simulator with SPICE


Simulation setup:

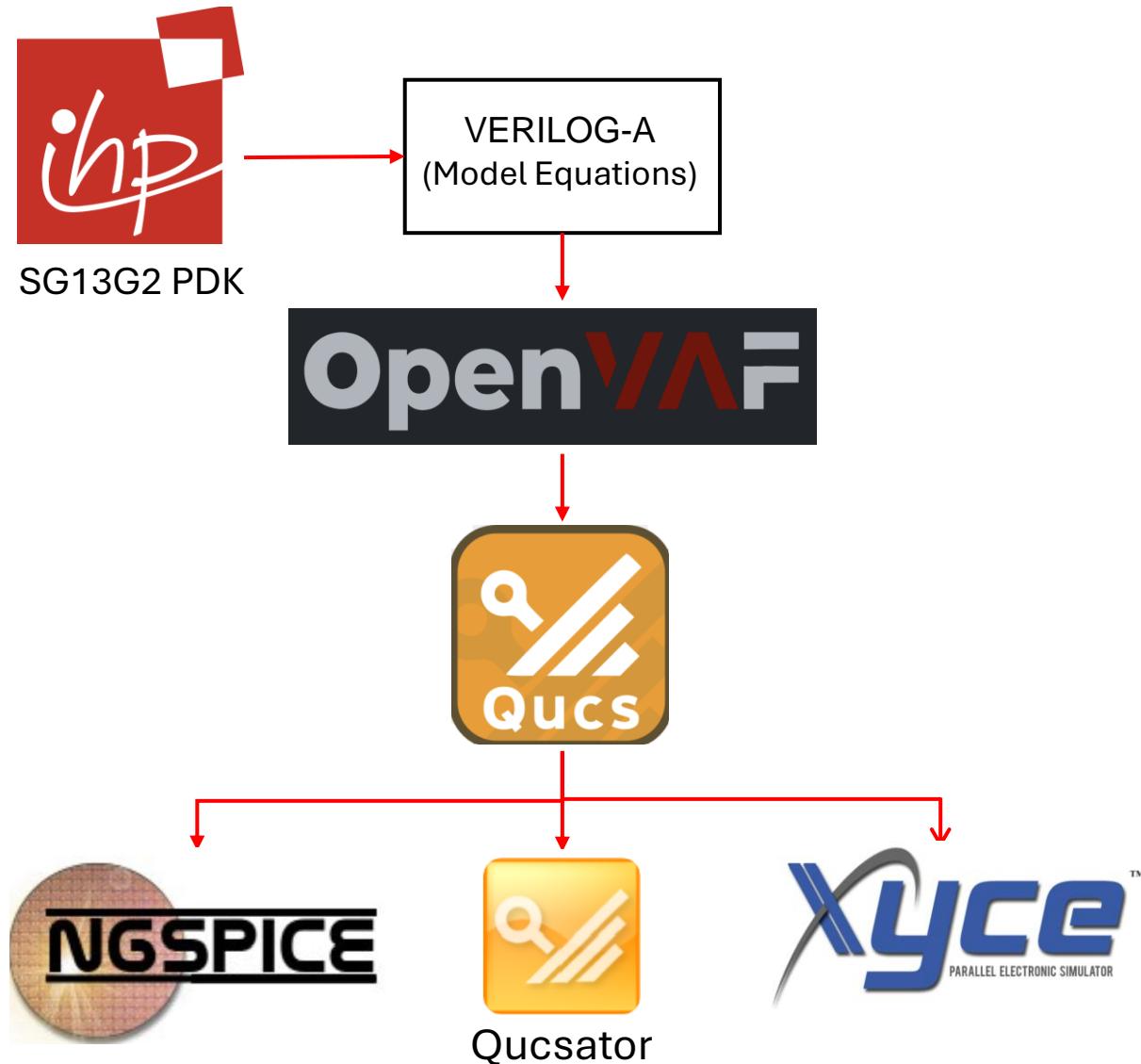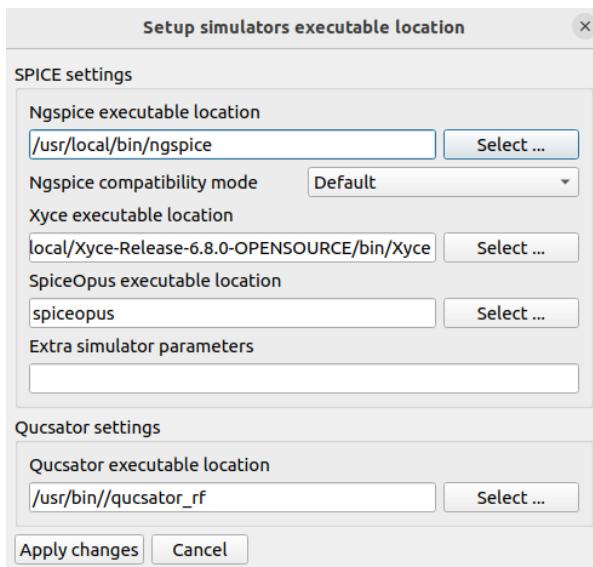

Qucs-S: Quite universal circuit simulator with SPICE

Simulations
Control

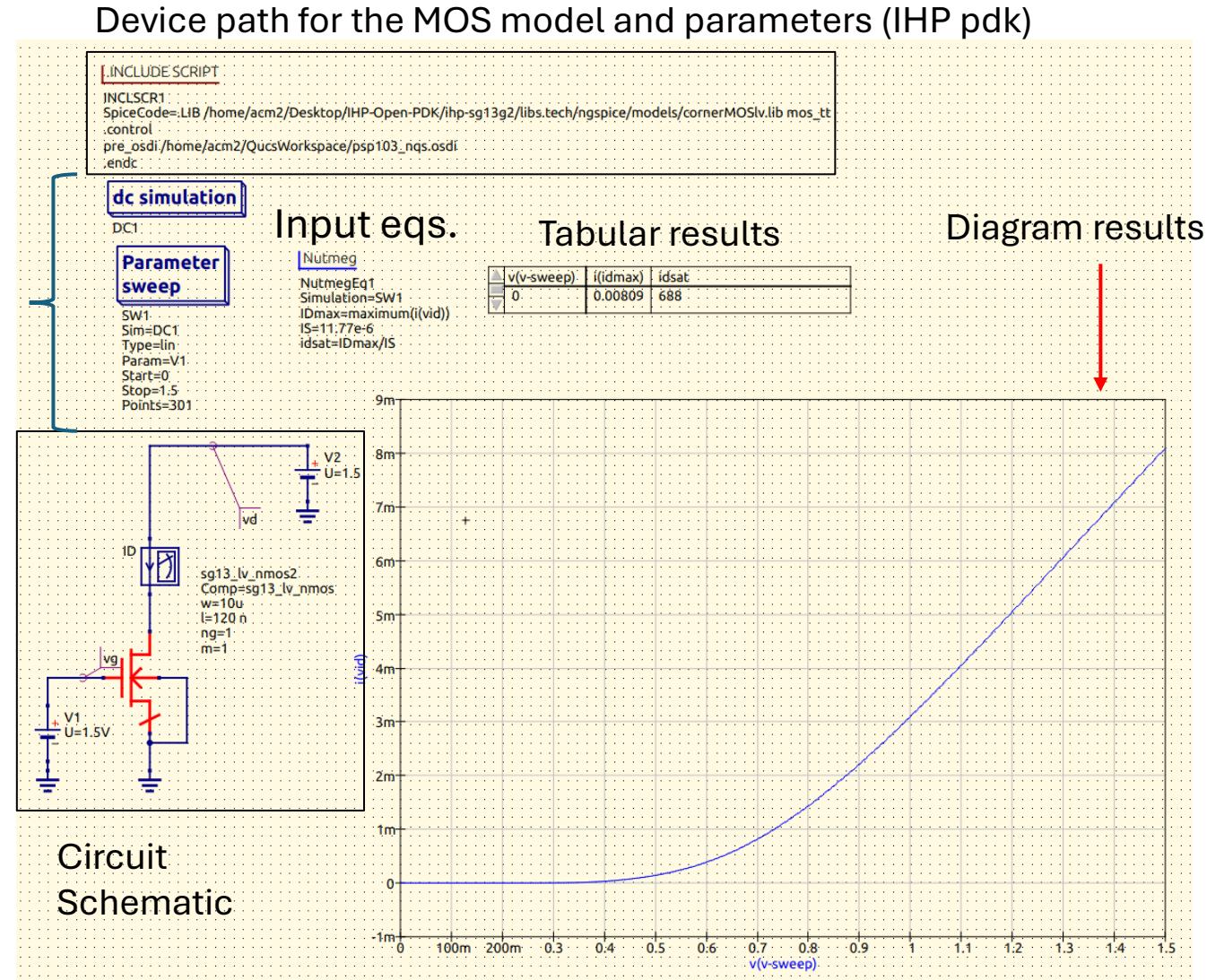- Ngspice simulations:
 - DC
 - AC
 - TRAN
 - S-parameters
 - Noise
 - Fourier



Let's go to Qucs-S!

Useful links:


- Qucs-S oficial page: <https://ra3xdh.github.io/>
- Qucs-S iterative doc: <https://qucs-s-help.readthedocs.io/>
- Ngspice oficial page : <https://ngspice.sourceforge.io/index.html>
- Google Colab: ACM2 & LNA design:
https://colab.research.google.com/drive/1s3PKF6pf3zlhlTj6jc-qhCLlcGfJ_UEE?usp=sharing

Github – ACM2


Github - Content

ACMmodel Merge pull request #26 from gabrielmaranhao/main		...
Examples	Update SKY130 and GF180 using ACM examples on xschem	
Verilog-A	Update PMOS_ACN_2V0.va	
docs	Delete 5PM_NewCAS.pdf	
LICENSE	Update LICENSE	
README.md	Update README.md	
README	ECL-2.0 license	

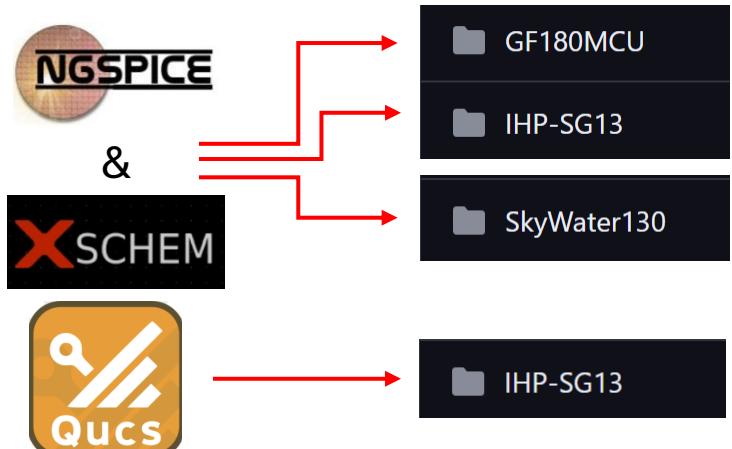Examples of PDKs and circuit simulators using the ACM model



Nancy, November 2024

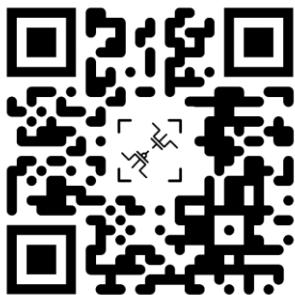

“Scan me”

Verilog-A code Available!

MOSFET_model / Verilog-A / NMOS_ACN_2V0.va



Part 3

Advanced Compact MOSFET Model: Design Methodology-Application to Low Noise Amplifier



“Scan me”



Sylvain Bourdel



https://github.com/ACMmodel/MOSFET_model

- Overview of Design Methods for RFIC
- LNA Design Considerations
- Resistive Feedback LNA
- What we need in ACM-2
- Inversion Level Based Method for R-Feedback LNA with ACM-2

- Overview of Design Methods for RFIC
- LNA Design Considerations
- Resistive Feedback LNA
- What we need in ACM-2
- Inversion Level Based Method for R-Feedback LNA with ACM-2

Overview of Design Methods for RFIC General Principle

- 1st Step: Architecture Choice

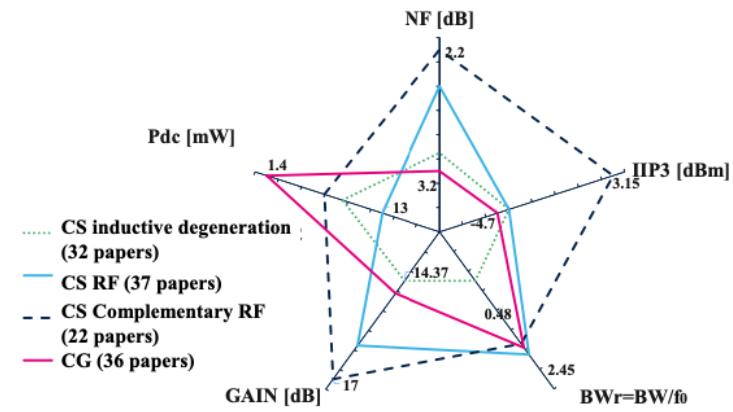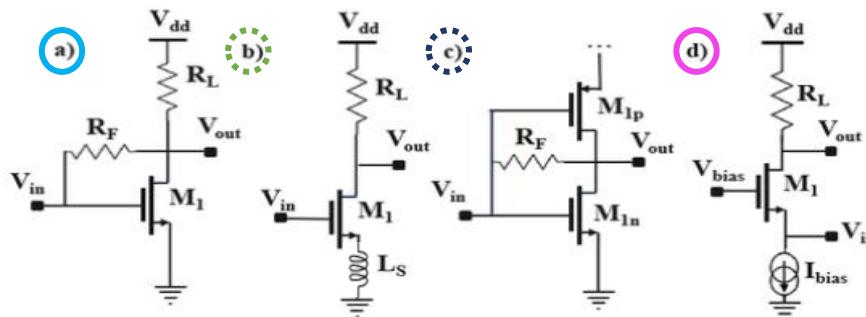

- 2nd Step: Circuit Analysis



Circuit
Perf.
(G_V , F ,
 $IIP3$...)




Circuit
Param.
(R_L , g_m ,
 R_F ...)

$$|G_T| = |G_v|Q_{IN} = \frac{(G_mR_F - 1)R_O}{(R_O + R_F)} \sqrt{1 + Q_P^2}$$

Overview of Design Methods for RFIC

General Principle


- 3rd Step: Circuit Sizing

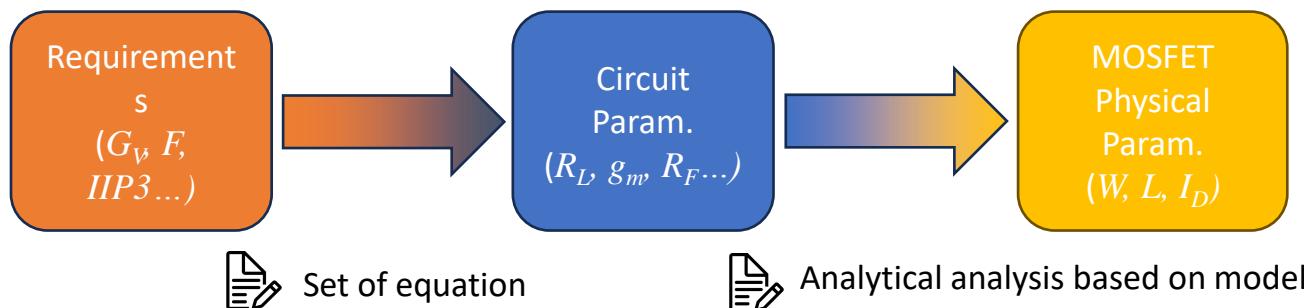

Overview of Design Methods for RFIC

General Principle

- 3rd Step: Circuit Sizing

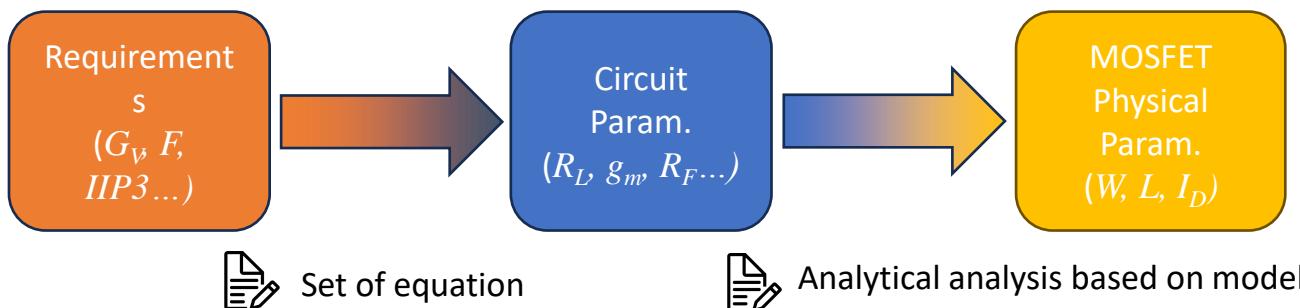

Region based model

$$\text{sat.} \quad I_d = 2.K_n \frac{W}{L} \left[(V_{gs} - V_t) V_{ds} - \frac{V_{ds}^2}{2} \right]$$


$$\text{lin.} \quad I_d = K_n \frac{W}{L} (V_{gs} - V_t)^2 \left(1 + \frac{k_{en}}{L} V_{ds} \right)$$

PROS: simple

CONS: Inaccurate with short channel MOS

Overview of Design Methods for RFIC General Principle

- 3rd Step: Circuit Sizing

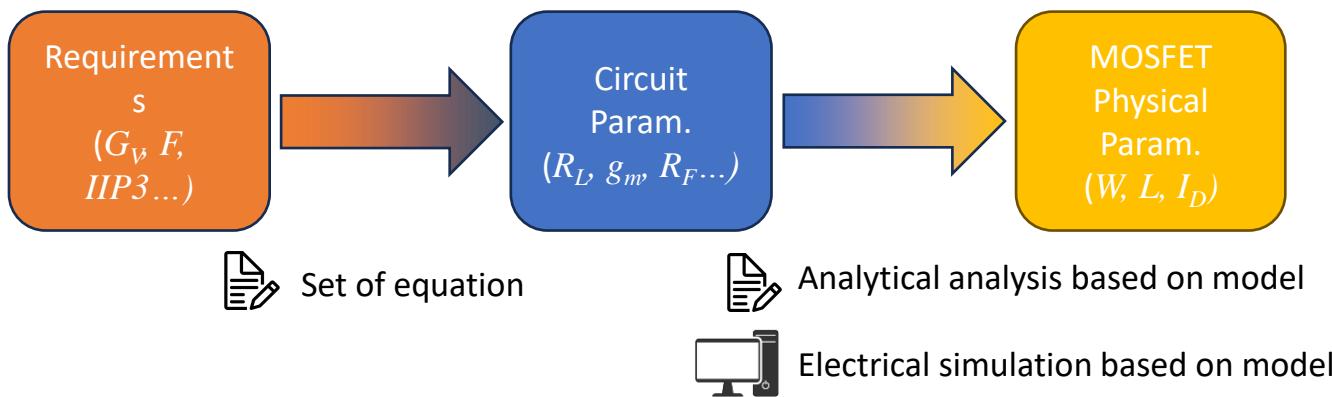


BSIM3 / UTSOI compact model

PROS: Accurate

Direct relationship between requirements and physical parameters

CONS: Increases the gap between Physic and design

- Issue in the sizing step

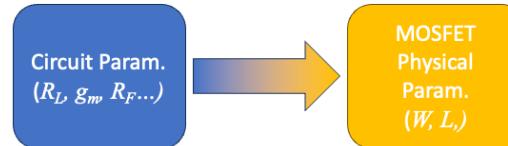


- How to maintain simplicity **and** accuracy with the scaling and especially Short Channel Effects (SCE) at the sizing step.
- g_m/I_d design approaches
 - LUT based
 - ACM or EKV based

Overview of Design Methods for RFIC g_m/Id approach based on LUT

General Principle [Silveira, Flandre, Jespers – JSSC 1996]



- For a given structure

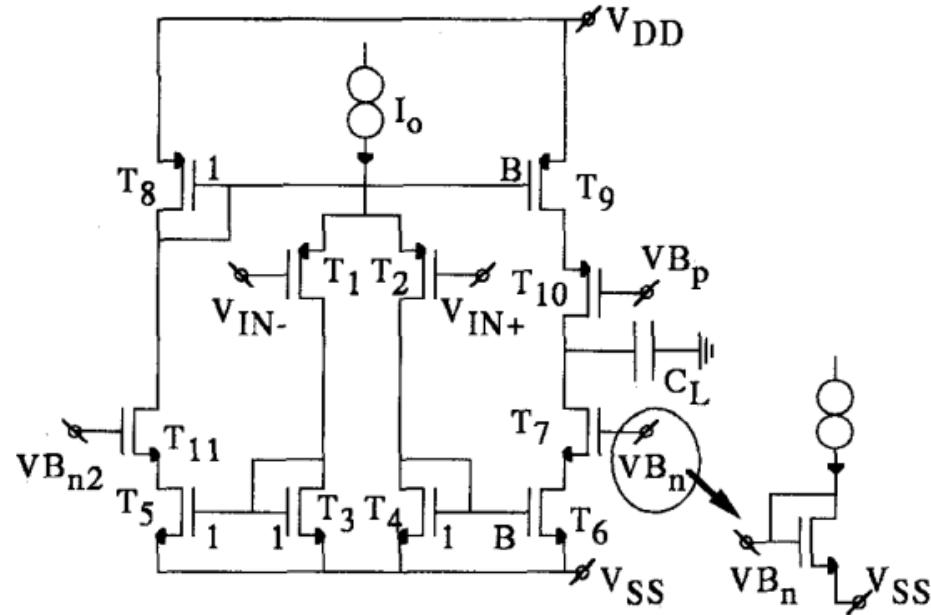

Overview of Design Methods for RFIC g_m/Id approach based on LUT


General Principle

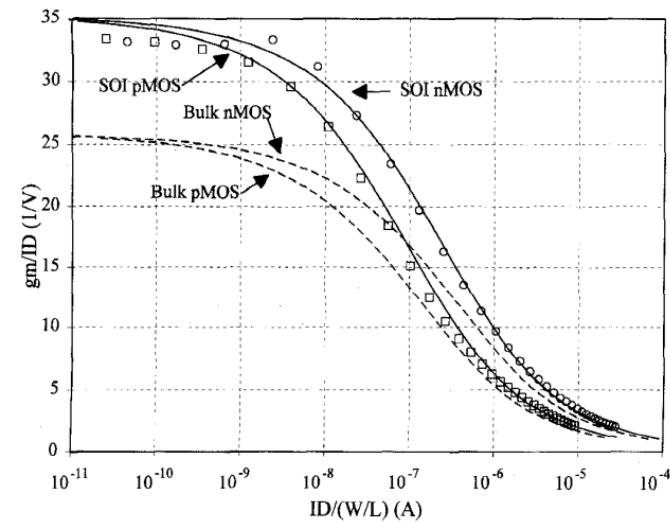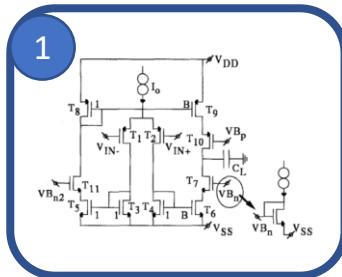- For a given structure
- Methods are based on
⇒ Extraction of MOS parameters (LUT)
 - $I_D/(W/L)$ vs g_m/I_D
 - g_m/I_D vs V_{gs0}



General Principle

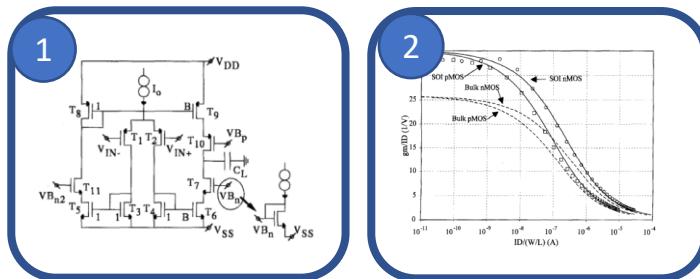- For a given structure
- Methods are based on
 - ⇒ Extraction of MOS parameters (LUT)
 - $I_D/(W/L)$ vs g_m/I_D
 - g_m/I_D vs V_{gs0}



⇒ Set of equations



$$SR = \frac{B \cdot I_{D1}}{C_L} \quad (5)$$

$$f_T = \frac{B \cdot g_{m1}}{2\pi \cdot C_L} \quad (5)$$

$$A_0 = \left(\frac{g_m}{I_D} \right)_1 \cdot \left(\frac{g_m}{I_D} \right)_2 \cdot \frac{1}{\frac{1}{V_{A6} \cdot V_{A7}} + \frac{1}{V_{A9} \cdot V_{A10}}} \quad (4)$$

General Principle

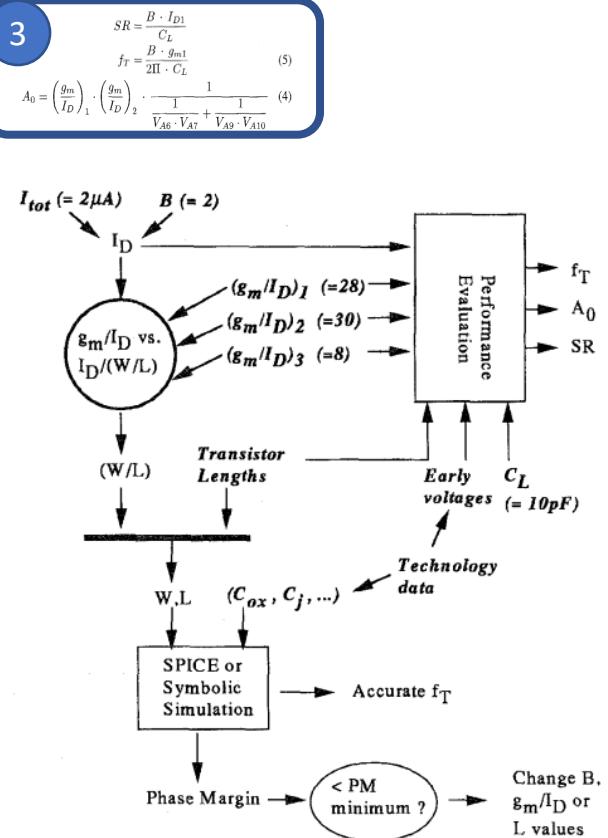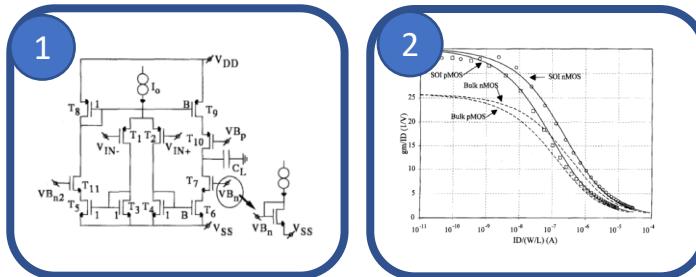- For a given structure
- Methods are based on
 - ⇒ Extraction of MOS parameters
 - $I_D/(W/L)$ vs g_m/I_D
 - g_m/I_D vs V_{gs0}
 - ⇒ Set of equations
- Methods helps the designers in sizing the structure
- Quite used in low frequency domain




LIMITATIONS ?

- Time Consuming
- Lakes of precision (parametric set of characteristics)

- ↓
- Long optimization sequence

Need for a model based approach

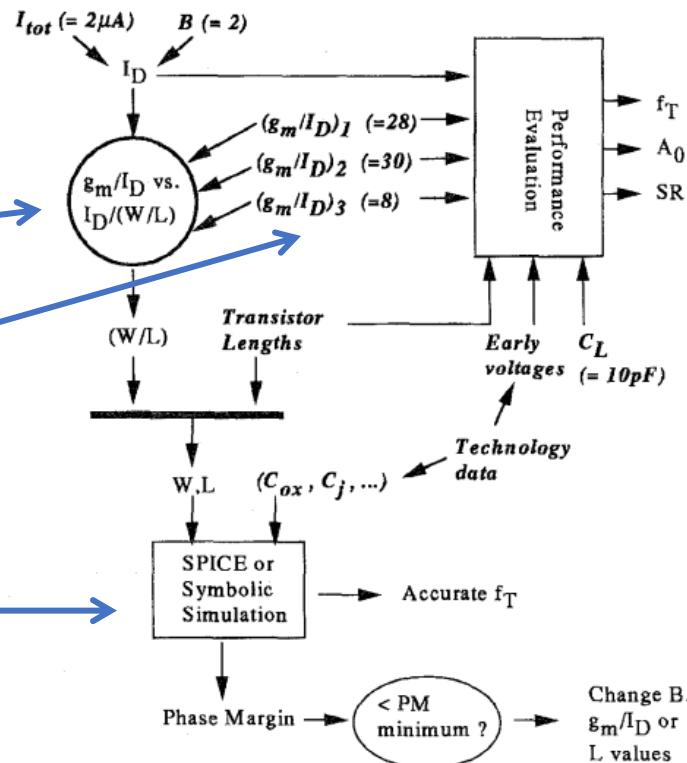

All Region 3PM model


- EKV – [Enz, Krummenacher, Vittoz]
- ACM – [Schneider, Galup]
- With a 3PM model we have :

$$\frac{I_D}{(W/L)} = i_f I_{S0}$$

$$\frac{g_m}{I_D} = \frac{2}{n\phi_t \left(1 + \sqrt{1 + i_f}\right)} \quad g_m = \frac{2I_S}{\phi_t} \left(\sqrt{1 + i_f} - 1 \right) \quad V_P - V_{S(D)} = \phi_t \left[\sqrt{1 + i_{f(r)}} - 2 + \ln \left(\sqrt{1 + i_{f(r)}} - 1 \right) \right]$$

$$V_P \equiv \frac{V_G - V_{T0}}{n}$$

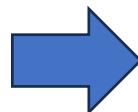- PROS: The sizing is straightforward
- CONS: Inaccurate with SCE
Non-linearities can't be captured
gds effect can't be captured





Is it possible in RFIC ?

Design Regions



Year 2000 (RF-180nm)



- f_t grows with i_f

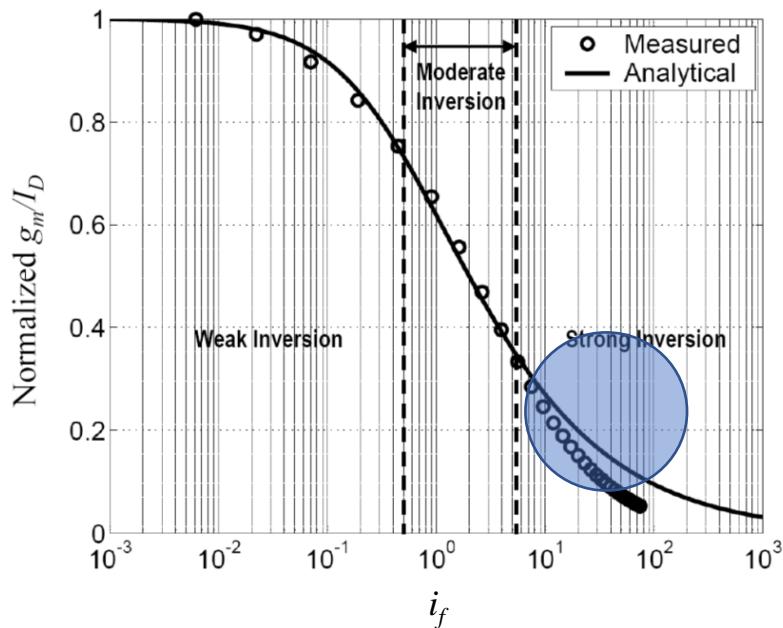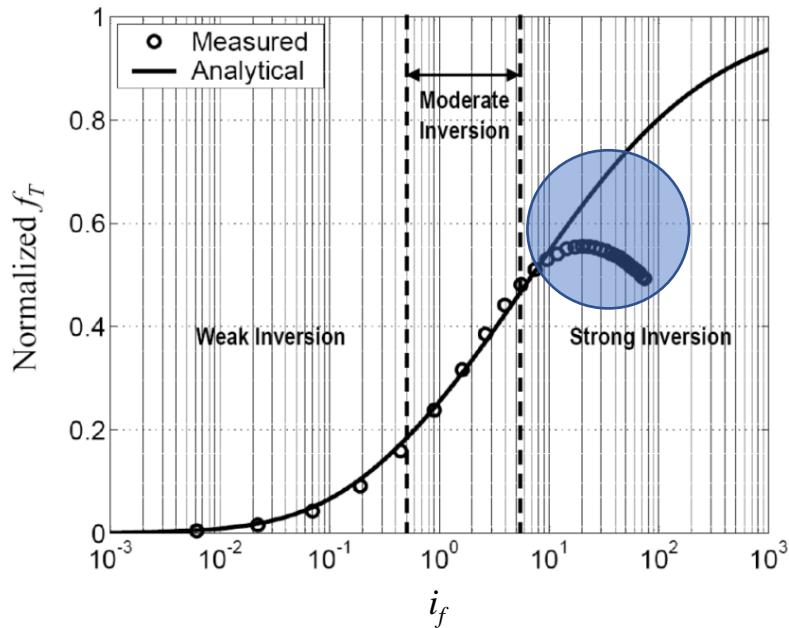

Design Regions

- f_T grows with i_f but g_m/I_D reduces with i_f

Year 2000 (RF-180nm)
Year 2016 (RF-22nm)

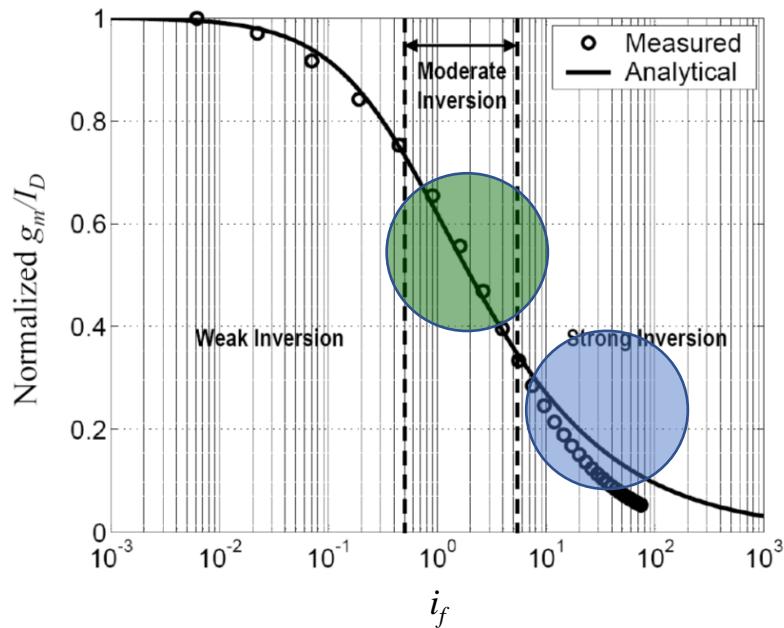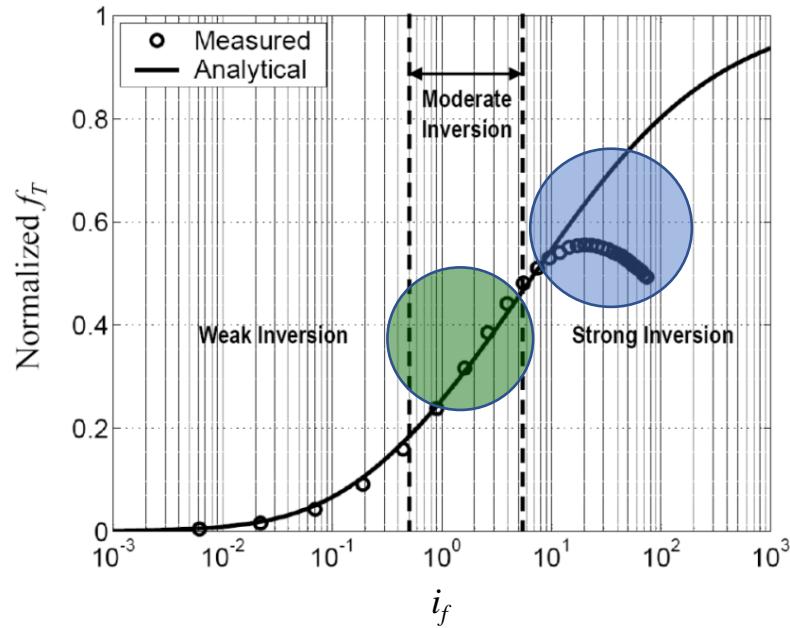


$g_m f_T / I_D : A First Approach$

- For RF design
- A FOM that maximize the gain bandwidth product

$$\frac{g_m f_T}{I_D}$$

- Gives the i_f that produces the best GBW product
- Not optimal :
 - the gain or the bandwidth might be oversized.
 - Do not depends on the topology

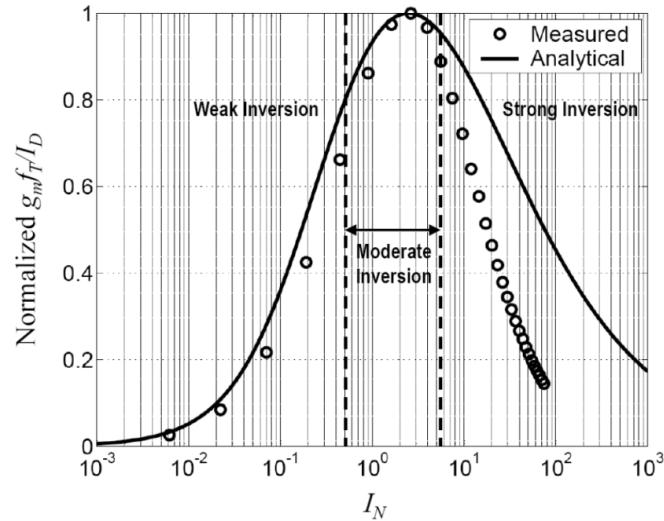A. Shameli et P. Heydari, « Ultra-Low Power RFIC Design Using Moderately Inverted MOSFETs: An Analytical/Experimental Study », *RFCI*, 2004.




- Overview of Design Methods for RFIC
- LNA Design Considerations
- Resistive Feedback LNA
- What we need in ACM-2
- Inversion Level Based Method for R-Feedback LNA with ACM-2

LNA Design considerations

Noise Factor

- NF is the signal to noise ratio (SNR) degradation (Eq. 1)
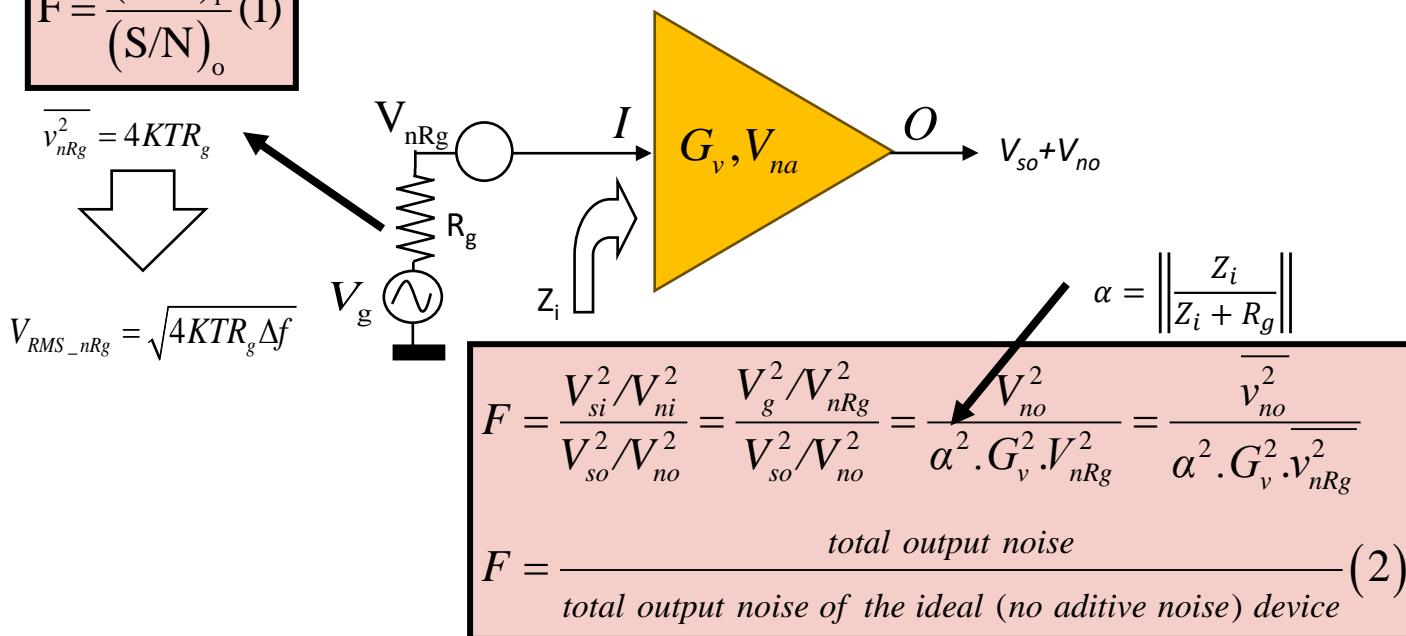
$$F = \frac{(S/N)_i}{(S/N)_o} \quad (1)$$




- NF also express the quantity of noise added by the stage regarding the noise delivered by the source (R_g) on Δf . (Eq. 2)

LNA Design considerations

Friss Formula

➤ RF Basis

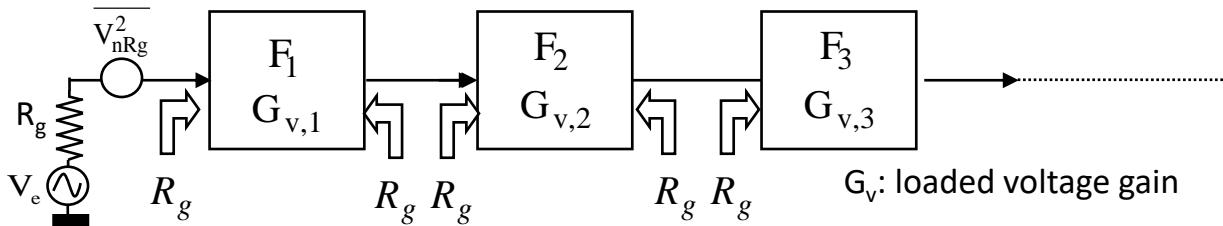

$$F = F_1 + \frac{(F_2 - 1)}{G_{v,1}^2} + \frac{(F_3 - 1)}{G_{v,1}^2 \cdot G_{v,2}^2} + \dots$$

This formula is valid only for real impedances and in case of power matching: ($Z_s = Z_e = R_g$)

In RFIC, impedances are complex and never equal. This formula cannot be used as is. However, the following statements remain valid in RFIC.

The gain of the first stages reduces the NF of the following ones.

=> The receiver chain must start by amplifiers

=> The NF of the first stage must be as low as possible

Note that lossy stages ($G_v < 1$) increase the NF, especially when they are in front of the receiver chain (**antenna filter, image rejection filter, antenna switch**).




LNA Design considerations

Input patching


System point of vue

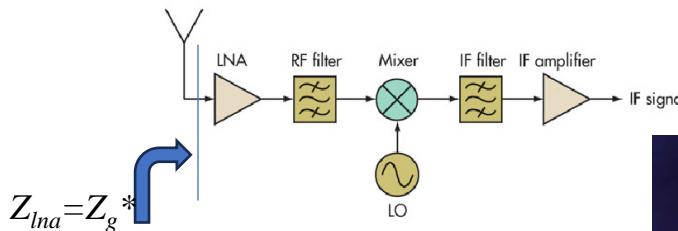- LNA is the first device due to Friss formula
- Antenna is mainly 50Ω .



In CMOS

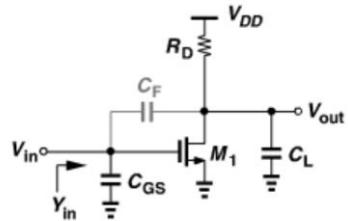- Generally, the input impedance is capacitive $\text{Re}(Y_{11})$ is very low
- For example : CS amplifier




$$\Re(Y_{in}) = R_D \| 1/g_m$$

$$\Im(Y_{in}) = \frac{1}{C_{GS} C_F \omega}$$


Common Structures

CG

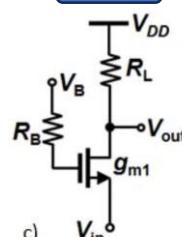


$$\Re(Z_{in}) = \frac{1}{g_{m1}}$$

R-Feedback

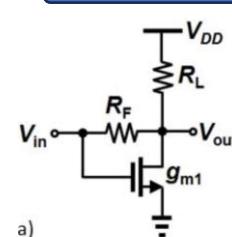

$$\Re(Z_{in}) = \frac{R_F}{1 + |A_V|}$$

Inductive Degeneration


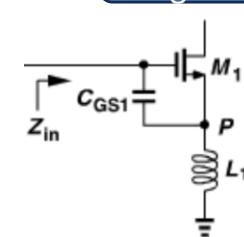


$$\Re(Z_{in}) = \frac{g_m L_1}{C_{GS}}$$

LNA Design considerations

Non-Linearities

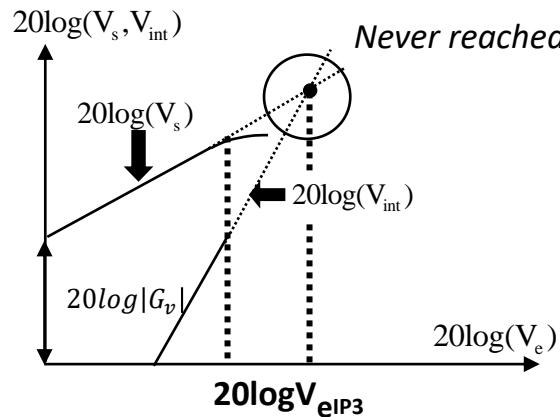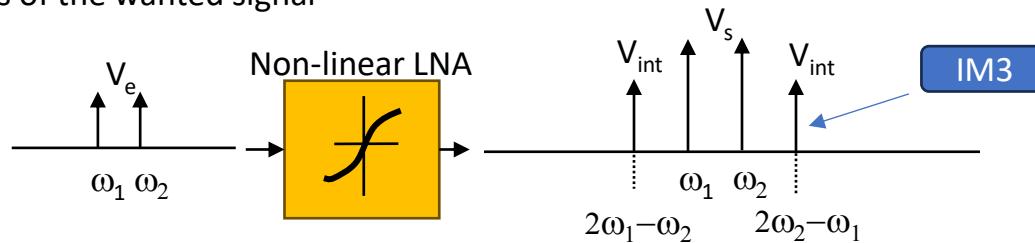ω_1 and ω_2 are 2 harmonics of the wanted signal



Never reached in measurement !

The IIP3 (V_{eIP3}) is the input signal level for which the output IM3 is equaling the fundamental harmonic (V_s) extrapolated from small signal (AC).

The IIP3 (V_{eIP3}) is related to the maximum power you can apply to your system

- Overview of Design Methods for RFIC
- LNA Design Considerations
- Resistive Feedback LNA
- What we need in ACM-2
- Inversion Level Based Method for R-Feedback LNA with ACM-2

R-Feedback general considerations

- Simple
- Compact (No-inductors)
- Wideband
- RF allows to synthesize a real part in Z_{in}
- LG and CGS' will help in cancelling the imaginary part while controlling Q_{in}

Input impedance

$$Z_{IN} = L_G s + \left(\frac{1}{(C_{GS} + C'_{GS})s} \right) // Z_P$$

$$\Re(Z_P) = R_P = \frac{(R_O + R_F)}{1 + G_m R_O},$$



$$C_P = \frac{R_O^2 C_L (G_m R_F - 1)}{(R_O + R_F)^2}$$

$$\Re(Z_{IN}) = R_S = \frac{R_P}{(1 + Q_P^2)} = 50 \Omega$$

$$Q_P = R_P C_T \omega_0$$

$$C_T = C_{GS} + C'_{GS} + C_P$$
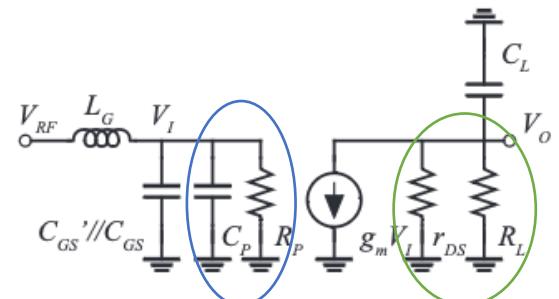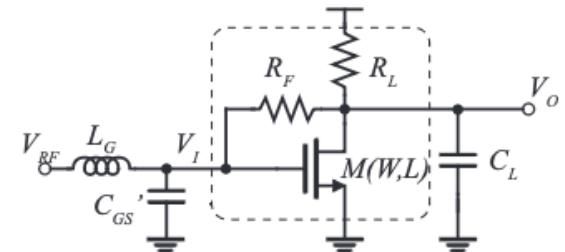
$$\Im(Z_{IN}) = 0 = L_G s + \frac{Q_P^2}{C_T s (1 + Q_P)^2}$$



$$R_O = \frac{R_L r_{DS}}{R_L + r_{DS}}$$


Resistive Feedback LNA Topology

Voltage Gain

$$|G_T| = |G_v|Q_{IN} = \frac{(G_m R_F - 1)R_O}{(R_O + R_F)} \sqrt{1 + Q_P^2}$$

$$Q_{IN} = V_I/V_{RF} = \sqrt{1 + Q_P^2} = \sqrt{\frac{R_O + R_F}{R_S(1 + G_m R_O)}}$$

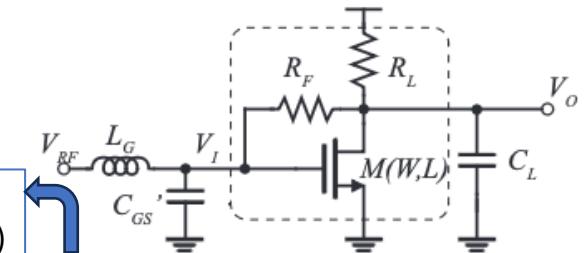R_S
(the source resistance seen at the 50 Ω input)



Noise Figure

$$F = 1 + \frac{4 \left(\frac{R_F}{Q_{IN}^2} + R_S \right)^2}{Q_{IN}^2 G_m R_S \left[\frac{R_F}{Q_{IN}^2} + R_S + \frac{G_m R_S R_F R_L}{R_F + R_L} \right]^2} \left[\gamma + \frac{1}{G_m R_L} + \frac{\left(1 + \frac{Q_{IN}^2 G_m R_S R_F}{R_F + Q_{IN}^2 R_S} \right)^2}{G_m R_F} \right]$$


$$\left(F_{min} = 1 + \frac{(1 + G_m) R_S^2 R_F}{R_S (1 - G_m R_F)^2} + \frac{\gamma g_m (R_S + R_F)^2}{R_S (1 - G_m R_F)^2} + \frac{(R_S + R_F)^2}{R_S R_L (1 - G_m R_F)^2} \right)$$

IIP_3

$$V_{IIP3} = \frac{2}{Q_{IN}} \sqrt{\frac{2G_m}{G_{m3}}}$$

BW
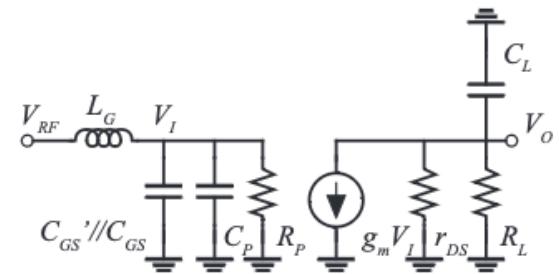
$$f_c = \frac{R_O + R_F}{2\pi R_O R_F C_L}$$



- Overview of Design Methods for RFIC
- LNA Design Considerations
- Resistive Feedback LNA
- What we need in ACM-2
- Inversion Level Based Method for R-Feedback LNA with ACM-2

Small signal (AC) parameters

- G_T , NF, IIP3 vs (G_m , G_{m3} , G_{DS})

$$g_m = \frac{\partial I_D}{\partial V_G} = \frac{I_S}{\phi_t} g_G = \frac{I_S}{n\phi_t} \frac{2(q_s - q_d) - i_d \zeta \left(\frac{q_s}{1+q_s} - \frac{q_d}{1+q_d} \right)}{1 + \zeta (q_s - q_d)} \quad g_{ds} = \frac{I_S}{\phi_t} g_D = \frac{I_S}{n\phi_t} \frac{2(q_s \sigma - q_d (\sigma - n)) - i_d \zeta \left(\sigma \frac{q_s}{1+q_s} - (\sigma - n) \frac{q_d}{1+q_d} \right)}{1 + \zeta (q_s - q_d)}$$

$$g_{m3} = \frac{I_S}{(n\phi_t)^3} \left\{ \frac{\frac{2q_s}{(1+q_s)^3} - \frac{2q_d}{(1+q_d)^3} - \zeta n^2 g_{G2} \left(\frac{q_s}{1+q_s} - \frac{q_d}{1+q_d} \right) - \zeta \left[2ng_G \left(\frac{q_s}{(1+q_s)^3} - \frac{q_d}{(1+q_d)^3} \right) + i_d \left(\frac{q_d(1-2q_d)}{(1+q_d)^5} - \frac{q_d(1-2q_d)}{(1+q_d)^5} \right) \right]}{1 + \zeta (q_s - q_d)} \right\}$$

- Valid in all region (q_s and q_d shall be explored)
 - We consider only saturation
 - It reduces the exploration to only q_s .

$$q_{dsat} = q_s + 1 + \frac{1}{\zeta} - \sqrt{\left(1 + \frac{1}{\zeta}\right)^2 + \frac{2q_s}{\zeta}}$$

$$g_{msat} = \frac{2I_S}{n\phi_t} \frac{q_s}{1 + \zeta(q_s + 1)} \quad g_{msat^3} = \frac{16I_S}{(n\phi_t)^3} \frac{q_s}{(q_s + 1)^3} \frac{2 - 2\zeta q_s - 3\zeta q_s^2}{(\zeta q_s + 2)^4} \quad g_{dsat} = \sigma \frac{2I_S}{n\phi_t} \frac{q_s}{1 + \zeta(q_s + 1)}$$

Large signal (DC) parameters

- To compute the final voltages


$$V_T = V_{T0} - \sigma(V_{SB} + V_{DB})$$

$$V_P = \frac{V_{GB} - V_T}{n}$$

$$\frac{V_P - V_{S(D)B}}{\phi_t} = q_{s(d)} - 1 + \ln q_{s(d)}$$

- Sometimes we'll use i_f in the code

$$i_d = i_f - i_r \quad \longleftrightarrow \quad q_{S(D)} = \sqrt{1 + i_{f(r)}} - 1, \quad \longleftrightarrow \quad i_d = \frac{(q_s + q_d + 2)}{1 + \zeta|q_s - q_d|} (q_s - q_d)$$

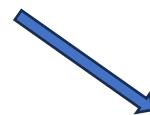

$$I_D = I_{SO} \cdot i_d$$



$$I_{SO} = \mu C'_{ox} n \frac{(U_T)^2}{2} \frac{W}{L}$$

- Overview of Design Methods for RFIC
- LNA Design Considerations
- Resistive Feedback LNA
- What we need in ACM-2
- Inversion Level Based Method for R-Feedback LNA with ACM-2

General Approach :

Requirements

- GT, NF, IIP3, IDC ← Possible Tradeoff
- fo, CL, BW ← No Tradeoff

Design parameters

- ACM parameters for a fixed L
- $V_{T0}, I_S, n, \sigma, \zeta$

Design Variables (parameters)

- W, qs are first order design variables (qs = inversion level sets the energy efficiency and the voltages)
- RL, RF are second order design variables

Approach :

- Explore the different tradeoff (the design space) on GT, NF, IIP3 and IDC by playing with W, qs.
- In saturation region (only qs is needed)

$$g_{msat} = \frac{2I_S}{n\phi_t} \frac{q_s}{1 + \zeta(q_s + 1)} \quad g_{msat3} = \frac{16I_S}{(n\phi_t)^3} \frac{q_s}{(q_s + 1)^3} \frac{2 - 2\zeta q_s - 3\zeta q_s^2}{(\zeta q_s + 2)^4} \quad g_{dsat} = \sigma \frac{2I_S}{n\phi_t} \frac{q_s}{1 + \zeta(q_s + 1)}$$

- Circuit equations depend on Gm and ACM depends on gm ...

$$|G_T| = \frac{(G_m R_F - 1) R_O}{(R_O + R_F)} \sqrt{\frac{R_O + R_F}{R_S(1 + G_m R_O)}} \quad G_{[m;DS]x} = \mu C'_{ox} \frac{(U_T)^{2-x}}{2} \frac{W}{L} g_{[m;DS]x}$$

Where we introduce W in the design space

$$I_{S0} = \mu C'_{ox} n \frac{(U_T)^2}{2} \frac{W}{L} \quad I_{SL} = \frac{I_{S0}}{W} = \mu C'_{ox} n \frac{(U_T)^2}{2L}$$

Inversion Level Based Method for R-Feedback LNA with ACM-2

Reducing the variables :

$$\text{Starting from : } |G_T| = \frac{(G_m R_F - 1) R_O}{(R_O + R_F)} \sqrt{\frac{R_O + R_F}{R_S(1 + G_m R_O)}}$$

$$G_{[m;DS]x} = \mu C'_{ox} \frac{(U_T)^{2-x}}{2} \frac{W}{L} g_{[m;DS]x} \quad \longrightarrow \quad g_{msat} = \frac{2I_S}{n\phi_t} \frac{q_s}{1 + \zeta(q_s + 1)} \quad \longrightarrow \quad G_m(q_s; W)$$

$$\rightarrow g_{dsat} = \frac{\sigma}{n} \frac{2I_S}{\phi_t} \frac{q_s}{1 + \zeta(q_s + 1)} \rightarrow G_{DS}(q_s; W)$$

$$R_O = \frac{R_L r_{DS}}{R_L + r_{DS}} \longrightarrow G_{DS}(q_S, W)$$

$$V_{DSAT} = \phi_t(\sqrt{1 + i_f} + 3)$$

$$R_L(I_D) = \frac{V_{DD} - V_{DSAT}}{I_D}$$

$$i_f = (1 + q_s)^2$$


$$I_D = I_{SL} * W * i_f$$

$$R_F = \frac{R_0}{2\pi R_0 C_L f_c - 1} \quad \rightarrow \quad R_F(q_S; W) \Big|_{f_c}$$

$$\left(f_c = \frac{R_O + R_F}{2\pi R_O R_F C_L} \right)$$

variables

parameters

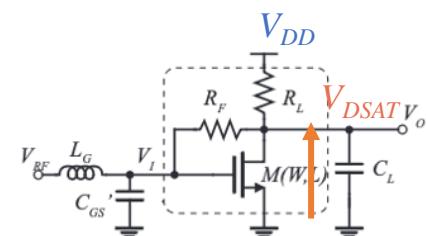


$$R_0(q_S; W)$$

$$G_T(G_m; R_0; R_F; R_S) = G_T(W; q_S)$$


Inversion Level Based Method for R-Feedback LNA with ACM-2

Finally : $I_D(q_s;W)$; $R_F(q_s;W)$; $R_0(q_s;W)$; $G_T(q_s;W)$


$I_D(q_s;W)$

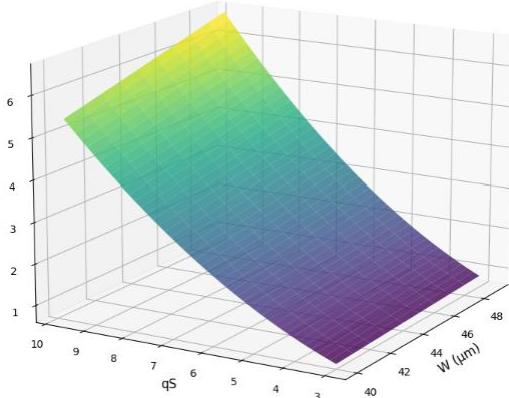

$R_0(q_s;W)$

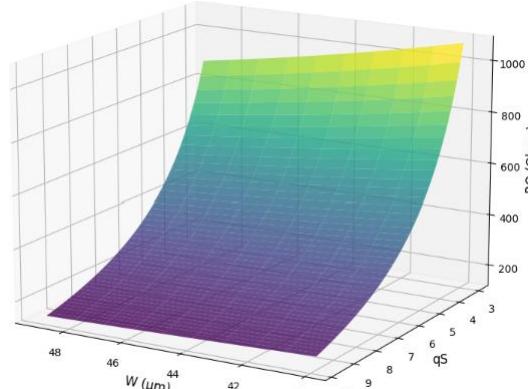

$R_F(q_s;W)$

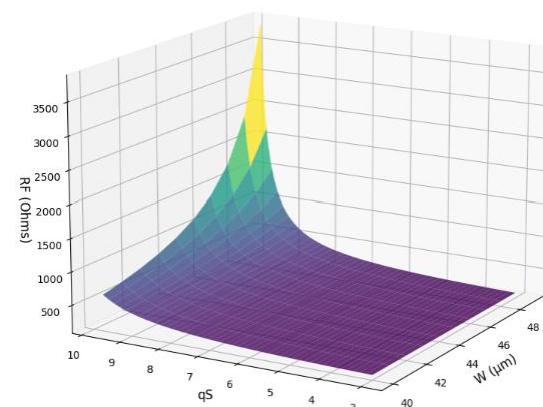

Computing GT , F and $IIP3$:

$$\text{Finally : } |G_T| = \frac{(G_m R_F - 1) R_O}{(R_O + R_F)} \sqrt{\frac{R_O + R_F}{R_S(1 + G_m R_O)}}$$





$$G_T(q_s; W)|_{f_c; C_L}$$

$$V_{IIP3} = \frac{2}{Q_{IN}} \sqrt{\frac{2G_m}{G_{m3}}}$$



$$IIP_3(q_s; W)|_{f_c; C_L; R_S}$$

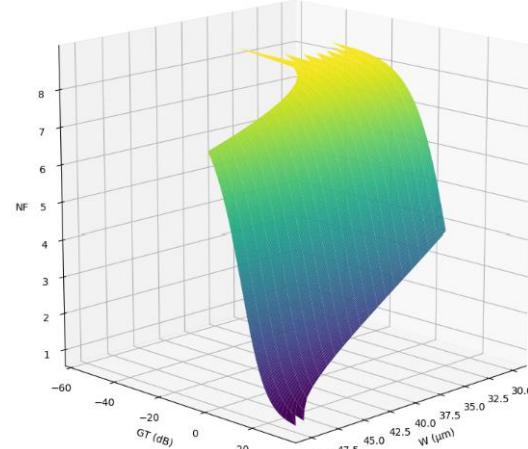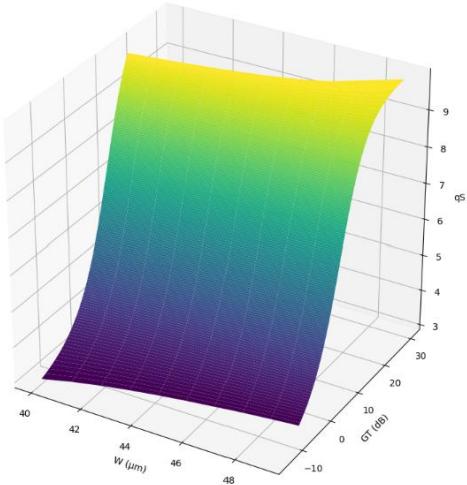

$$F = 1 + \frac{4 \left(\frac{R_F}{Q_{IN}^2} + R_S \right)^2}{Q_{IN}^2 G_m R_S \left[\frac{R_F}{Q_{IN}^2} + R_S + \frac{G_m R_S R_F R_L}{R_F + R_L} \right]^2} \left[\gamma + \frac{1}{G_m R_L} + \frac{\left(1 + \frac{Q_{IN}^2 G_m R_S R_F}{R_F + Q_{IN}^2 R_S} \right)^2}{G_m R_F} \right]$$



$$F(q_s; W)|_{f_c; C_L; R_S}$$

with $G_T(q_s; W)|_{f_c; C_L}$




$$F(G_T; W)$$

Remember :

$$Q_{IN} = V_I / V_{RF} = \sqrt{1 + Q_P^2} = \sqrt{\frac{R_O + R_F}{R_S(1 + G_m R_O)}}$$

$IIP_3 \text{ dB}(q_s, W)$

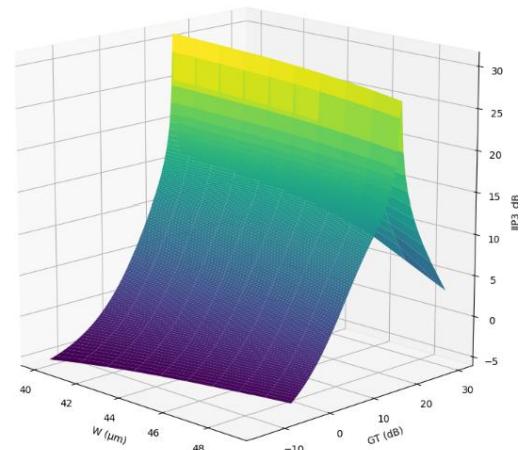

Exploring the design space:

Setting GT (or NF, or IIP3) helps to build 2D plots.




For a particular G_T

=> We get the relationship $q_S \Leftrightarrow W$

=> We plot $NF(W)$

=> We plot $IIP3(W)$

And We already have I_D

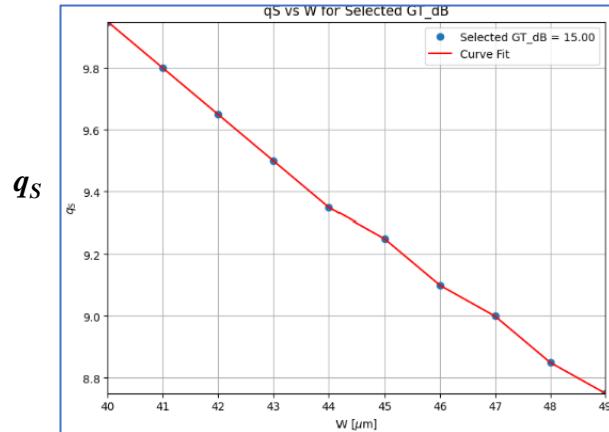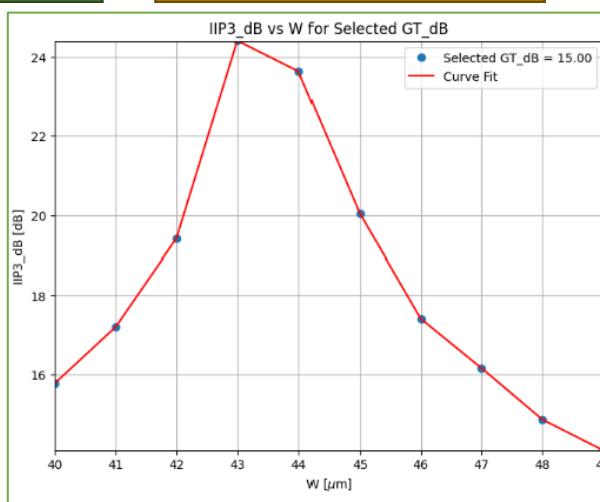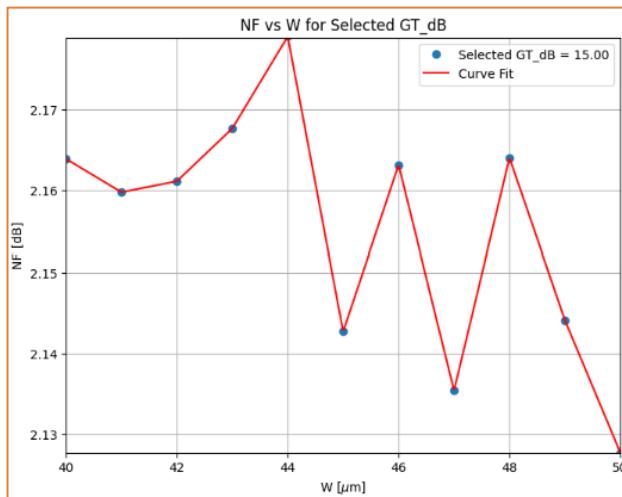

$W(\mu\text{m})$

Setting the final value:

- We choose W , that gives q_S for a given G_T .
- $(W; q_S)$ gives R_O , R_L , I_D , G_m , V_{DSAT} and V_G

Input Matching

- With R_O , R_F , $G_m \Rightarrow R_P$ $\Re(Zp) = R_P = \frac{R_O + R_F}{1 + G_m R_O},$
- With R_S and R_P calculate Q_P $\Re(Z_{IN}) = R_S = \frac{R_P}{(1 + Q_P^2)} = 50 \Omega$
- With Q_P calculate C_T and C_{GS} $Q_P = R_P C_T \omega_0 \quad C_T = C_{GS} + C'_{GS} + C_P \quad C_P = \frac{R_O^2 C_L (G_m R_F - 1)}{(R_O + R_F)^2}$
- With C_T calculate L_G $\Im(Z_{IN}) = 0 = L_G s + \frac{Q_P^2}{C_T s (1 + Q_P)^2}$

Now, let's simulate with a real PDK

