



Federal University of Santa Catarina
Department of Electrical Engineering
Integrated Circuits Laboratory



Modeling and Parameter Extraction of Zero-VT MOSFETs for Ultra-Low-Voltage Operation


Carlos Galup-Montoro, Márcio C. Schneider, and Márcio B. Machado



Outline

- ⇒ MOSFET model in weak inversion & triode regions
- ⇒ Low voltage operation of the basic amplifiers
- ⇒ Zero-VT MOSFETs
- ⇒ Colpitts oscillators

MOSFET: Weak inversion (WI) model

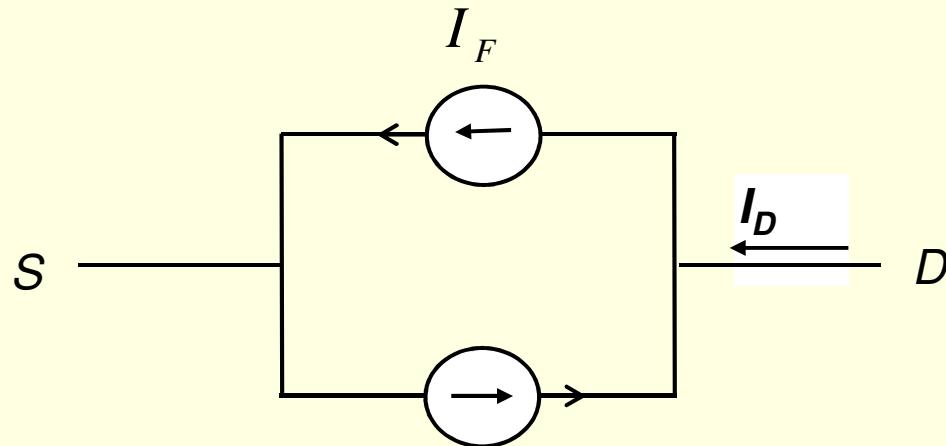


$$I_D = I_F - I_R = I_0 \left(e^{\frac{V_P - V_S}{\phi_t}} - e^{\frac{V_P - V_D}{\phi_t}} \right)$$
$$V_P \equiv \frac{V_G - V_{T0}}{n}$$
$$\phi_t = \frac{kT}{q} (= 26 \text{ mV} @ 300\text{K})$$

n : slope factor ($= 1.05 - 1.1$ for zero-VT transistors),


V_P : pinchoff voltage; V_{T0} : threshold voltage

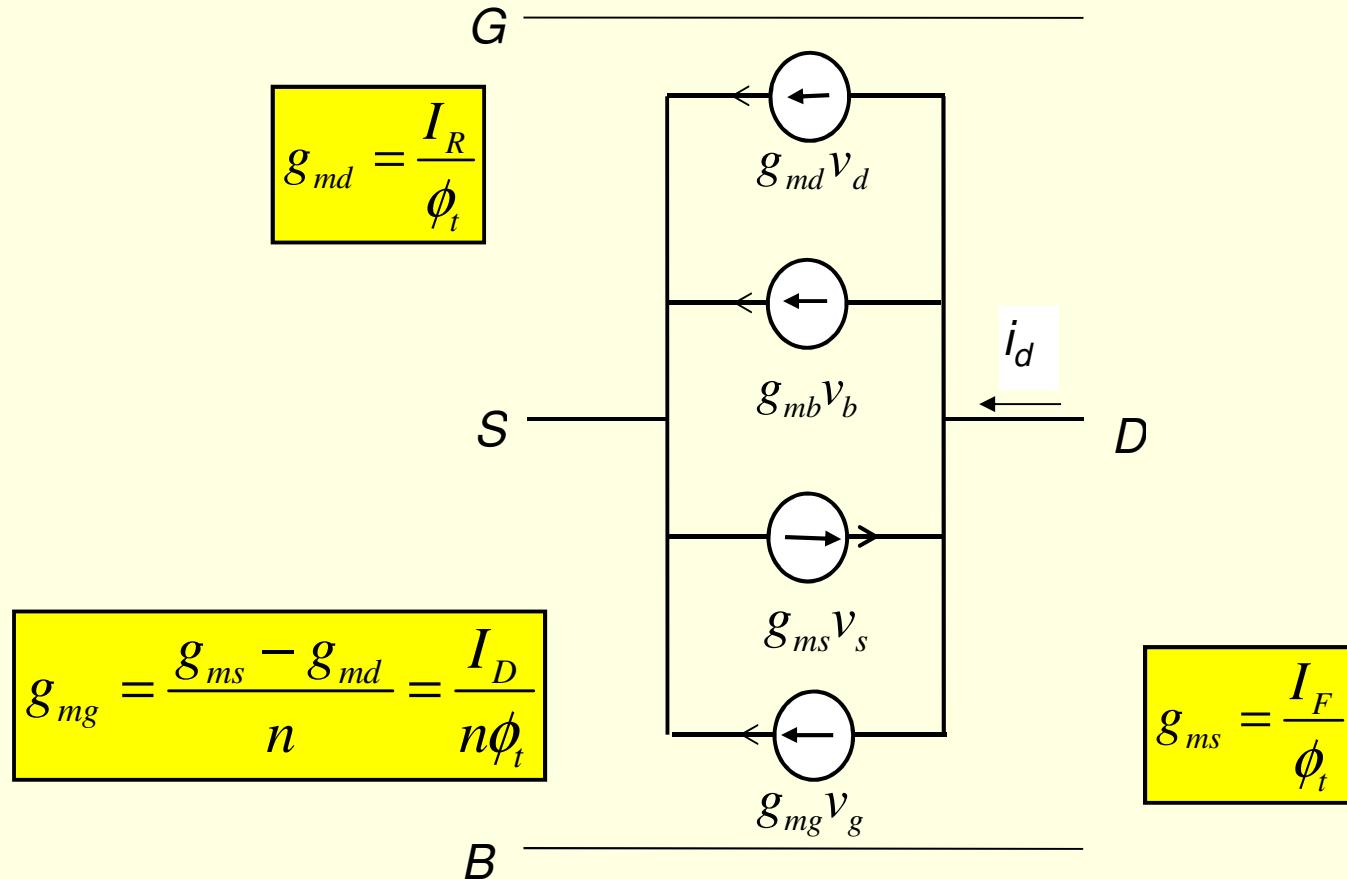MOSFET: low-frequency small-signal model in the triode region




$$g_{ms} = g_{mg} + g_{mb} + g_{md}$$

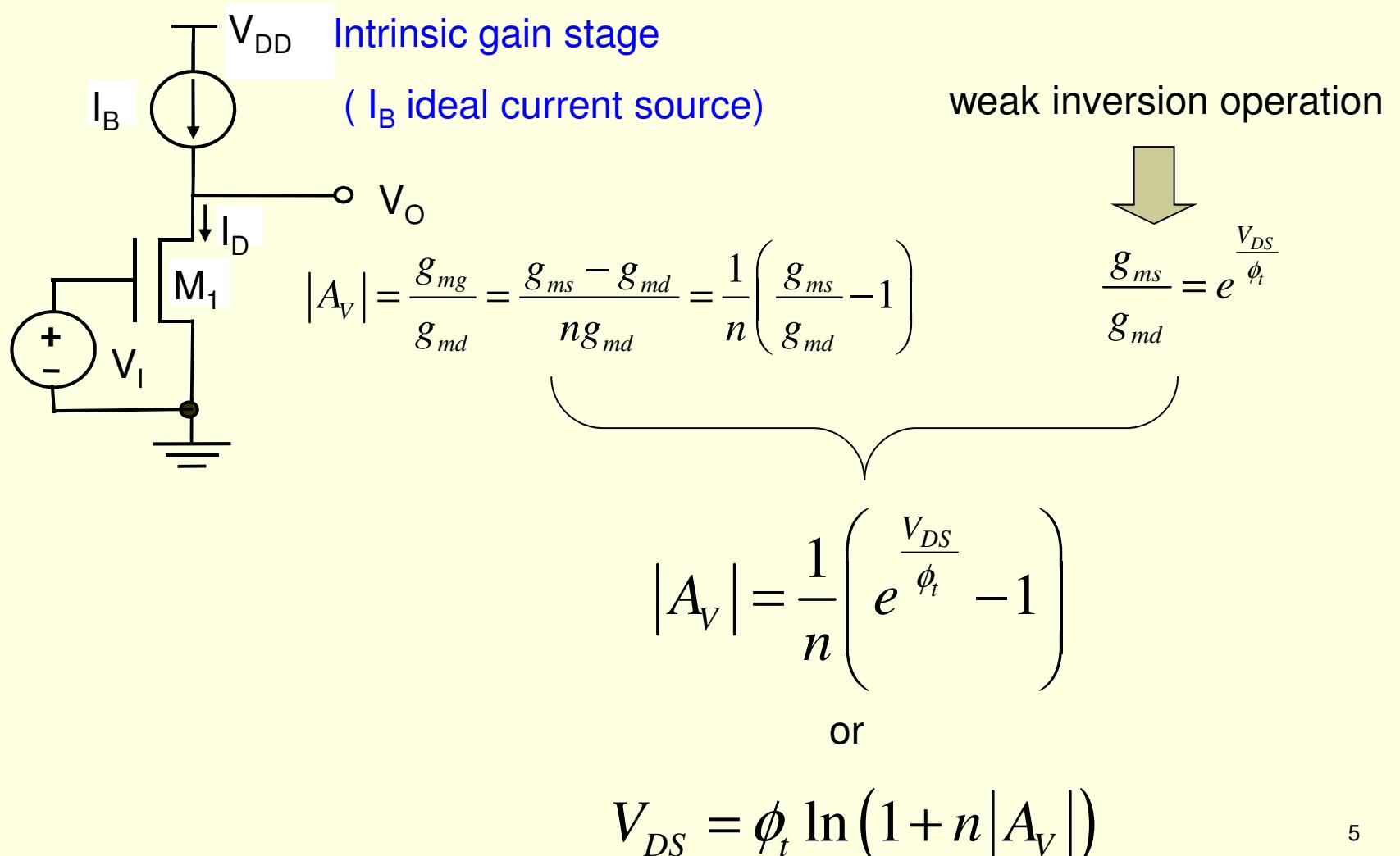Low-voltage operation of the common-source amplifier




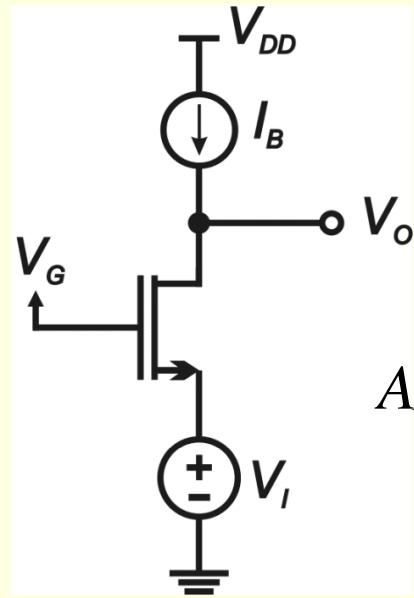Low-voltage operation of the common-gate amplifier




$$A_{v,cg} = \frac{v_o}{v_i} = \frac{g_{ms}}{g_{md}} = e^{\frac{qV_{DS}}{kT}}$$

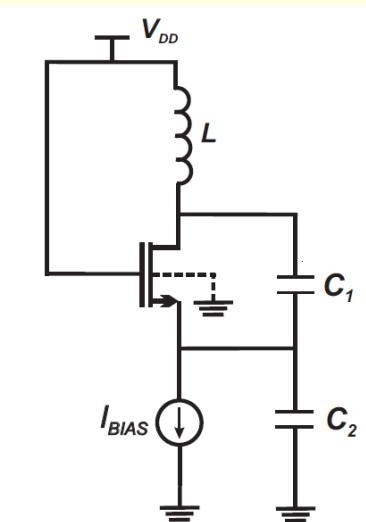The common-gate amplifier provides a voltage gain of greater than unity for $V_{DS}>0$. → Very useful property for lowering the supply voltage limit for the operation of oscillators (later).




Common- gate
Colpitts oscillator

Zero-VT MOSFETs - 1

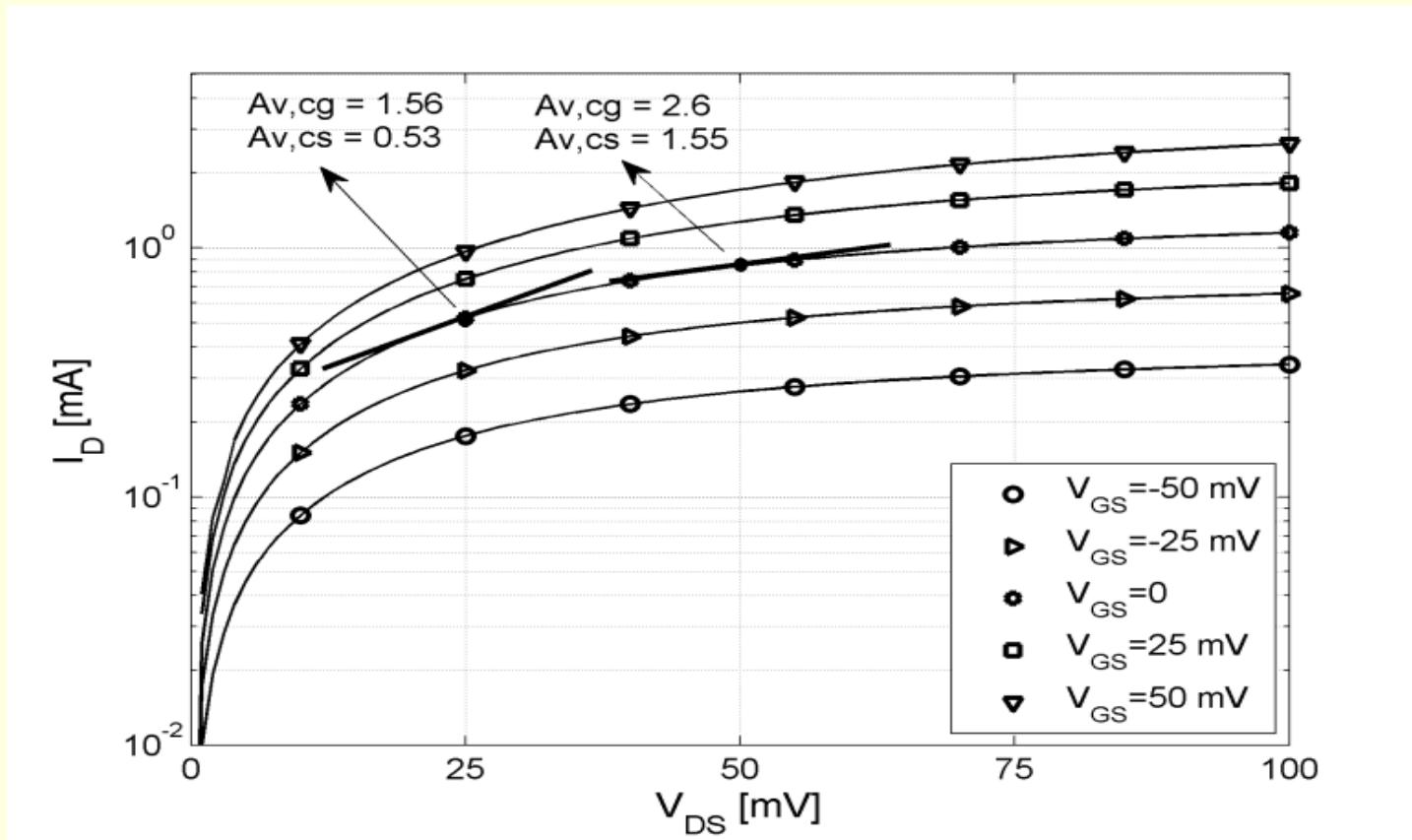



- $I_D \times V_{DS}$ ($V_S = V_B$) characteristics for a zero-VT transistor with $W/L = 2500\mu\text{m}/420\text{nm}$. The values of the common-gate and common-source gains are 1.56 and 0.53, respectively, for $V_{GS} = 0\text{ V}$ and $V_{DS} = 25\text{ mV}$.

Zero-VT MOSFETs - 2

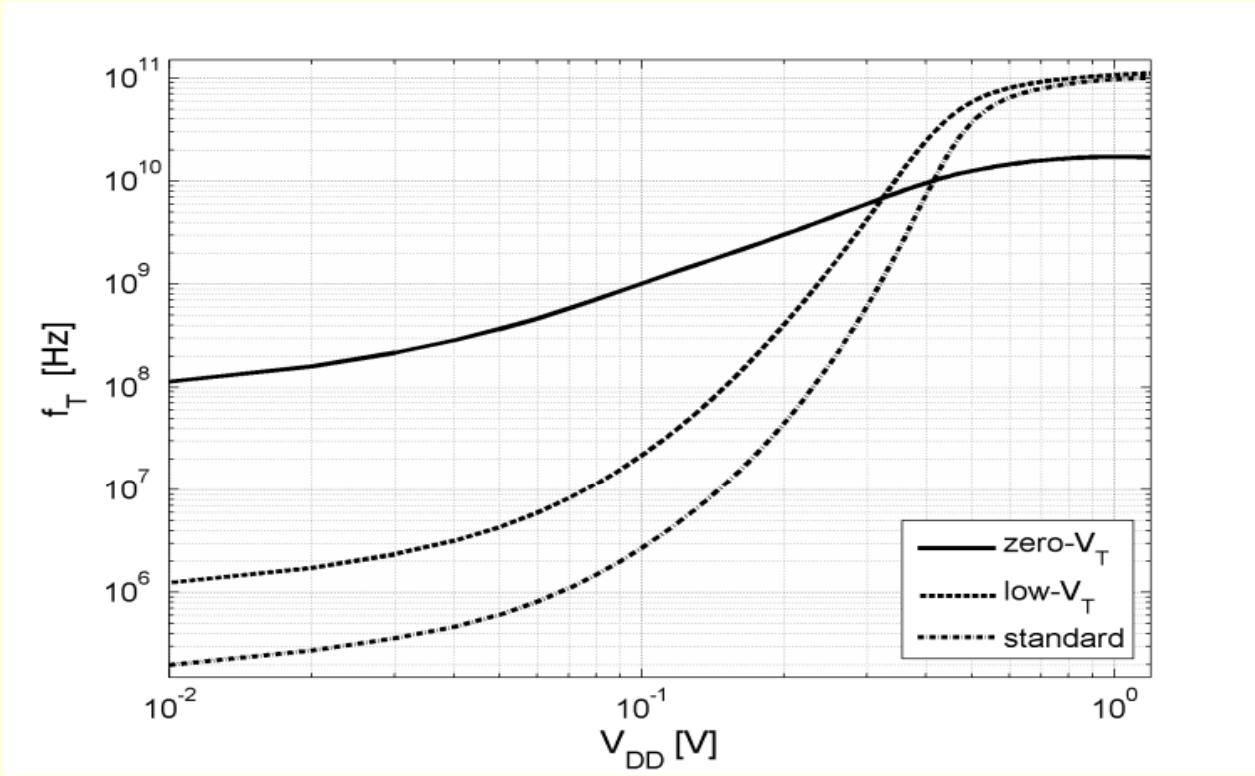

- First order approximation of the intrinsic cutoff frequency of the zero-VT ($W/L=3\mu m/0.42\mu m$), low-VT ($W/L=0.84\mu m/0.12\mu m$), and standard transistors ($W/L=0.84\mu m/0.12\mu m$) of a $0.13\mu m$ CMOS technology. The transconductance g_m was simulated for $V_S=V_B=0$, and $V_D=V_G=V_{DD}$.



Zero-VT MOSFETs - 3

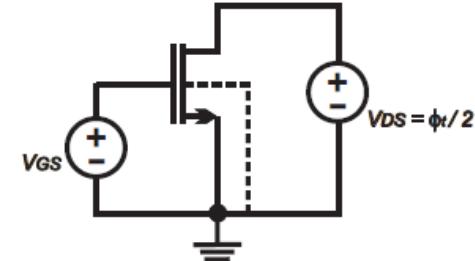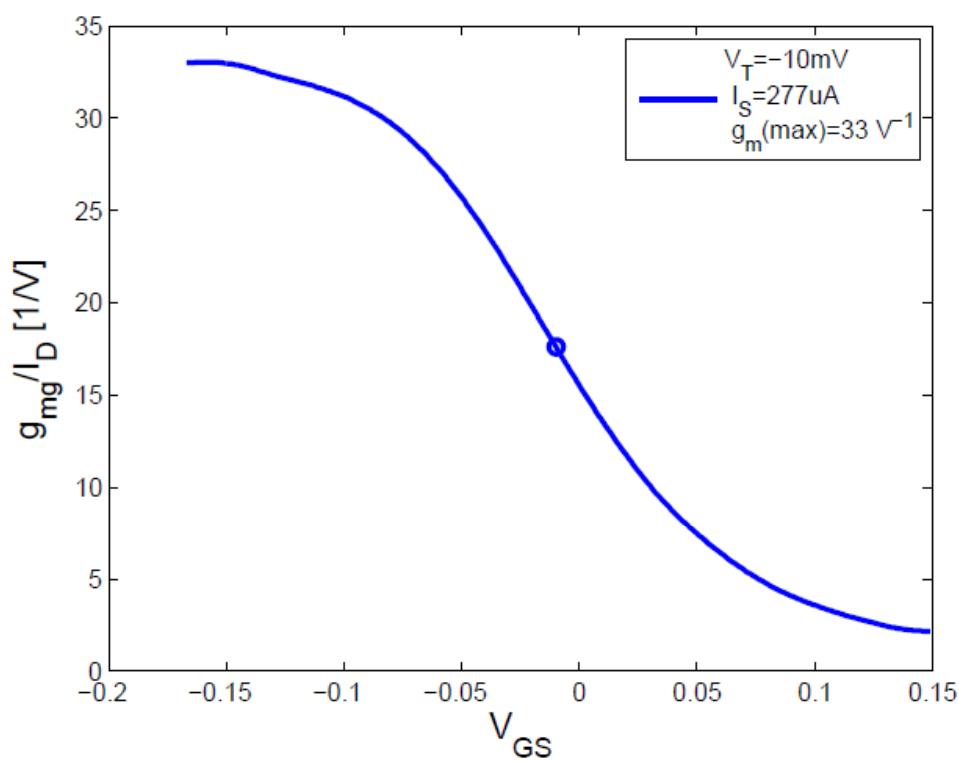

Circuit configuration for measuring the g_{mg}/I_D characteristic in the linear region

Experimental g_{mg}/I_D characteristic for a transistor with $W/L = 2500 \mu\text{m}/0.42 \mu\text{m}$


Zero-VT MOSFETs - 4

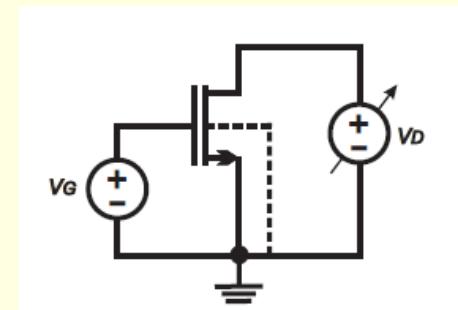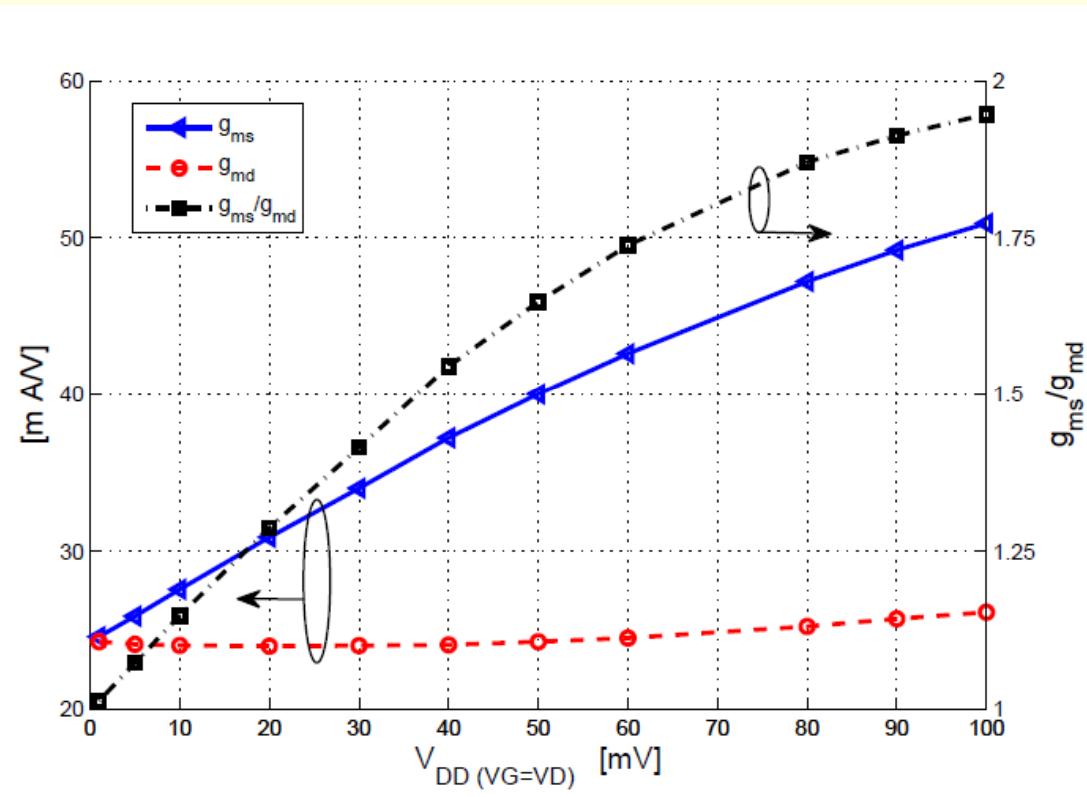


Circuit configuration for measuring g_{md}

g_{ms} , g_{md} and g_{ms}/g_{md} as functions of V_{DD} for a transistor with $W/L = 2500 \mu\text{m}/0.42 \mu\text{m}$

Colpitts oscillators

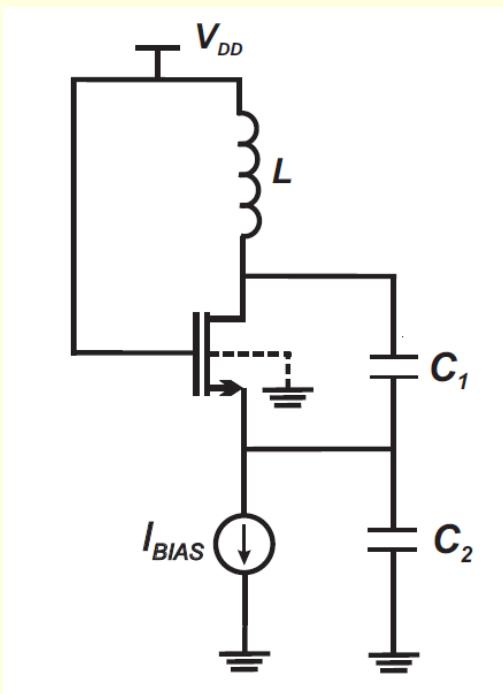


Conventional Colpitts oscillator

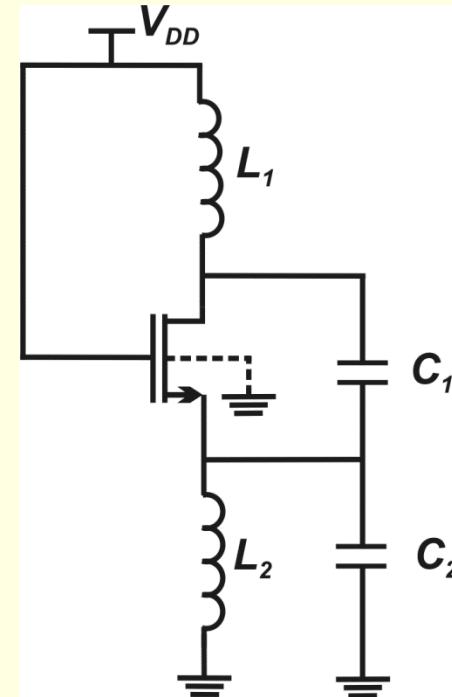

Enhanced swing Colpitts oscillator
(ESCO) *

* T. W. Brown et al, *IEEE JSSC*, Aug. 2011.



ESCO: small-signal model 1

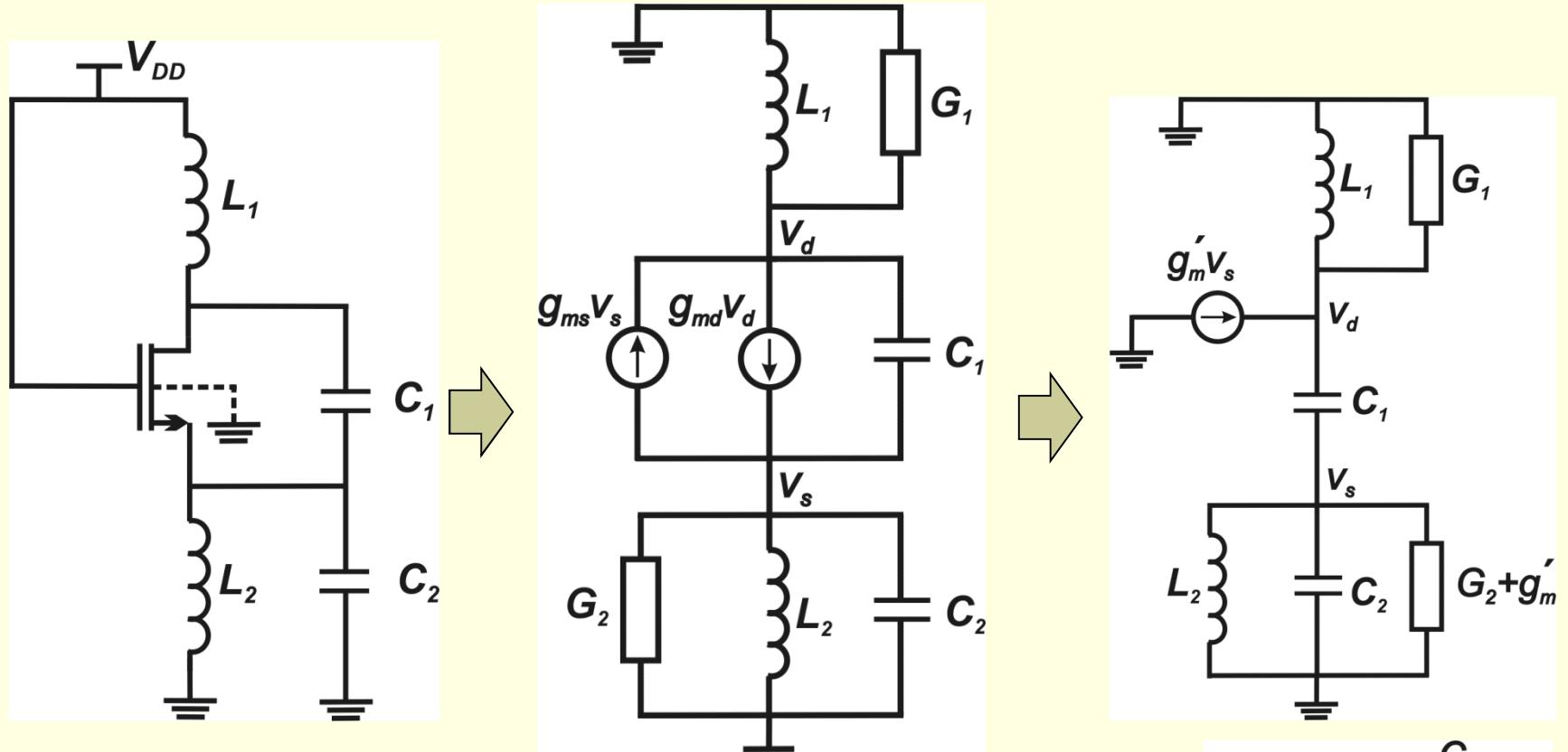

$$g'_m = g_{ms} - \left(1 + \frac{C_2}{C_1}\right)g_{md}$$

$$v_s \cong \frac{v_d}{1 + \frac{C_2}{C_1}} \rightarrow g_{ms}v_s - g_{md}v_d \cong g'_m v_s$$

ESCO: small-signal model 2

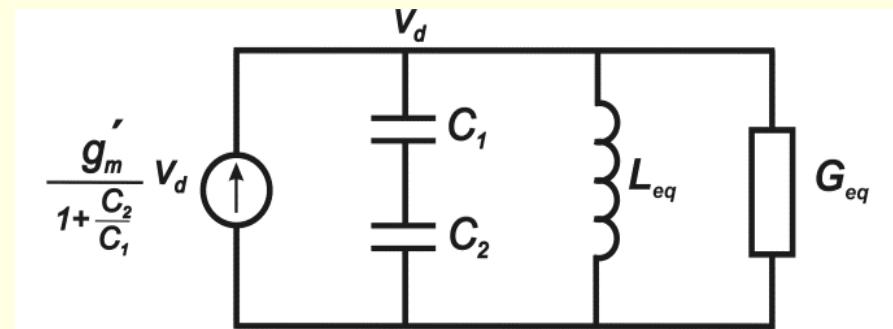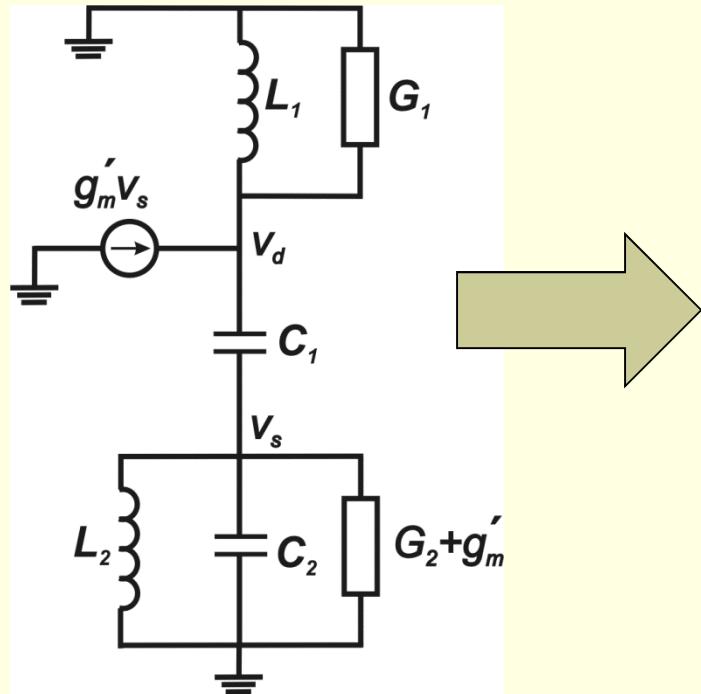


$$G_{eq} = G_1 + \left(\frac{C_1}{C_1+C_2} \right)^2 (G_2 + g'_m) \quad \frac{1}{L_{eq}} = \frac{1}{L_1} + \left(\frac{C_1}{C_1+C_2} \right)^2 \frac{1}{L_2}$$


Second-order small-signal model of the ES Colpitts oscillator.

ESCO: start-up condition
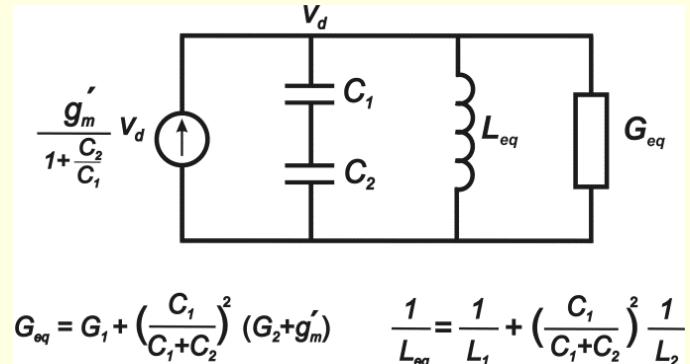
$$g_{ms} > \left(1 + \frac{C_2}{C_1}\right) g_{md} + \frac{C_1}{C_2} G_2 + \left(2 + \frac{C_1}{C_2} + \frac{C_2}{C_1}\right) G_1$$




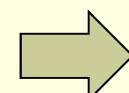Optimum value of capacitors
to minimize g_{ms} (for the conventional
Colpitts $g_{md} = G_2 = 0$!)




$$\frac{C_2}{C_1} = \sqrt{\frac{G_1 + G_2}{g_{md} + G_1}}$$

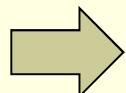For ideal inductors (and
capacitors) $G_1 = G_2 = 0$




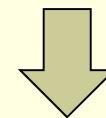
$$g_{ms} > \left(1 + \frac{C_2}{C_1}\right) g_{md}$$




$$V_{DD\lim} = \frac{kT}{q} \ln \left(1 + \frac{C_2}{C_1} \right)$$

Colpitts oscillator: first prototype

*Powered by a
thermoelectric generator*

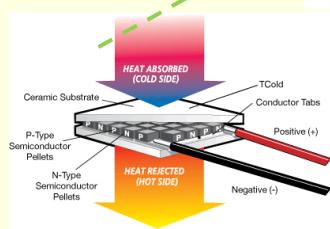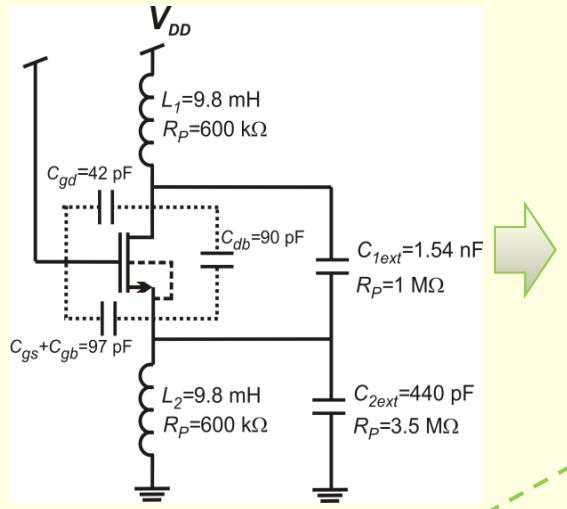




thermoelectric generator

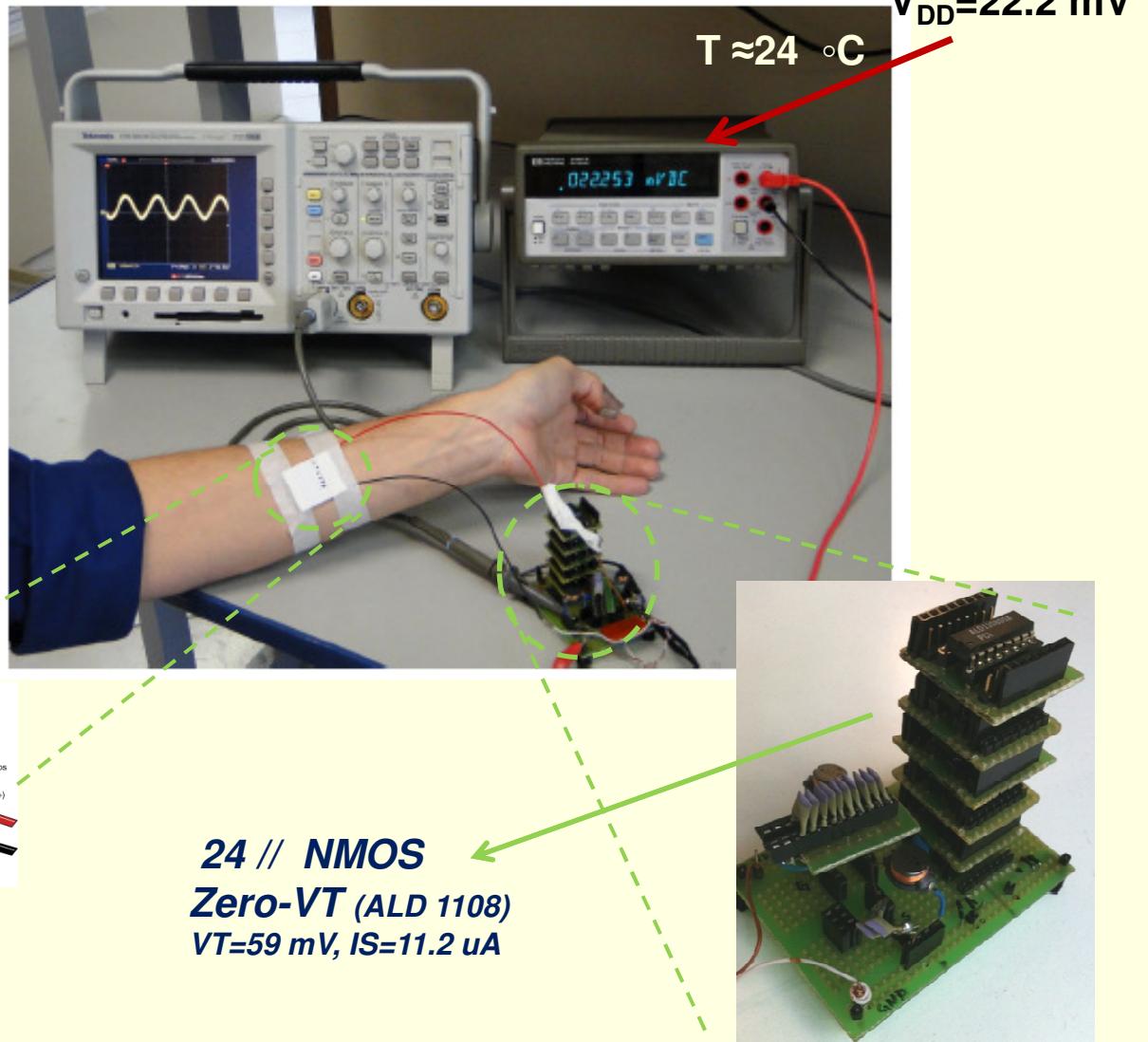

Colpitts oscillator: second prototype

$V_{DD} < 20 \text{ mV}$


Zero-VT
IBM 130 nm

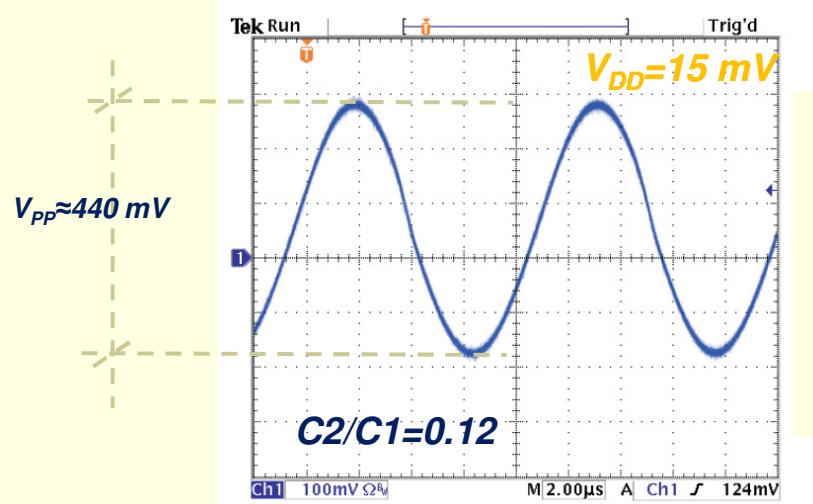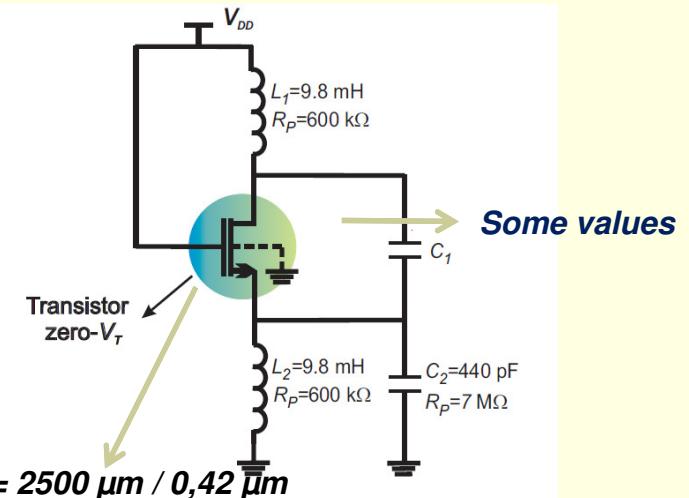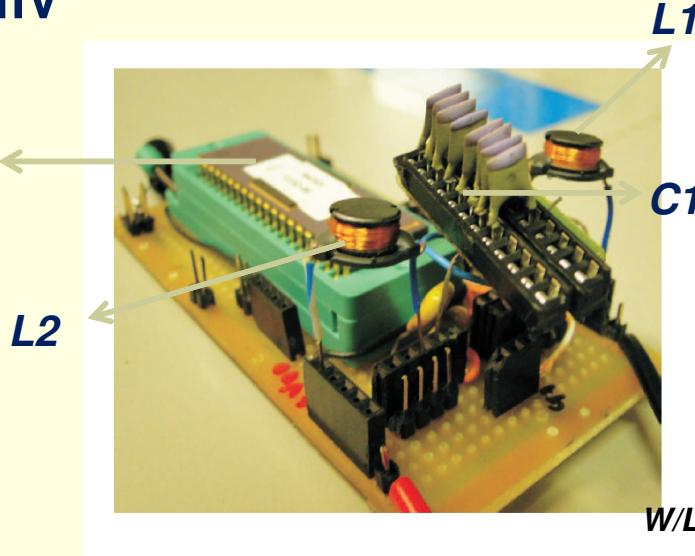

$f_{osc} \approx 110 \text{ kHz}$
 $V_{DD} = 15 \text{ mV}$


Second prototype: experimental results

$V_{DD,min} \times C2/C1$

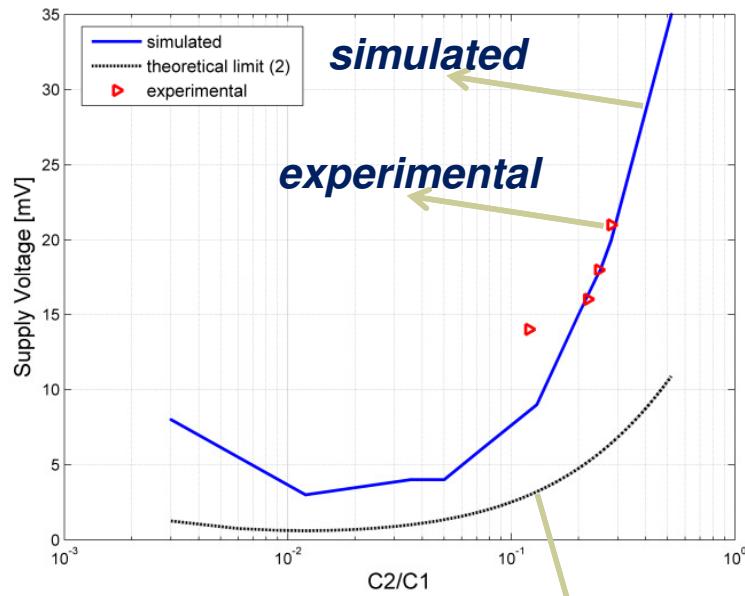


$f_{osc} \approx 110 \text{ kHz}$

weak inversion

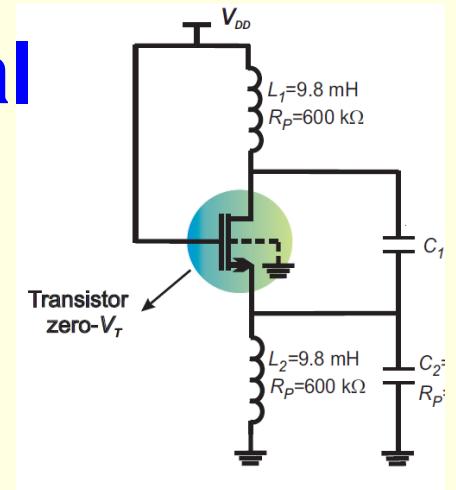


$V_{PP} \times V_{DD}$

calculated

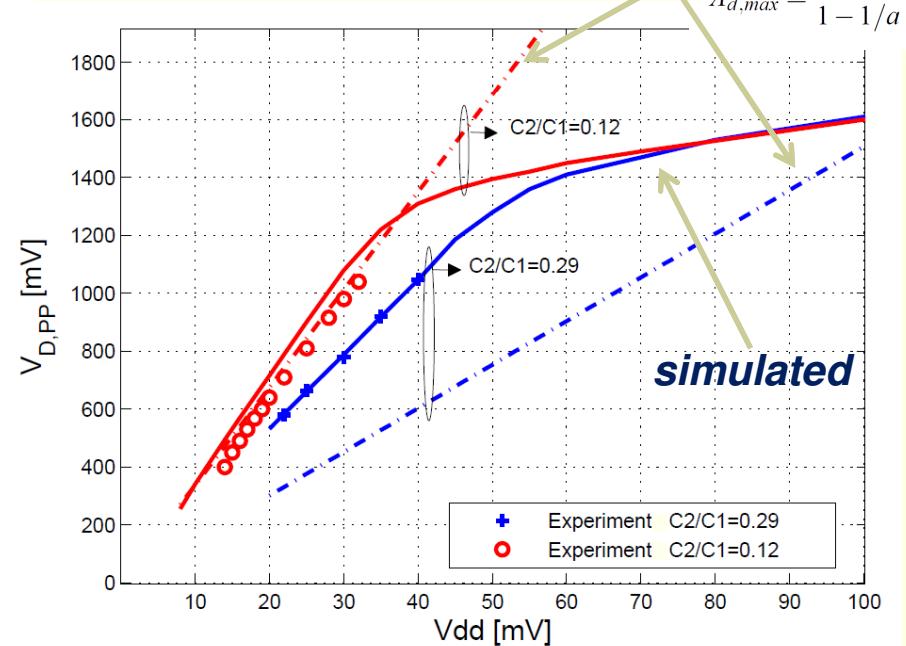


Colpitts oscillator IC: simulation results

Design : $f=300$ MHz

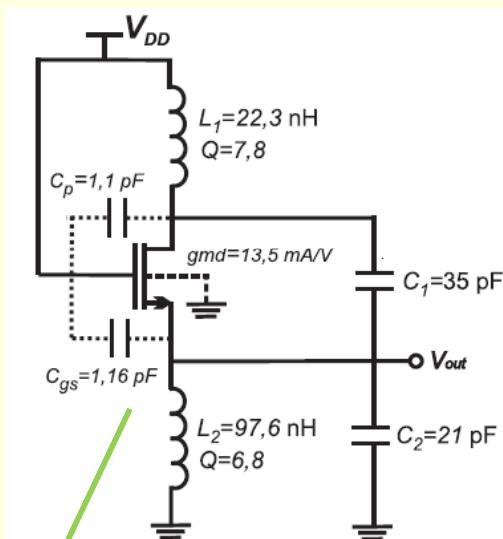

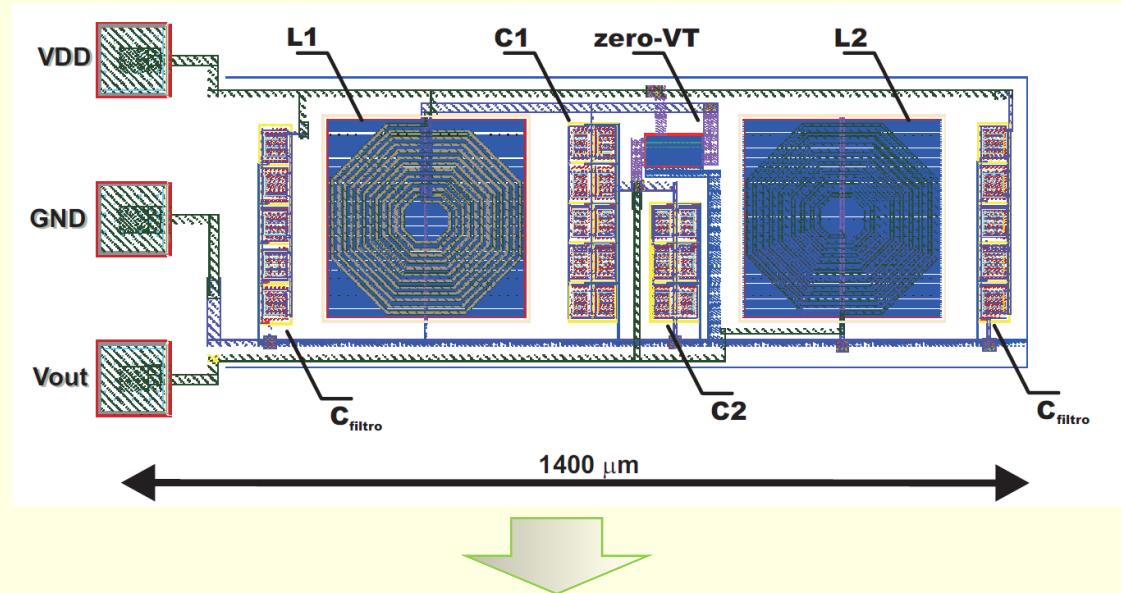
$W/L = 2500 \mu\text{m} / 0,42 \mu\text{m}$



Results (Simul. from layout)

Designed f	300 MHz
f	262 MHz
$V_{DD,min}$	86 mV
$V_{S,PP}$	23 mV
$V_{DD,max}$	650 mV

($V_{dd}=86$ mV)

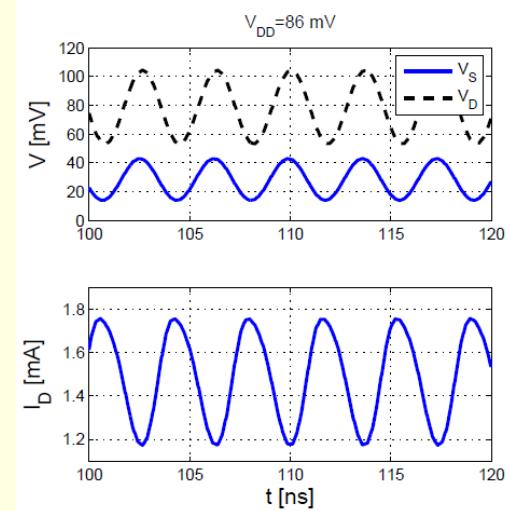

Summary

- There is no V_{DD} hard limit for low voltage operation of analog MOS circuits (oscillators can operate with supply voltage values below kT/q)
- The ideal active device for low voltage operation is characterized by small footprint and high drive capability at low supply voltages → MOSFETs with threshold voltage ~ 0 V are excellent choices for ULV operation
- The charge-based MOSFET model is very convenient for the design of ultra-low-voltage circuits (operation in triode region/ WI)

References

- F. R. de Sousa, M. B. Machado, C. Galup-Montoro, “A 20 mV Colpitts Oscillator powered by a thermoelectric generator”, *ISCAS 2012*.
- C. Galup-Montoro, M. C. Schneider, and M. B. Machado, “On the ultra-low-voltage operation of CMOS analog circuits: amplifiers, oscillators, and rectifiers’, to appear in IEEE TCAS II.