

1.5 Low-voltage ultra-low-power analog IC design — switched-MOSFET technique

Outline

- Introduction
- The basic Switched-MOSFET (SM) cell
- Why Switched-MOSFET
- Basic SM Integrators
- Universal SM Biquad
- Practical Issues
- Results
- Conclusions

ISCAS 2001 - Switched-MOSFET Technique 2

Sampled-data Circuits

Three basic elements may be used

Capacitors

Current Sources

Resistors

Switched-capacitor (SC)

Switched-current (SI)

Switched-resistor ?? (SR)

ISCAS 2001 - Switched-MOSFET Technique 4

Switched-MOSFET Sampled-Data Technique for Low-Voltage Supply

Luís Cléber C. Marques¹, Carlos Galup-Montoro,
Sidnei Noceti Filho, Fathi Farag, Wouter Serdijn²,
and Márcio Chereim Schneider

Universidade Federal de Santa Catarina (UFSC)/Brazil

¹ - Centro Federal de Educação Tecnológica de Pernambuco (CEFET-PE)/Brazil;
Currently in a cooperation with TU Delft, Boissière du CRPQ - Brazil.

² TU Delft, 2 - Delft University of Technology (TU Delft)/The Netherlands

ISCAS 2001 - Switched-MOSFET Technique 3

Introduction

```

    graph TD
      AC(Analog Circuits) --> CT(Continuous-time)
      AC --> DT(Discrete-time)
      DT --> CP(Charge Processing)
      DT --> CurP(Current Processing)
      CP --> SC(SC)
      CurP --> SI(SI)
      CurP --> SR(SR)
      CurP --> SM(SM)
    
```

ISCAS 2001 - Switched-MOSFET Technique 3



Sampled-data Circuits – Basic building blocks

Switched-capacitor (SC) Integrator

Switched-current (SI) Delay Cell

Switched-resistor (SR) Delay Cell

ISCAS 2001 - Switched-MOSFET Technique 5

Switched-resistor / Switched-MOSFET

$i_o = -[R_1/R_2]i_{in}$

$i_o = -[(W/L)_{M2}/(W/L)_{M1}]i_{in}$

ISCAS 2001 - Switched-MOSFET Technique 6

Why Switched-MOSFET ? (1) – Low-voltage operation

Conduction Gap of CMOS Switches

ISCAS 2001 - Switched-MOSFET Technique 7

Why Switched-MOSFET ? (1) – Low-voltage operation

Op_amp input stage

The maximum common-mode input voltage V_{CM} is around $V_{DD} - (|V_{Tnp}| + |V_{DSsat}|)$

ISCAS 2001 - Switched-MOSFET Technique 8

Why Switched-MOSFET ? (2) – Programmability

The MOSFET-Only Current Divider (MOCD)

Same potential

Digital word

$$a = \sum_{i=0}^{M-1} b_i 2^{i-M}$$

DUMP

ISCAS 2001 - Switched-MOSFET Technique 9

Generation of common-mode voltage

ISCAS 2001 - Switched-MOSFET Technique 10

Basic SM Integrators

1st Generation Integrator

$$\frac{I_{Ox}^+(z)}{I_{In}^+(z)} = -\alpha \frac{1}{1 - \beta z^{-1}}$$

$$\frac{I_{Ox}^-(z)}{I_{In}^-(z)} = \gamma \frac{z^{-1}}{1 - \beta z^{-1}}$$

ISCAS 2001 - Switched-MOSFET Technique 11

Basic SM Integrators


2nd Generation Integrator

$$\frac{I_{Ox}^+(z)}{I_{In}^+(z)} = -\alpha \frac{1}{1 + \beta z^{-1}}$$

$$\frac{I_{Ox}^-(z)}{I_{In}^-(z)} = \gamma \frac{z^{-1}}{1 + \beta z^{-1}}$$

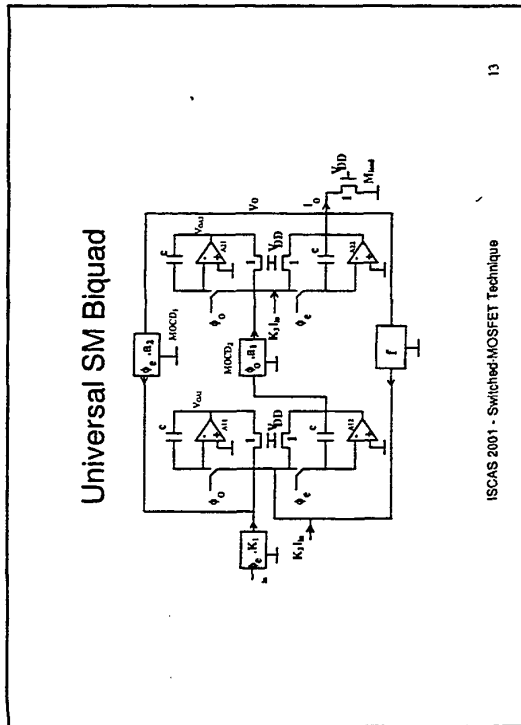ISCAS 2001 - Switched-MOSFET Technique 12





First Conclusions

1. SM does not need any special process or voltage doubler;
2. SM allows independent digital programming of the filter center frequency (f_0), quality factor (Q) and gain.
3. Programming is not area demanding.

♣ The SM technique is adequate for the implementation of programmable filters at low-voltage supply.

ISCAS 2001 - Switched-MOSFET Technique

14

Some practical issues

- 1 - SM technique relies on opamps. Opamp GBW > 3.5 fs (same as for SC circuits) and $AV_{(DC)} > 77$ dB (linear - easily achievable) for THD < 0.1% (sinusoidal signals).
- 2 - Charge injection will give rise to harmonic distortion. The nonlinearity of the output current is dependent on both the Q-to-V conversion of the holding capacitor and the V-to-I conversion of the MOSFET. Therefore, switches should be minimum-size.
- 3 - In the SM technique, there are no "natural" integrators as in SC circuits. In SC circuits the integrator (non-switched capacitor in the feedback loop of an op amp) is the "natural" element while current amplifier is the "natural" element of the SM technique. Integrators of the SM technique are implemented by feeding back a fraction of the output current to the input. As a consequence of the operating principle of the SM technique, the offset of filters is not as easily compensated as in SC circuits.

ISCAS 2001 - Switched-MOSFET Technique

15

Some practical issues

- 4- Offset-compensating schemes may be used. In this case, the compensating capacitor contributes to total noise in the same way as holding capacitor, and thus cannot be made very small.
- 5 - Opamps must drive resistive loads. Hence, opamps with class AB output stage should be employed in order to avoid large power consumption.

ISCAS 2001 - Switched-MOSFET Technique

16

Some practical issues

Offset Compensation

ISCAS 2001 · Switched-MOSFET Technique

17

Some practical issues

Offset Compensation / Clock Generation

ISCAS 2001 · Switched-MOSFET Technique

18

Some practical issues

V/I and I/V Converters

ISCAS 2001 · Switched-MOSFET Technique

19

Some Results

Circulating FIR Structure

$$y(n) = h_1 x(n) + h_2 x(n-1) + h_3 x(n-2) + h_4 x(n-3)$$

ISCAS 2001 · Switched-MOSFET Technique

20



