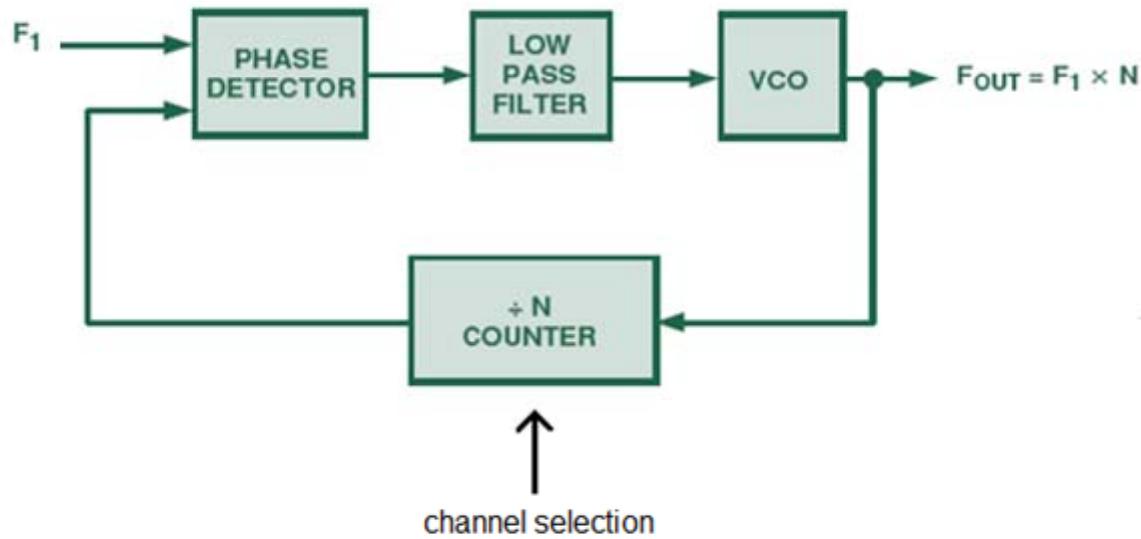


# PRESCALERS

*Frequency Synthesizers*



Using a reference counter in a PLL synthesizer


resolution:  $F_1$



## Synchronous vs. asynchronous counters (high-frequency)

Synchronous counters

- consume large power
- represent large CLOAD to oscillator
- race problems




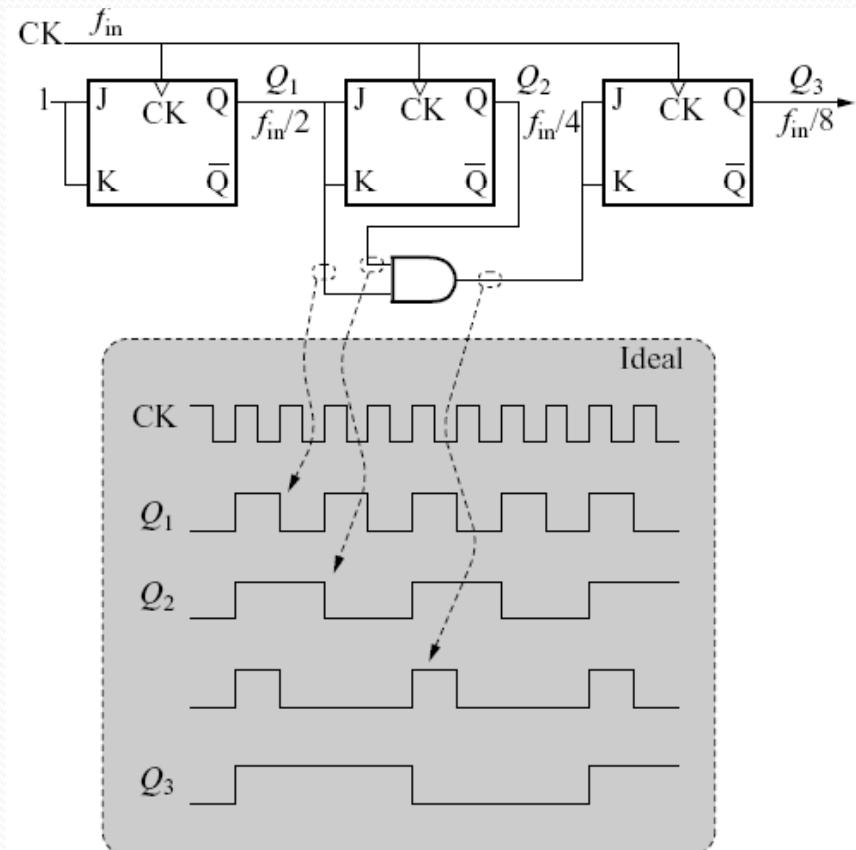
Ex: if Q2 is slower to go to 0 than Q1 to go to 1, the output of the AND gate experiences glitches.



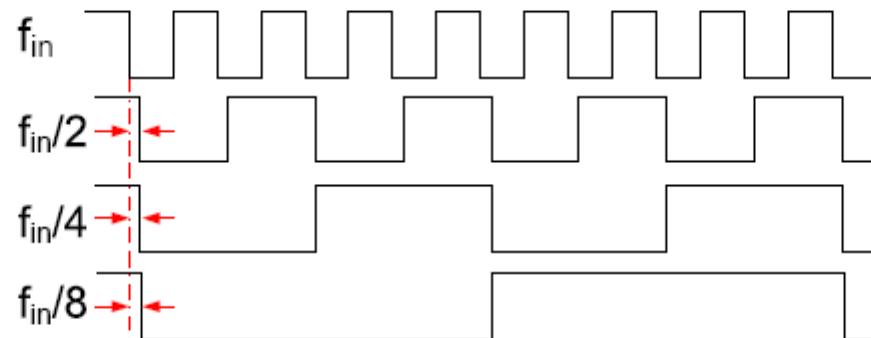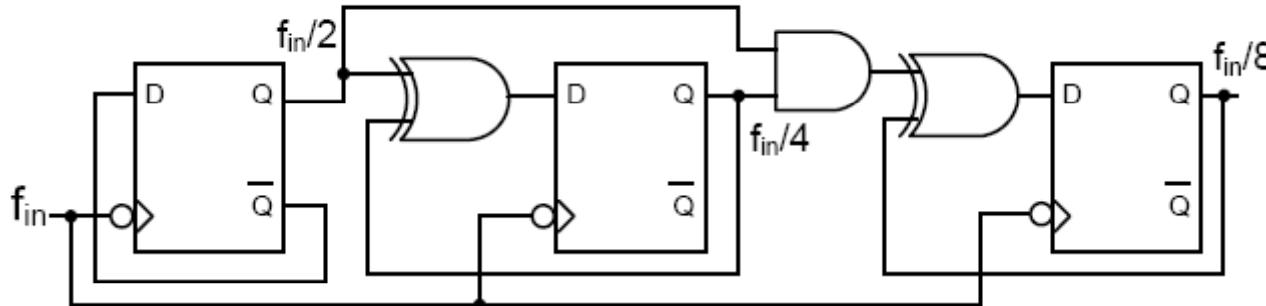


Synchronous counter

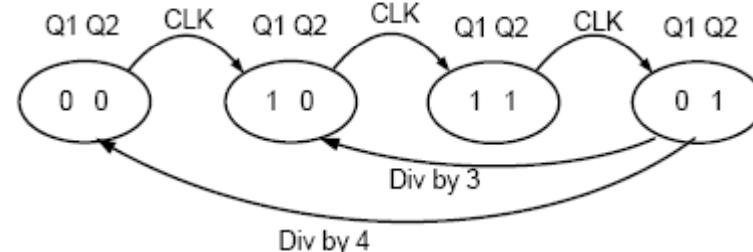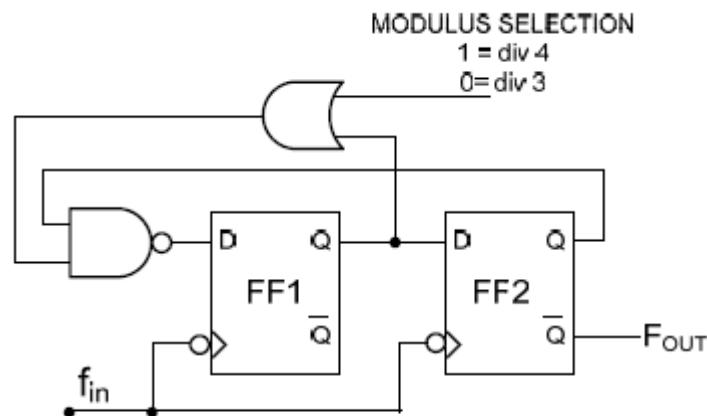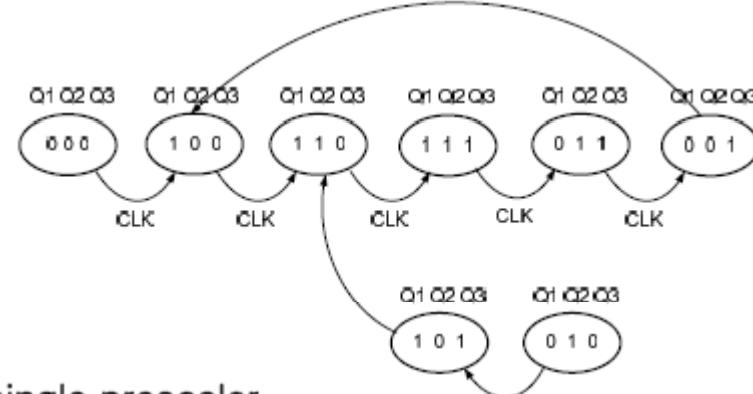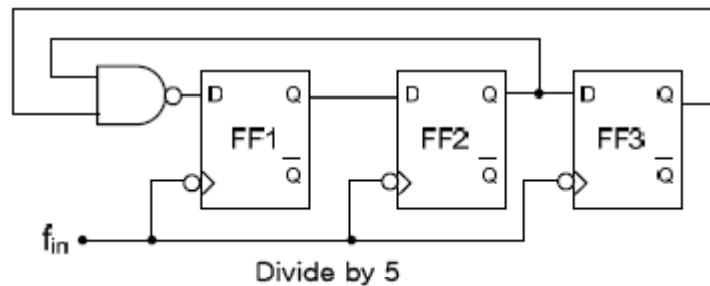- delay almost constant between the input clock and the output at the divided frequency (NOT proportional to no. of flip-flops)





Dual 3/4 prescaler and state diagram

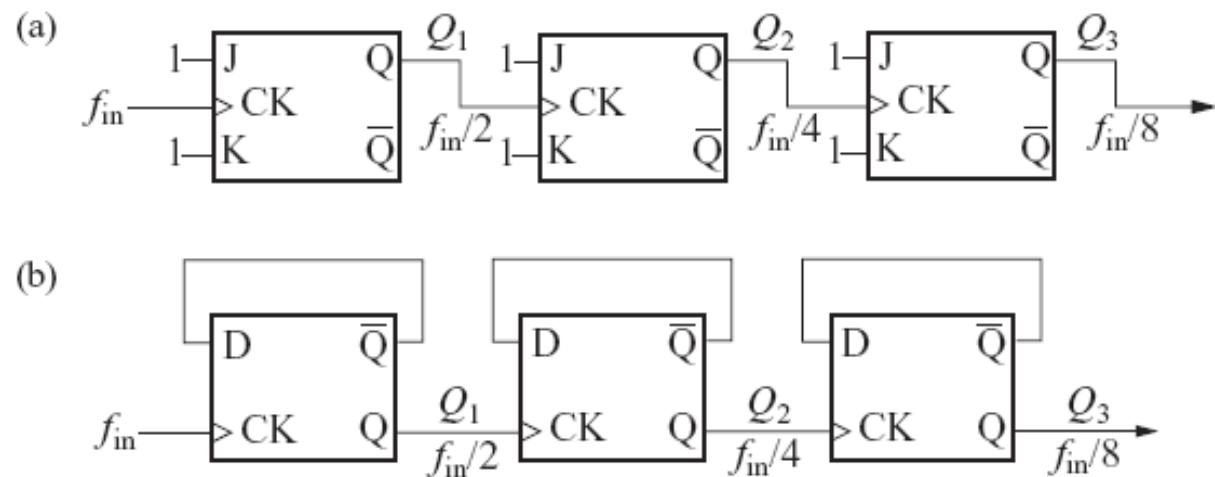asynchronous counters  $\Rightarrow$  preferred option for high-frequency



Asynchronous counters: (a) cascade of toggle flip-flops and (b) cascade of modulo-2 Johnson counters

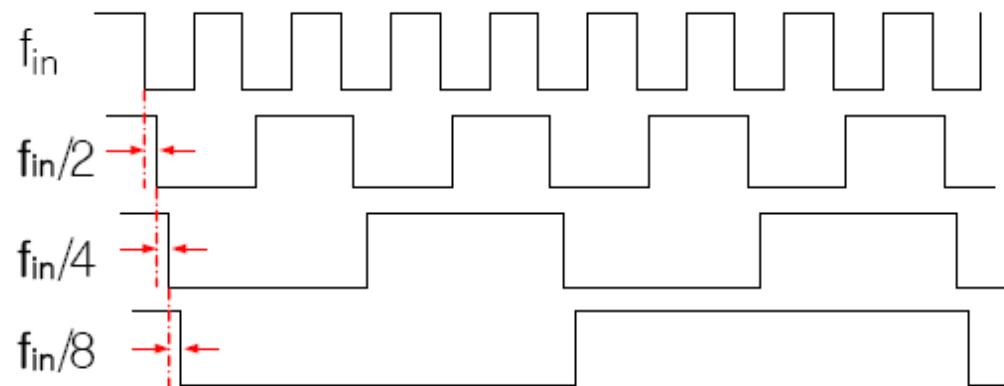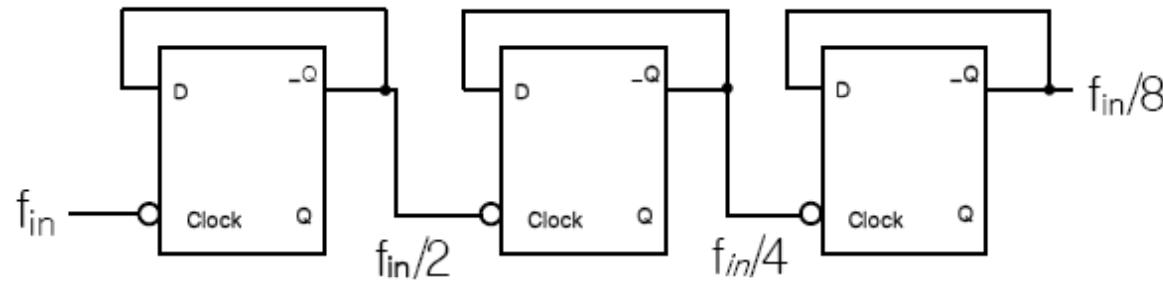
- forward/backward counting
- power consumption is reduced, as each stage operates at half frequency of previous stage



Asynchronous ripple counter

- delay is however added between the input clock and the output at the divided frequency (**proportional** to no. of flip-flops)

## Programmable dividers

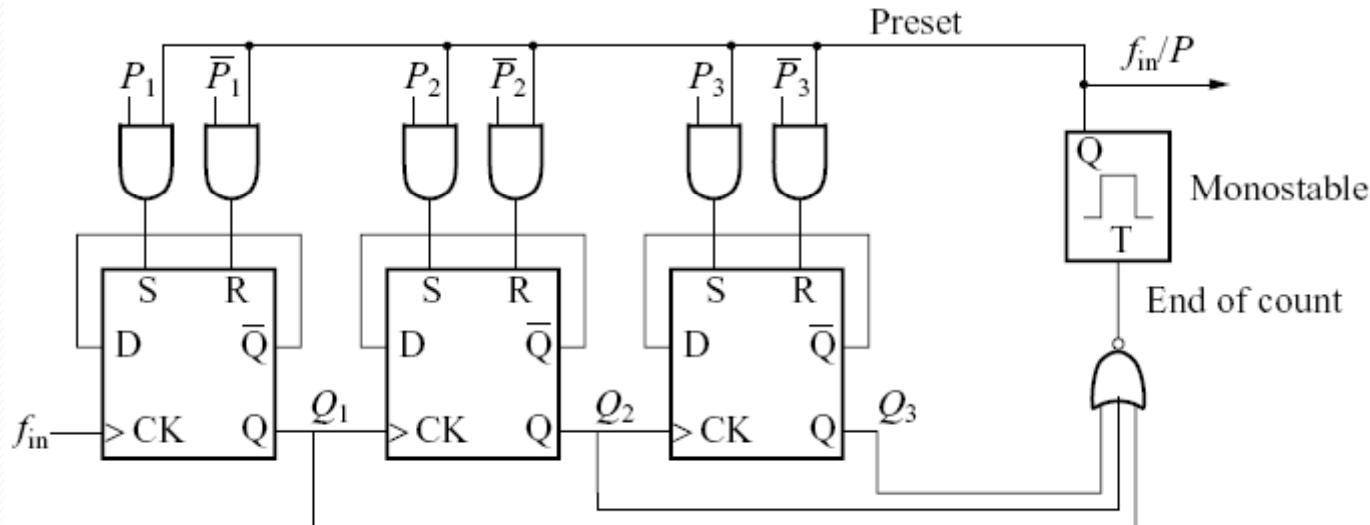


Presetable modulo- $P$  asynchronous counter (modulus-8 with backwards counting from  $Q_3Q_2Q_1 = 111$  to 000)

Basic principle: to preset counter to a initial state P and detect final state F by means of an ‘end-of-count’ EOC logic  $\Rightarrow$  the counter counts down between P and F

- limitation is max  $f_{in}$  as correct operation is guaranteed if EOC signal presets the counter before the next clock edge arrives

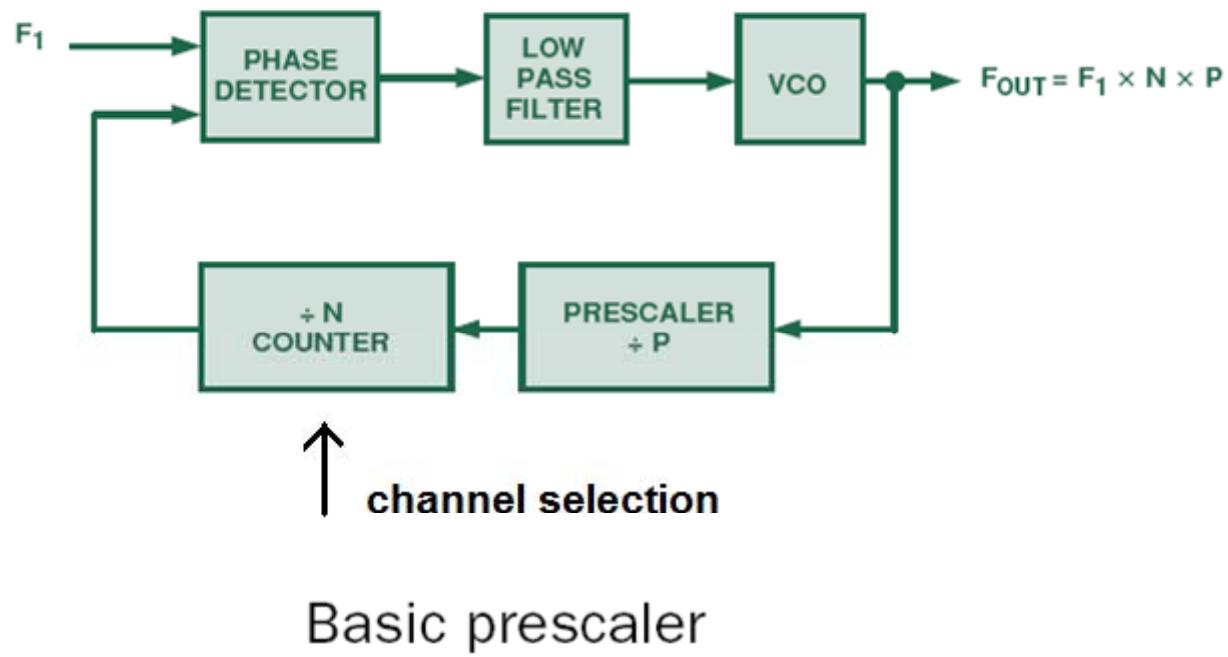- i) High-frequency operation is attained when logic function is kept simple
  - i) simplest dividers divide by fixed numbers
- ⇒ programmable divider could have a fixed-modulus high-speed divider as first stage
- If a pre-settable modulus-P divider follows a modulus-N prescaler, overall frequency division ratio is NxP.
  - the input frequency has to be lowered exactly by P to keep same resolution  
⇒ implies narrowing the PLL loop bandwidth, which may be undesirable!



resolution degraded:  $P \times F_1$

## Pulse Swallowing Technique

- If  $S$  input pulses are swallowed the output period becomes longer by  $S$  reference periods

$\Rightarrow$  overall frequency division-ratio is  $M = (NP + S)$ , which can be varied in unity steps by changing  $S$


$$M_1 = (NP + S)$$

$$M_2 = (NP + S+1)$$

$$\Rightarrow \Delta M = M_2 - M_1 = 1 \text{ (same resolution without prescaling!)}$$

## asynchronous counter

*high-speed*

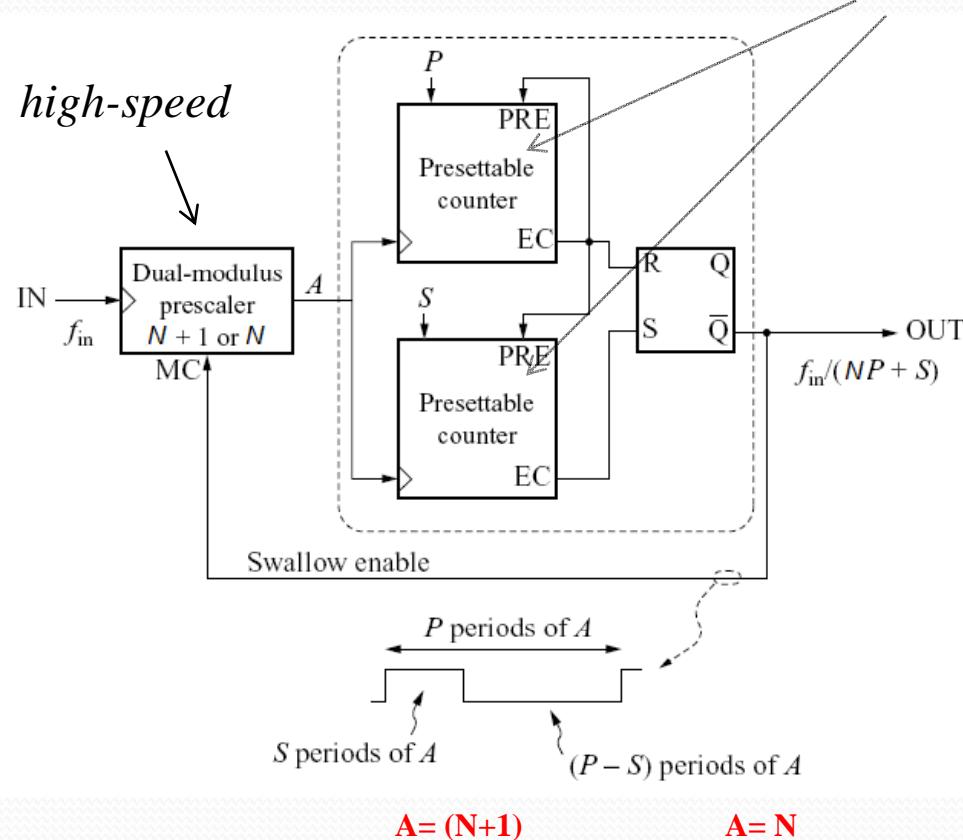


Programmable divider based on pulse swallowing.

- at beginning of counting,  $N+1$  factor is selected in dual-modulus prescaler ( $OUT = 1$ )
- $P$  and  $S$  count in parallel, with  $P > S$
- when  $S$  overflows, set = 1 and  $OUT \rightarrow 0$
- $N$  factor is selected in dual-modulus prescaler
- it remains like that until  $P$  overflows and  $OUT \rightarrow 1$
- cycle is restarted.

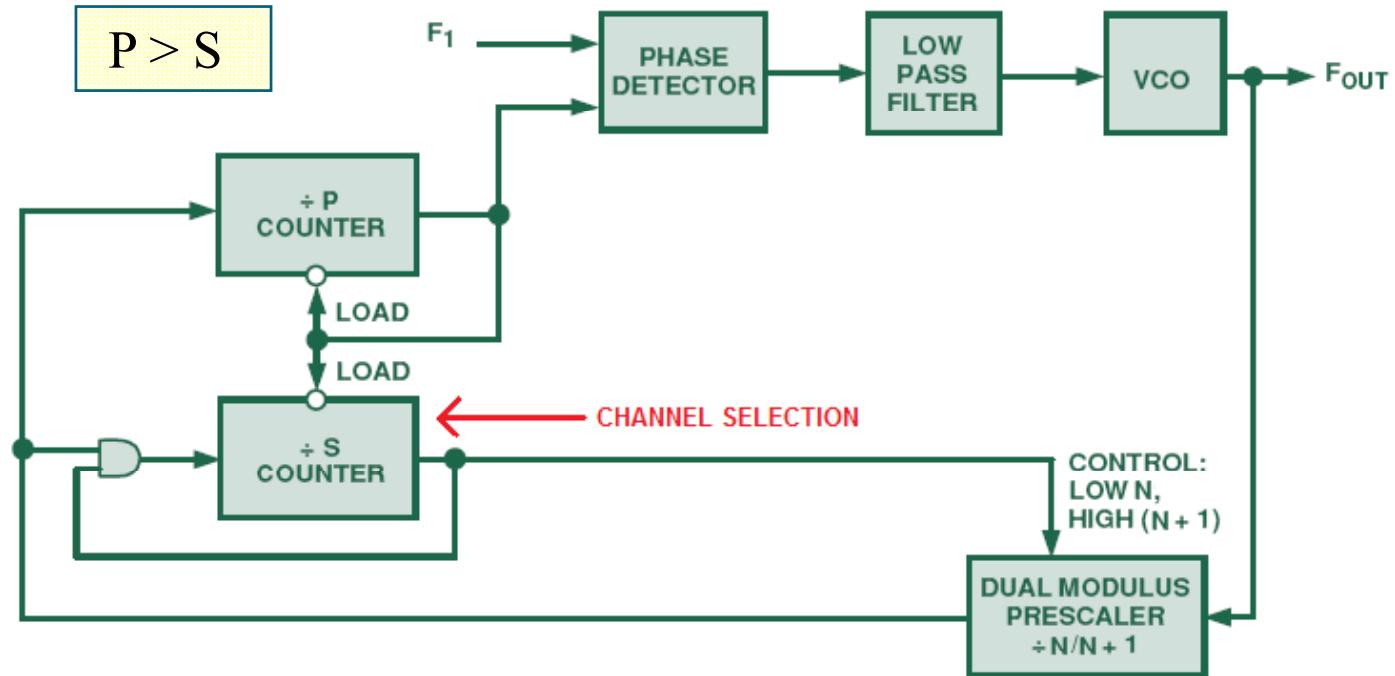**total counts of  $F_{out}$  is a full  $F_1$  cycle:**

$$\begin{aligned}
 & S \times (N+1) + (P-S)N \\
 & SN + S + PN - SN \\
 & PN + S = M
 \end{aligned}$$



frequency synthesizer with pulse swallowing technique

total counts of  $F_{out}$  is a full  $F_1$  cycle:

$$\begin{aligned} S \times (N+1) + (P-S)N \\ SN + S + PN - SN \\ PN + S = M \end{aligned}$$

Ex 1 (using pulsing swallowing):

- frequency synthesizer in 2400–2480 MHz ISM band
- 1 MHz channel spacing  $\Rightarrow$  division factor ( $M = NP + S$ ) between 2400–2480

*Design steps:*

- i) choice of the modulus  $N$  (*dual-modulus prescaler*),  $P$  (*program counter*) and  $S$  (*swallow counter*), with  $P > S$
- ii) assume that only S can vary to simplify channel-select logic.
- iii) make either  $N$  or  $N + 1$  a power of two
- iv) choose  $S$  as low as possible so that  $P > S$  is a minimum

Assuming initially S varies between 1 and 81 (to cover 81 possible division ratios) then P > 81:

$$N < \frac{M-S}{P} = \frac{2399}{81} = 29.6$$

Choosing N = 16  $\Rightarrow$   $P = \frac{M-S}{N} = \frac{2399}{16} = 149$  and  $P > S$

*Design values for pulse swallower*

N	P	S	M	P > S
16	149	16	2400	TRUE
16	149	96	2480	TRUE
32	75	0	2400	TRUE
32	75	80	2480	<b>FALSE</b>
32	76	48	2480	TRUE
22	109	2	2400	TRUE
22	109	82	2480	TRUE
9	256	96	2400	TRUE
9	256	176	2480	TRUE

$$M = (P \times N) + S$$

$$\begin{aligned} M_{MIN} &= (P_{min} \times N) + S_{min} \\ &= ((N+1) \times N) + 1 \\ &= N^2 + N + 1 \end{aligned}$$

$$M_{MAX} = (P_{max} \times N) + S_{max}$$

$P_{max}$  and  $S_{max}$  are determined by the size of P and S counters.

$M_{MIN}$ - $M_{MAX}$ : range over which it is possible to change N in discrete integer steps.

Ex2: assume that prescaler is programmed to  $N/N+1 = 32/33$

S counter: 6 bits means S can be  $2^6 - 1 = 63$

P counter: 13 bits means P can be  $2^{13} - 1 = 8191$

$$M_{MIN} = N^2 + N + 1 = 1057$$

$$M_{MAX} = (P_{max} \times N) + S_{max}$$

$$= (8191 \times 32) + 63 = 262175$$

If  $F_1 = 10\text{KHz}$  and  $P = 6000$ ;  $S = 40$

$$F_{OUT\_MIN} = 1.057\text{GHz}$$

$$F_{OUT\_MAX} = 2.62\text{GHz}$$


$$F_{OUT} = F_1 (PN + S) = 10\text{KHz} (6000 \times 32 + 40) = 1.92040\text{GHz}$$

$$F_{OUT1} = F_1 (PN + S+1) = 10\text{KHz} (6000 \times 32 + 41) = 1.92041\text{GHz}$$



$$\Delta F_{OUT} = 10\text{KHz}$$
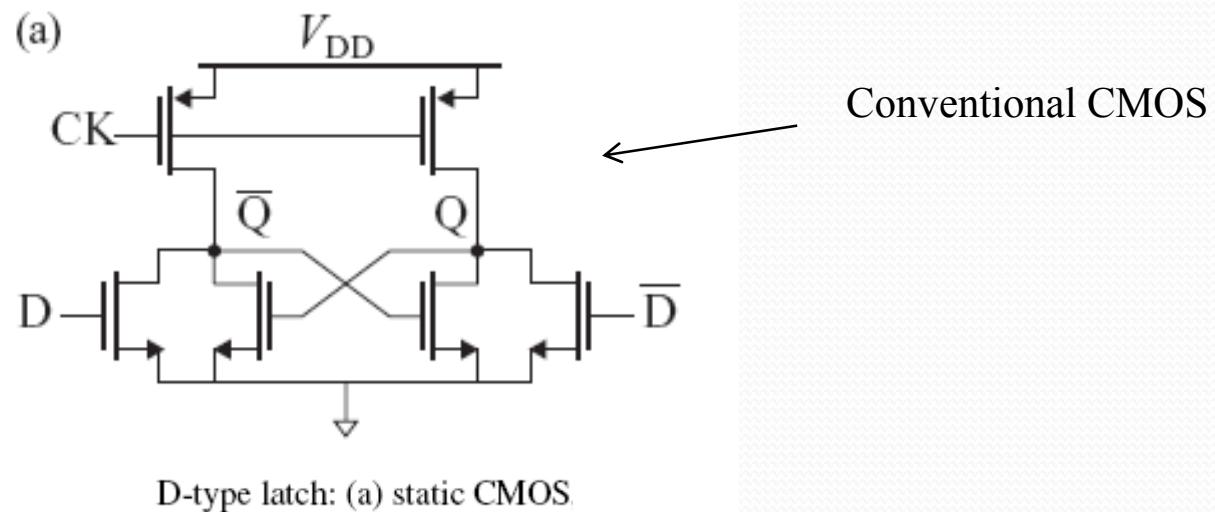
## (Differential) CMOS Current Mode Logic - (D)CML

- The main building block of the before-described counters is the D-type level-triggered latch




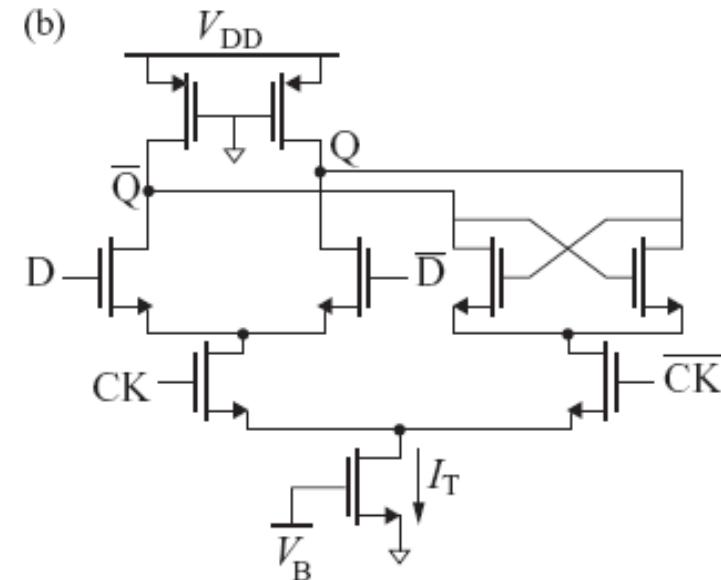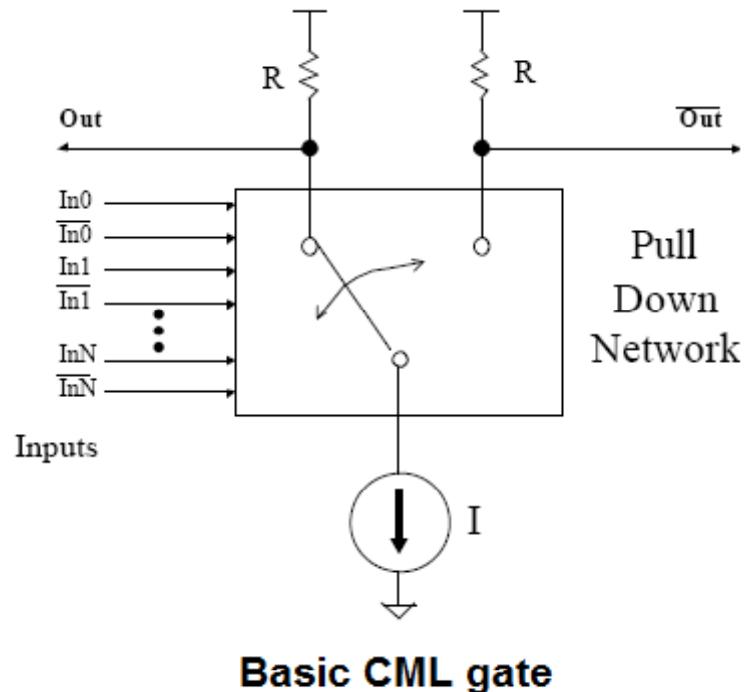- CK swing has to be wide enough ( $V_{TH} + V_{GO}$ ) to turn on pMOS. Since CK has a finite slope, this implies a certain delay before the latch is able to sense at CK transition  
⇒ Differential CML for high-speed processing





- CML is based on the use of differential stages
- tail current is switched between two branches by CK
- a regenerative pair holds the data when CK is low
- loads can be triode-operating or diode-connected PMOS.

## Single-Ended vs Differential

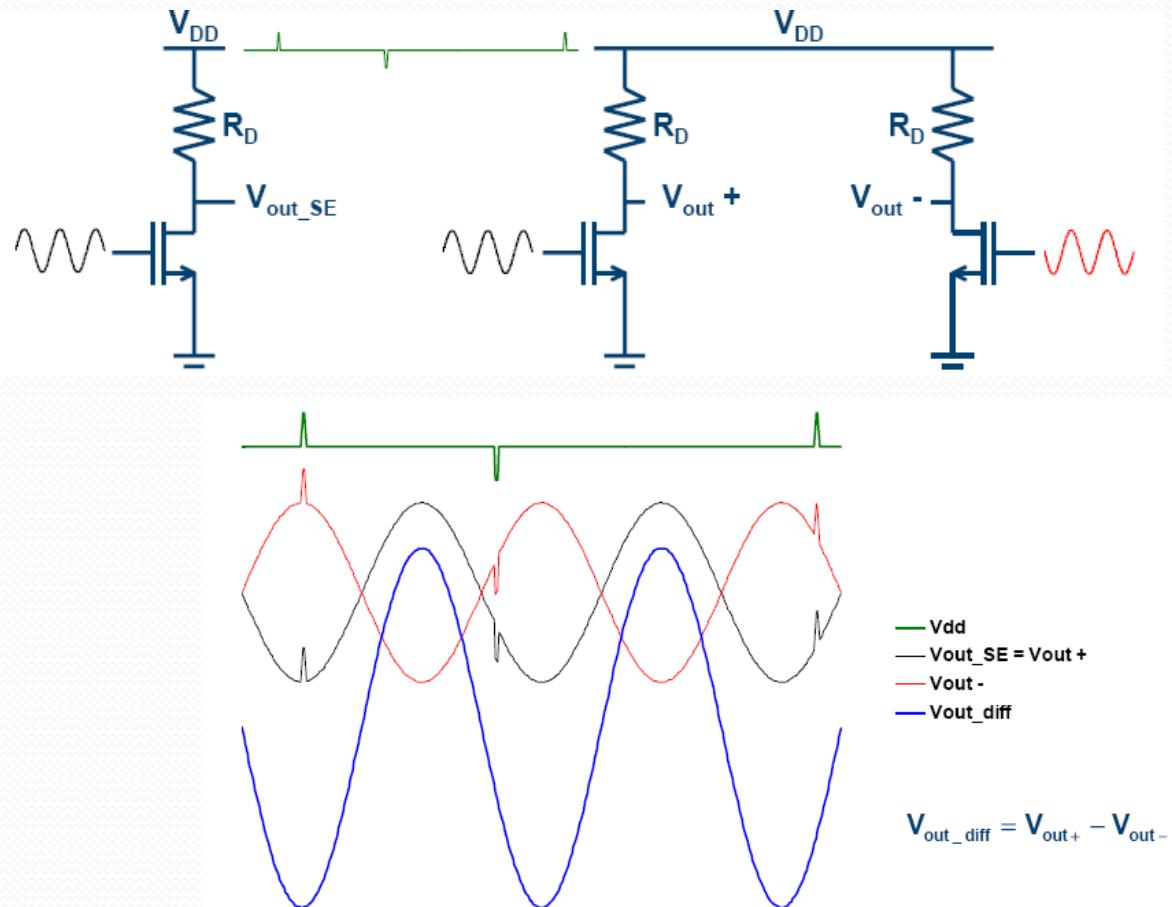

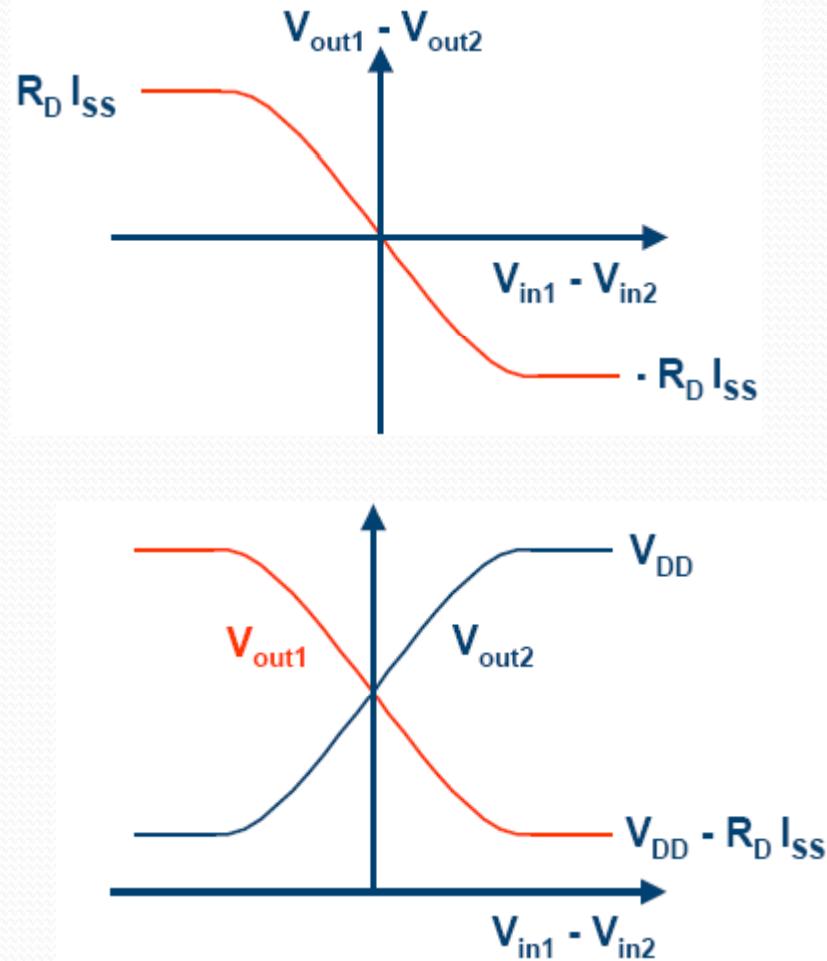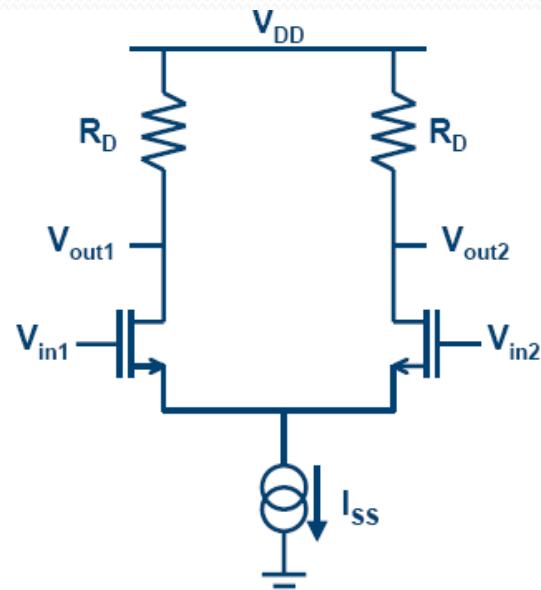Common-Mode disturbances disappear in the differential output



- small  $\Delta V_{in}$  already develops full  $V_{out}$

## CML x CMOS


### Pros:

- i) reduced voltage swing ( $V_{GO}$  against  $V_{GO} + V_{TH}$  of CMOS stages)  $\Rightarrow$  less delay before input sensing  $\Rightarrow$  higher speed
- ii) current-steering operation: current drained from supply less variable
- iii) differential circuits are immune to coupled disturbances; they reject disturbances coming from substrate and power supply due to other blocks

### Cons:



- i) larger area
- ii) 2 “wires” per signal
- iii) higher consumption

## - Emitter-Coupled Logic (origin)

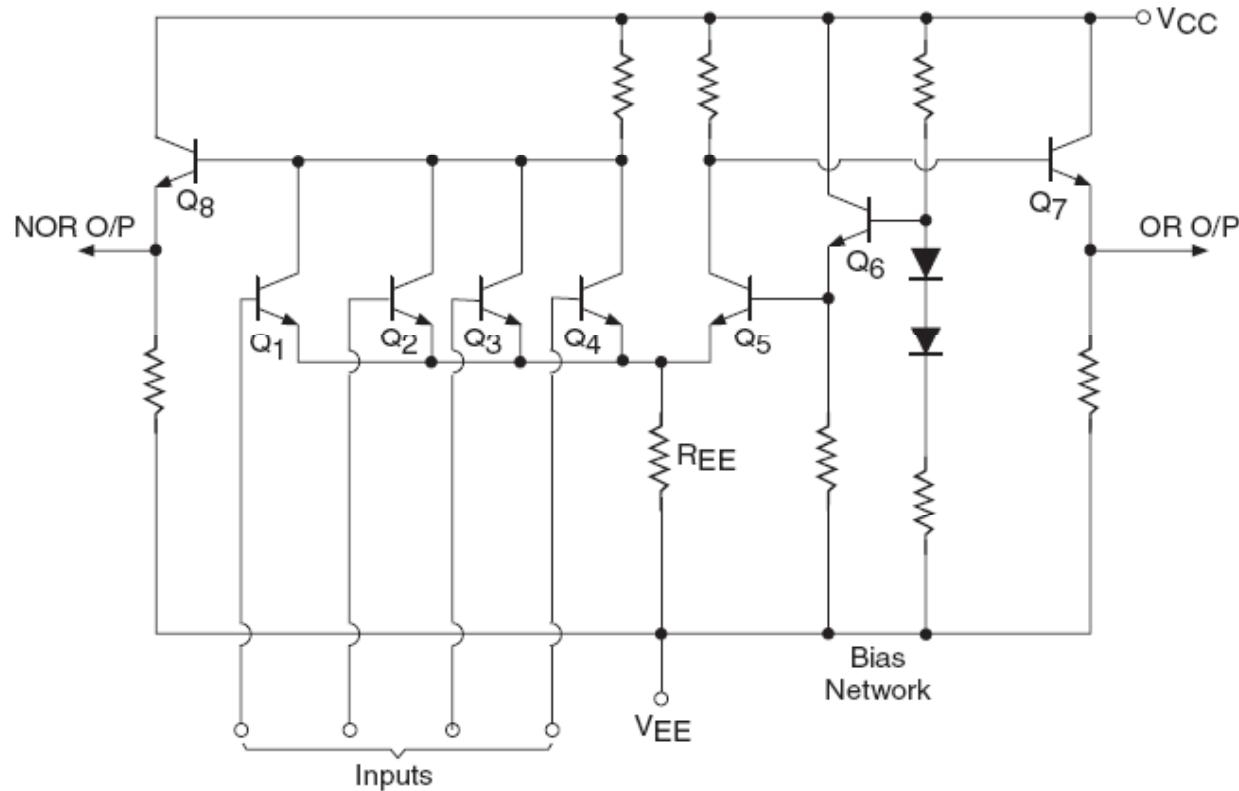


OR/NOR in ECL.

## - Emitter-Coupled Logic

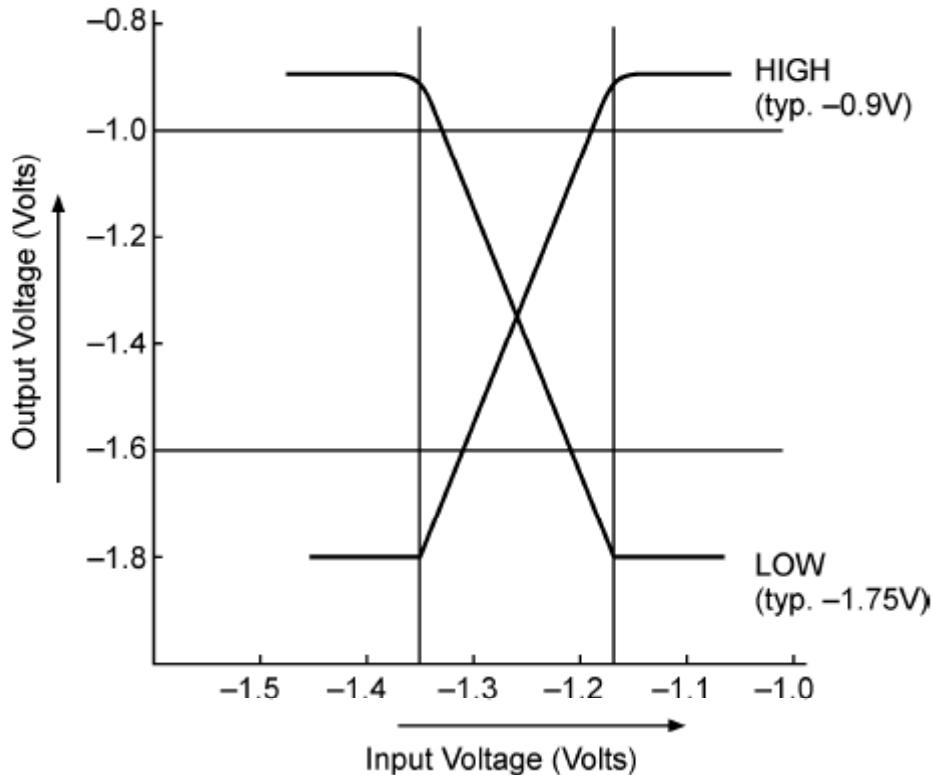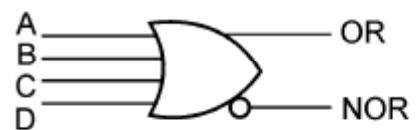


ECL input/output characteristics.

## CML AND / NAND gates

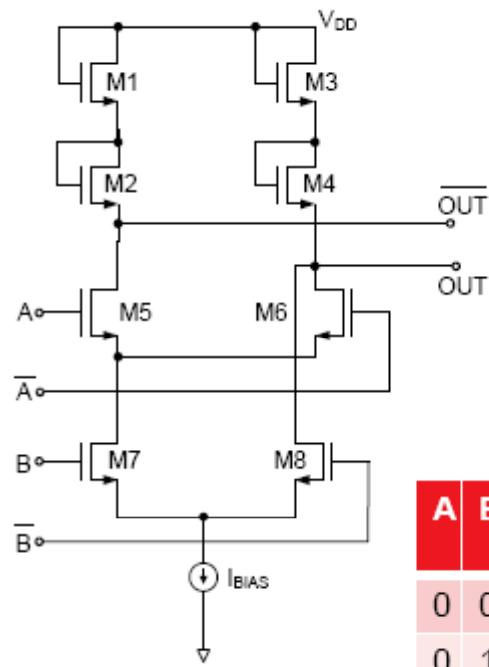

AND



A	B	out	out-not
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0


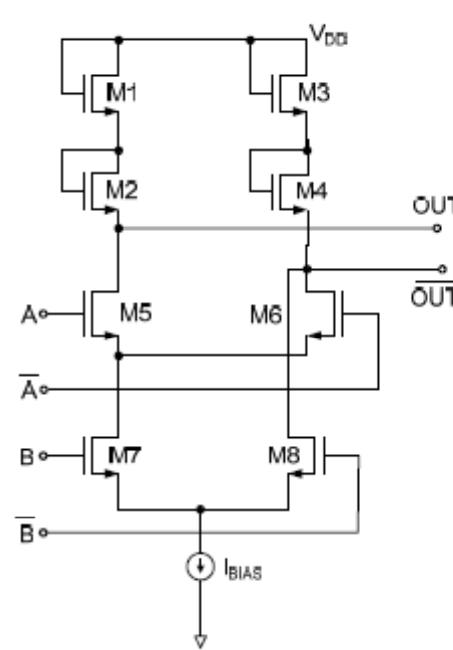


NAND


A	B	out	out-not
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

## CML OR / NOR gates

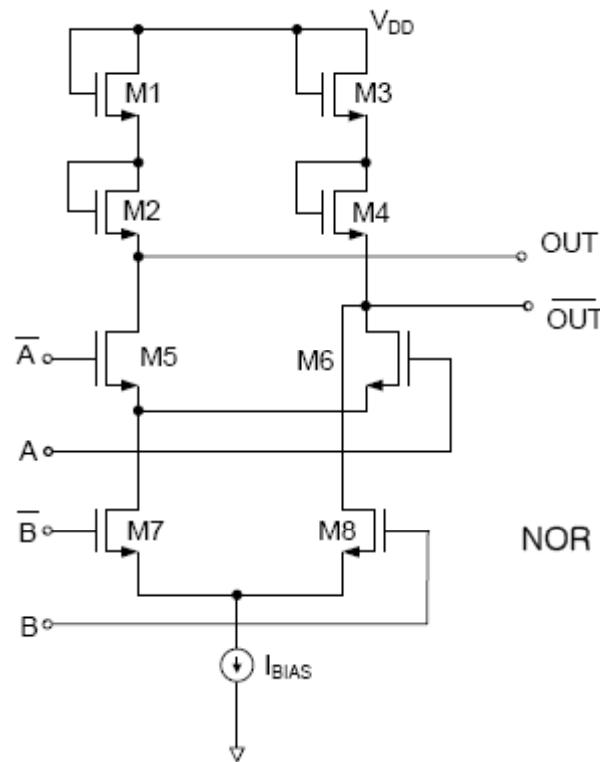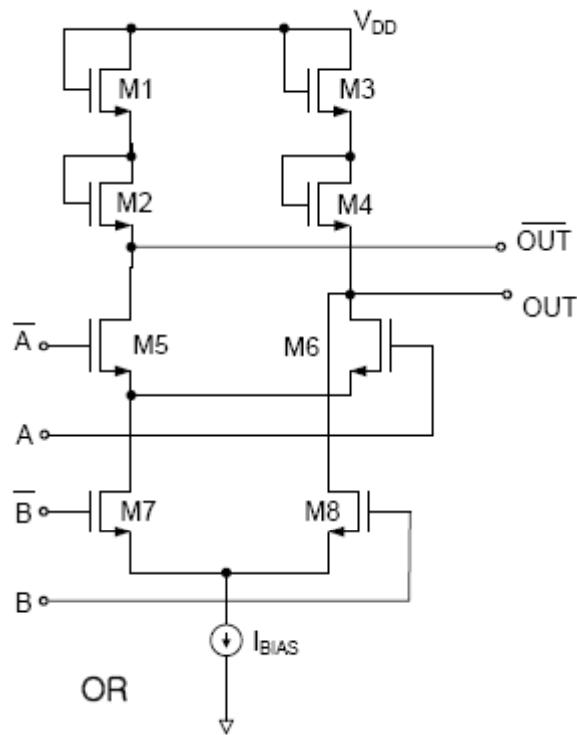

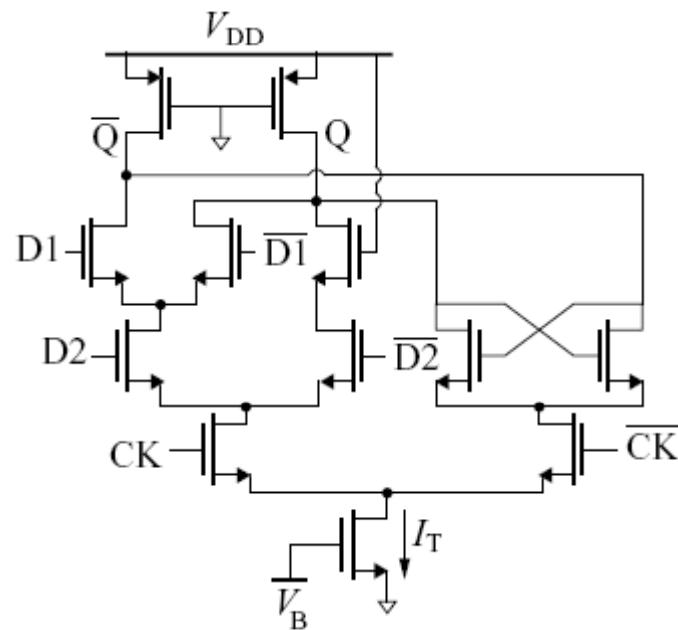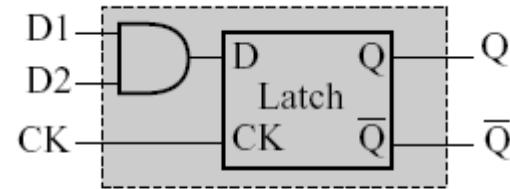

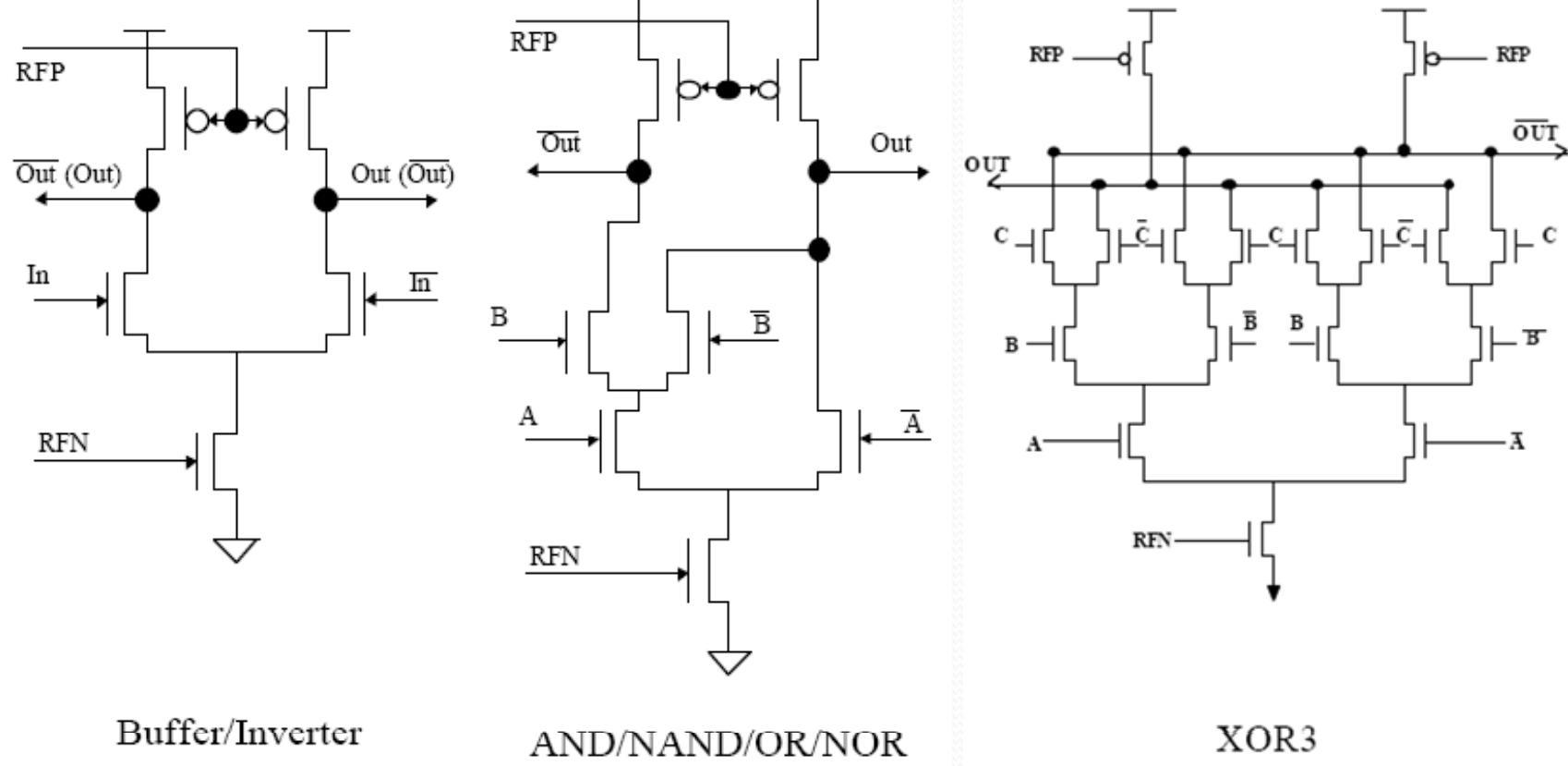Merged AND gate and D-type latch in CML logic



Buffer/Inverter

AND/NAND/OR/NOR

XOR3